

Summary

A commonly asked question from engineers is “How do I use X2Y® components in my circuit?” To answer this question, one must first understand the proper printed circuit board (PCB) pad/trace layout requirements. [Application Note 1001 - X2Y® G1/G2 Attachment](#) is recommended for an explanation of the proper PCB pad/trace layout.

The next step is connecting the X2Y® component into a circuit. It should be noted that X2Y® components are NOT simply a discrete capacitive element, but a capacitive circuit that can be used in several different ways. Therefore, purpose of this application note is to show the advantages of the X2Y® structure as a capacitive circuit and to discuss the two most commonly used circuit configurations, Circuit 1 and Circuit 2.

X2Y® as a Complex Capacitive Circuit

Simply viewing an X2Y® component as a discrete capacitive element overlooks the benefits the unique structure has to offer. To properly implement and use X2Y® Technology, the reader of this application note needs to view the component as a complex capacitive circuit capable of several different modes.

To highlight X2Y® performance vs. a standard discrete element, Figure 1 - Figure 3 uses s21 measurements to investigate the current paths and the performance the structure has to offer as a circuit.

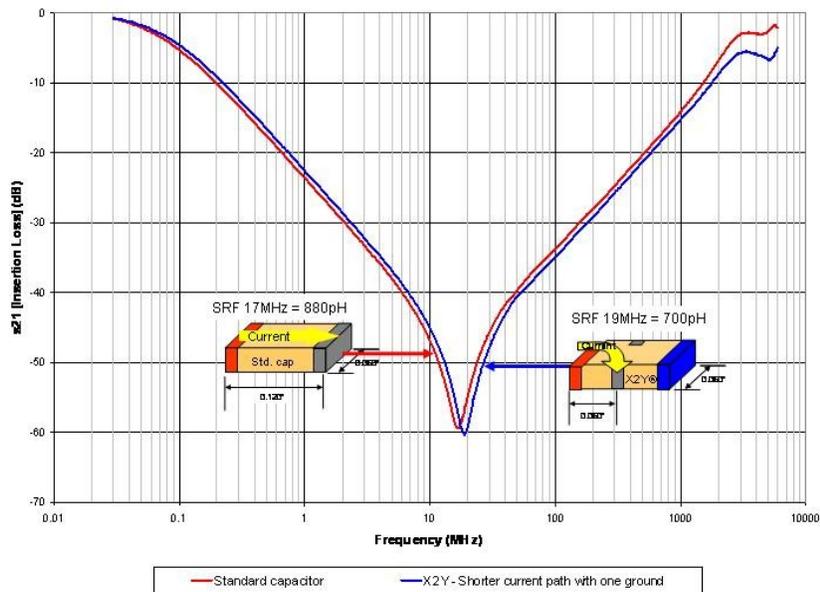


Figure 1. X2Y® has a shorter path to ground which results in a smaller current loop. The result is a 1-2dB improvement in attenuation and 20% less inductance over standard surface mount capacitors.

DISCLAIMER: Information and suggestions furnished in this document by X2Y Attenuators, LLC are believed to be reliable and accurate. X2Y Attenuators, LLC assumes no responsibility for its use, nor for any infringements of patents or other rights of third parties which may result from its' use. X2Y® is a registered trademark. All other brand or product names mentioned in this document are trademark or registered trademarks of their respective holders. These notes are subject to change without notice. Copyright © X2Y Attenuators, LLC all rights reserved.

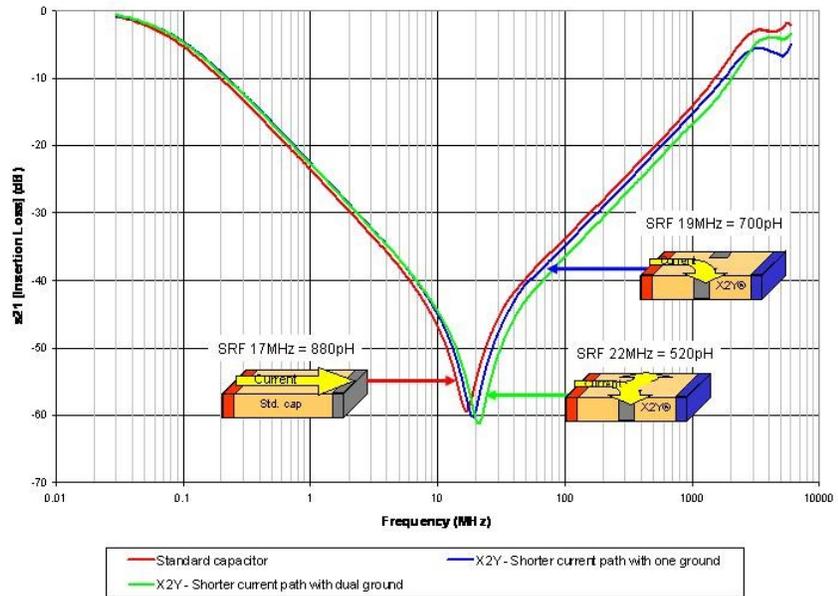


Figure 2. The X2Y® structure is designed for a parallel connection to ground thus reducing attachment impedance. The result is a 3-dB improvement in attenuation and 40% less inductance over standard surface mount capacitors.

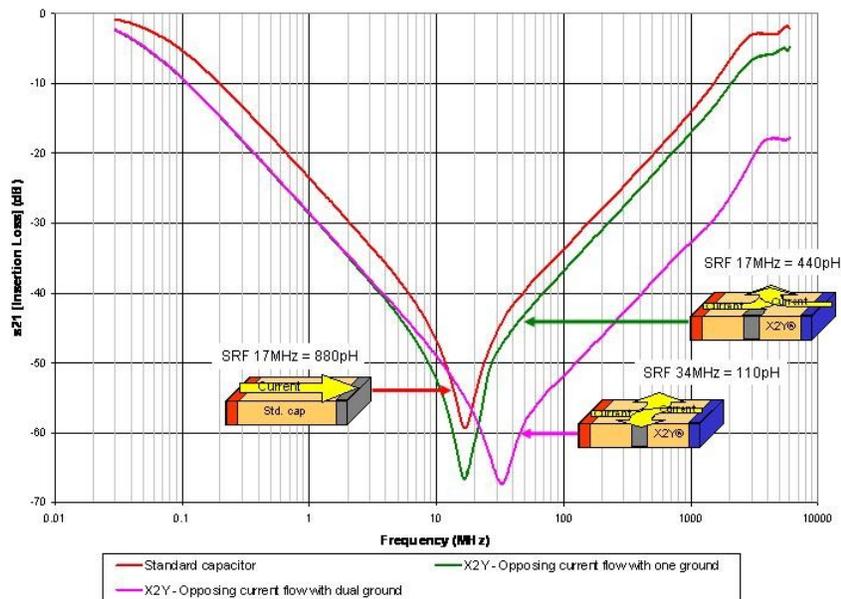


Figure 3. When both the A and B terminals are connected, the structure forces current in opposing directions. When both the G1 & G2 terminals are connected mutual inductance is canceled thus resulting in a 15dB improvement in attenuation and nearly 75% less inductance versus when only a single G terminal is connected. **The key to viewing an X2Y® component as a circuit is to understand the passive cancellation that occurs internally.** Note: when both the A and B terminals are connected the capacitance value is doubled. The standard surface mount capacitor is plotted as a reference.

Circuit 1 & Circuit 2

Let's now evaluate which X2Y® circuit configuration is appropriate for a design. The criteria for Circuit 1 and Circuit 2 configurations are shown in Figure 4.

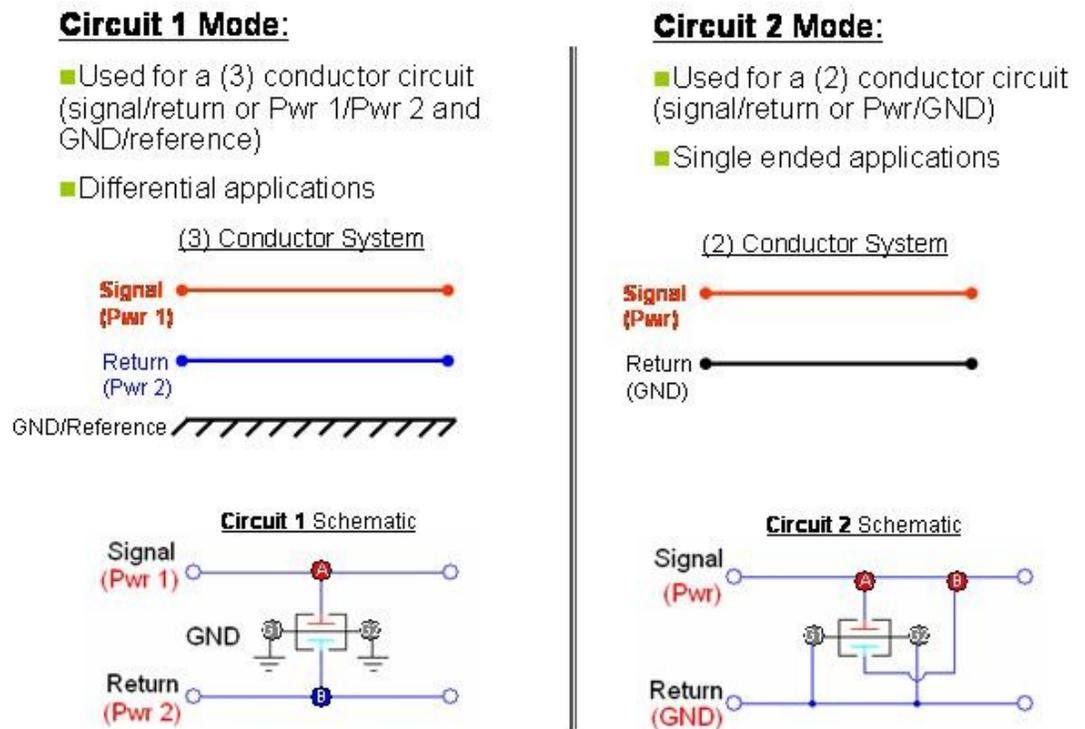


Figure 4. Comparison criteria of Circuit 1 and Circuit 2.

To fully appreciate the electromagnetic differences between Circuit 1 and Circuit 2, let's examine the E- and H-fields internal to the structure of the two different configurations (Figure 5 and Figure 6). (For more information on modeling the internal structure see [Application Note 1003 - Internal Model of X2Y®](#).)

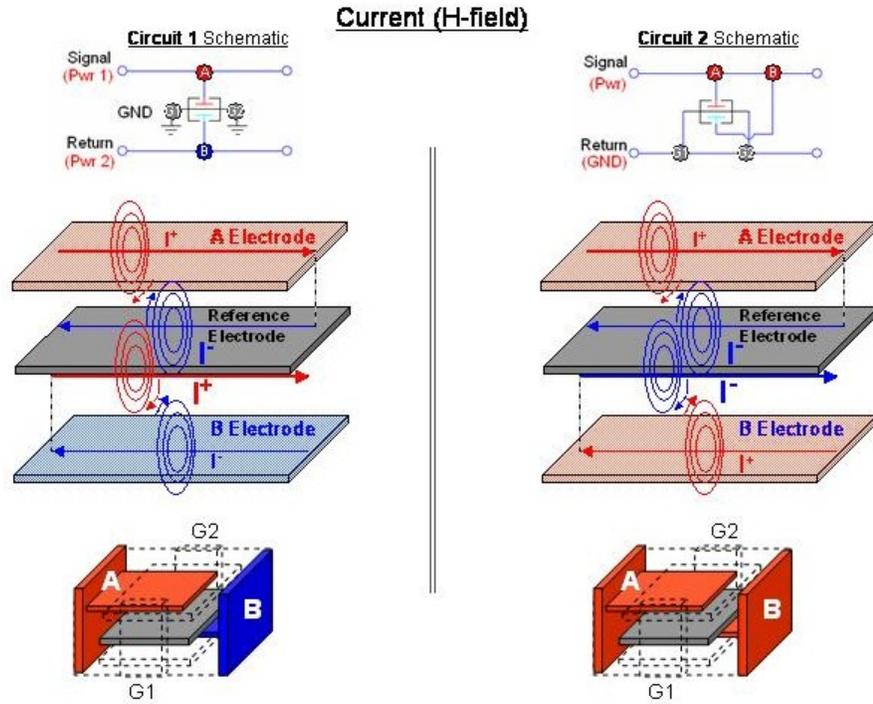


Figure 5. For Circuit 1 and Circuit 2 the H-field cancels internally at the reference electrode.

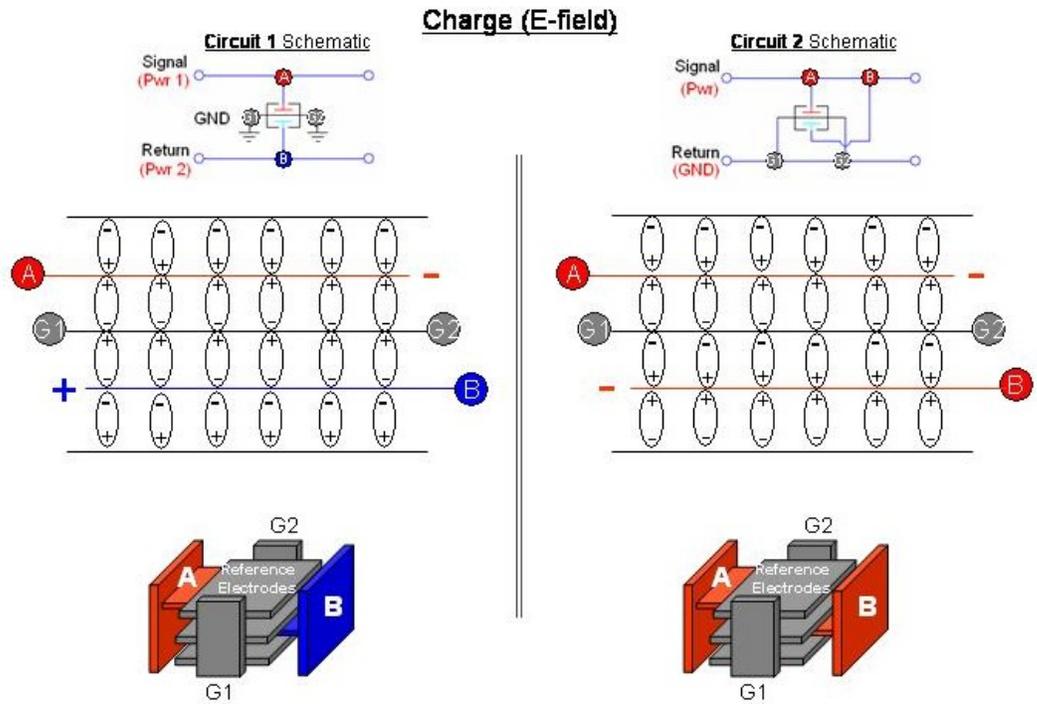


Figure 6. For Circuit 1 the E-field cancels at the shared reference electrode, while for Circuit 2 the E-field is shunted to the reference electrodes, which are attached to the return path.

Selecting a Component Value

Does the circuit configuration matter when selecting a component value? The short answer is YES. When selecting an X2Y® component value for Circuit 1 both the differential (Line-to-Line) and common mode (Line-to-GND) “pass” functions need to be considered. When selecting an X2Y® component value for Circuit 2, only the common mode function (Line-to-GND) needs to be considered. Figure 7 is an example of the differential and common mode “pass” functions.

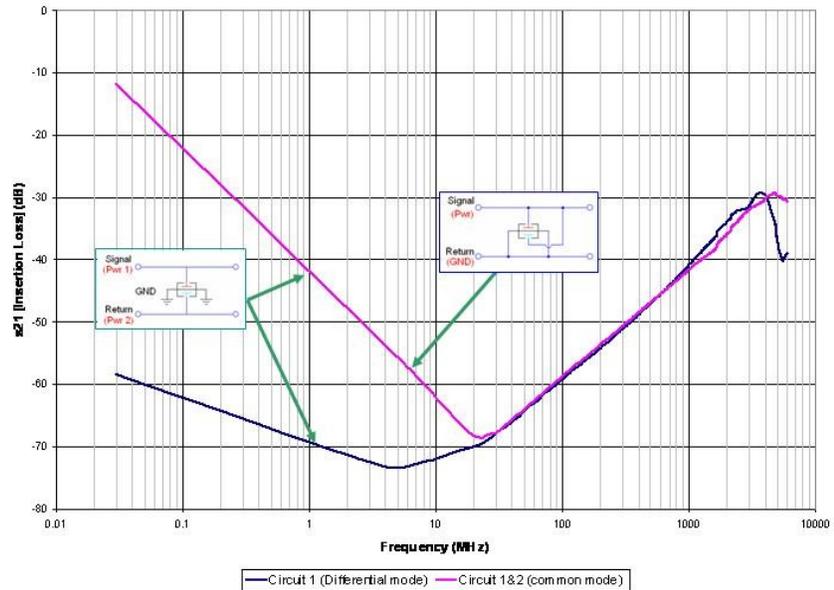


Figure 7. “Pass” Function for Circuit 1 & Circuit 2.

Conclusion

What does this mean to the design engineer? Circuit 1 is the most effective configuration to provide the best broadband filtering and decoupling performance. Circuit 2 is an alternative option for single-ended applications where Circuit 1 use is not possible.

For more information on circuit configurations, applications, or benefits that X2Y® Technology offer go to our website www.x2y.com or use the contact information at the end of this application note to get answer for specific questions.

Note: Performance results reported in this and other application notes can only be achieved with patented X2Y® components sourced from X2Y® licensed manufacturers or their authorized distribution channels.

**Contact
Information**



Direct inquiries and questions about this application note or X2Y® products to x2y@x2y.com or telephone:

X2Y Attenuators, LLC
2730B West 21st Street
Erie, PA 16506-2972

Phone: 814.835.8180
Fax: 814.835.9047

To visit us on the web, go to <http://www.x2y.com>.