

X2Y

®



Technology In Balance

Common Mode Filters

X2Y[®] Capacitors

vs.


Common Mode Filters

Contents


- Common and Differential Mode Noise
- Mode Conversion
- Filter Solutions
- Test Comparisons
- Comparative Applications
- X2Y Capacitor Selection Methodology
- Mounting Suggestions

Common Mode and EMI

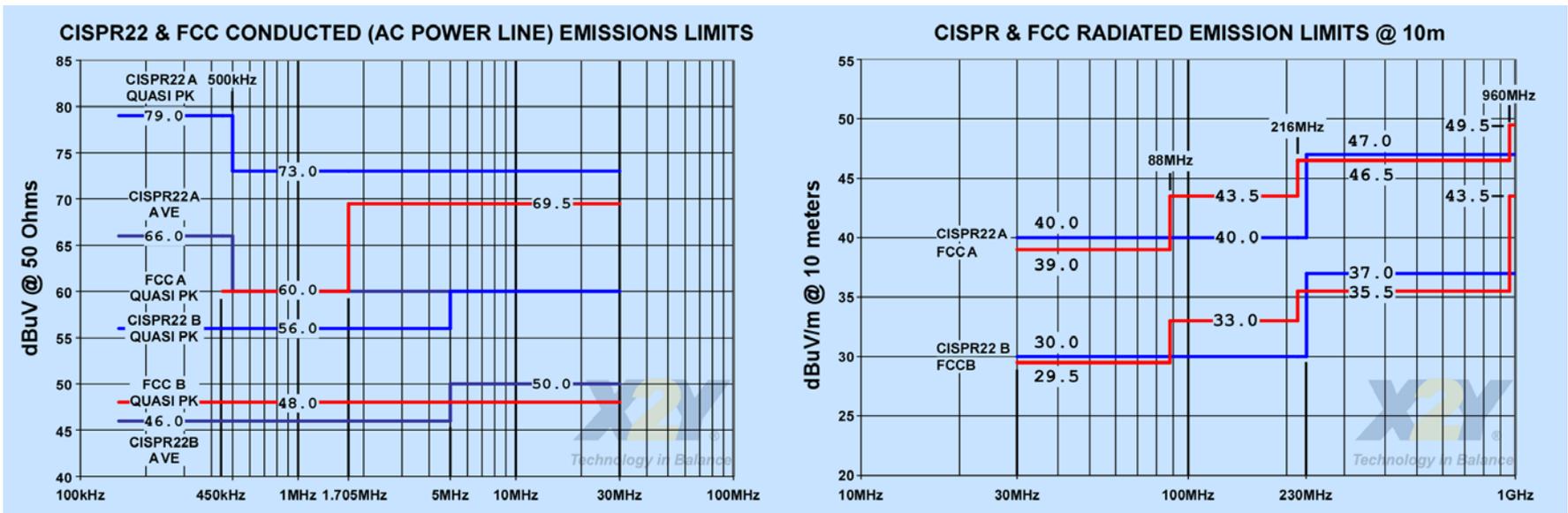- Most EMI compliance problems are common mode emissions.
- Only 10's of uAs in external cables are enough to violate EMC standards.




Common Mode Radiated Noise Model

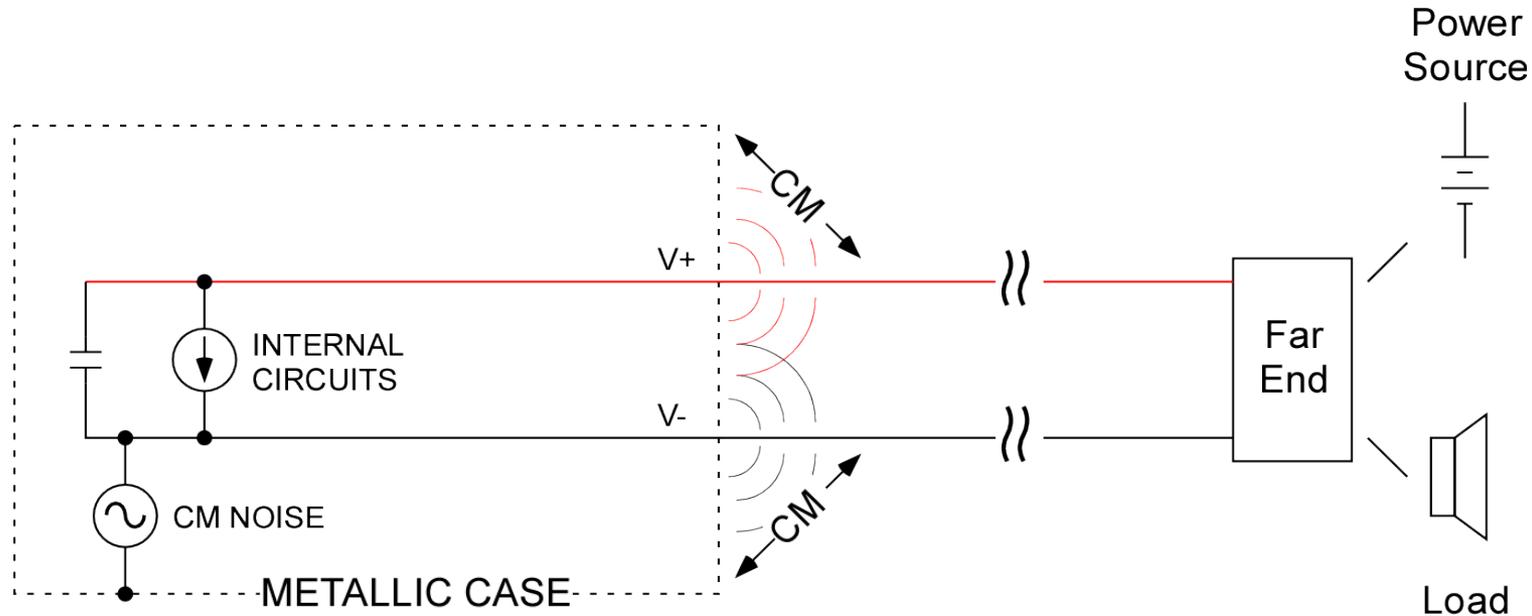


- E field developed between any lead exiting a shielded enclosure and the enclosure outer skin radiates.
- Complementary H field couples to victim antennae.
- Ability to radiate depends on:
 - Power in the noise source
 - Coupling efficiency between the effective antenna structure and the surrounding space
 - Leads and case form the antenna

Common Mode Radiated Noise Model

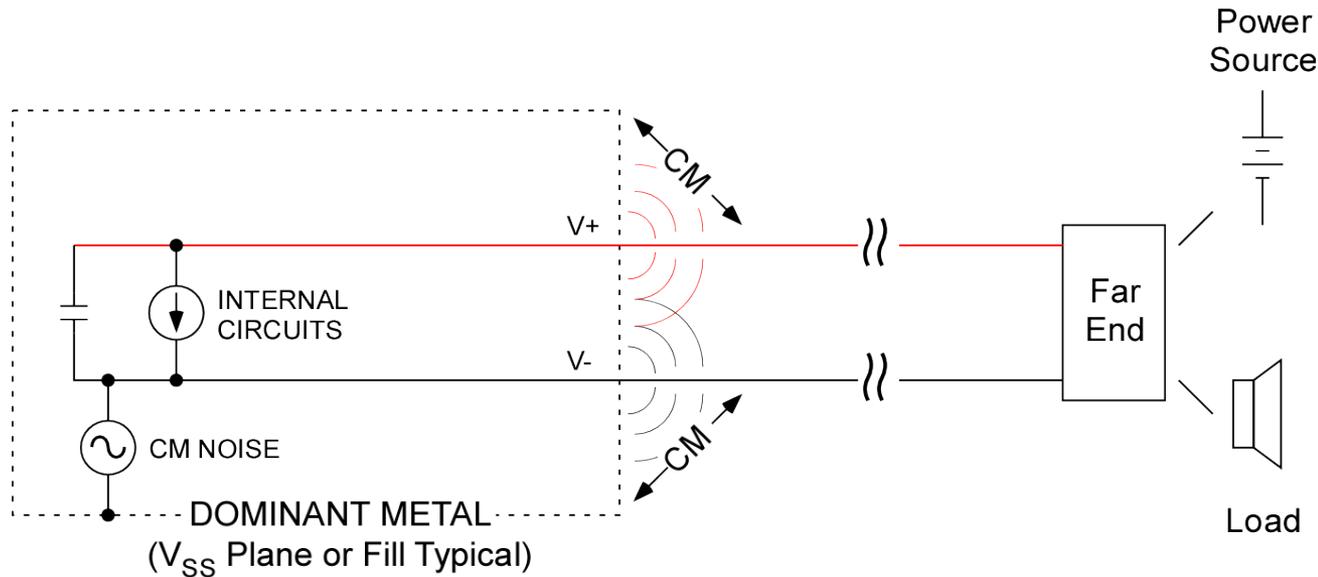

- Device w/o metallic case: “CM” develops between dominant external metal, such as V_{SS} solid polygon, or hatch.

Common Mode Radiated Noise Model

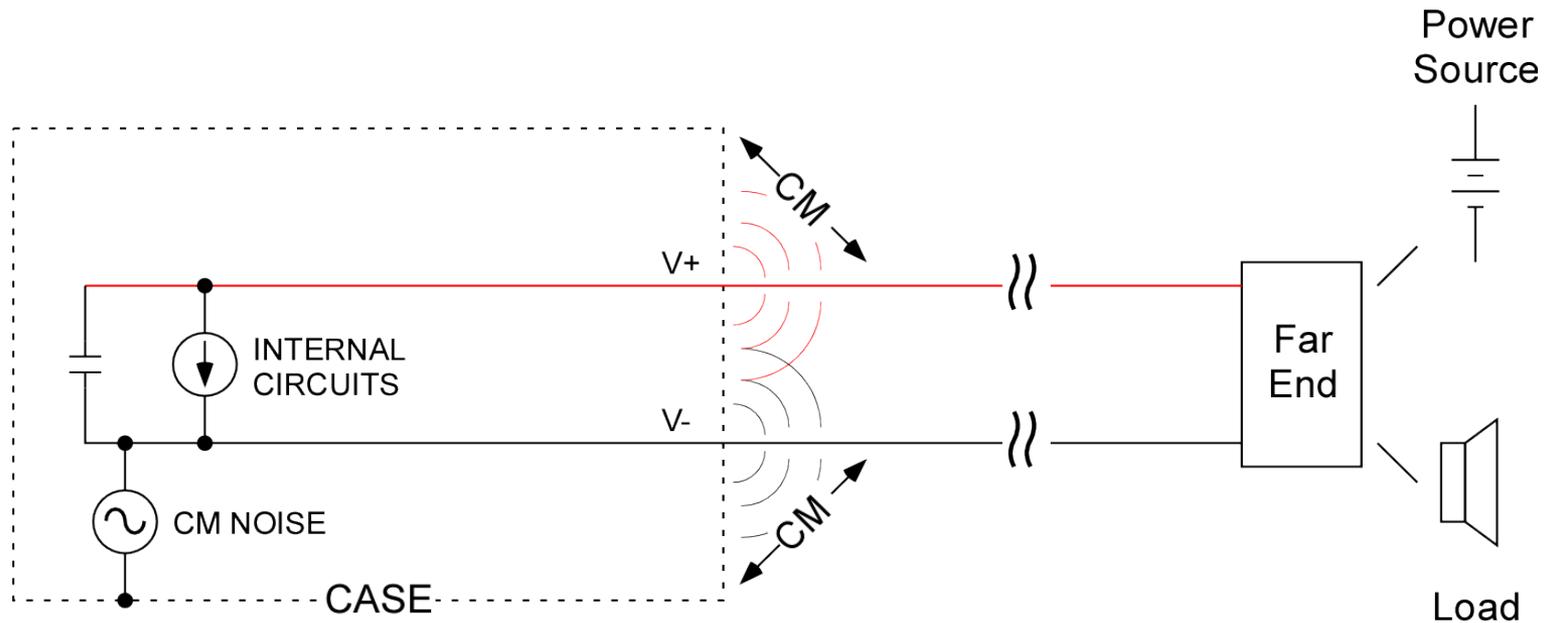


- Reduce radiation by:
 - Reducing potential between the case and leads, AND/OR
 - Reducing coupling efficiency to surrounding space
 - Reduce antenna gain.
 - Mismatch source impedance to the antenna impedance.


Reduce CM Source Power

- Reduce HF current in product
 - Rarely an option
- Decrease shunt impedance to case
 - Optionally insert additional series impedance between source and shunt
 - Effectiveness requires low impedance compared to the source and antenna.


REDUCE SOURCE POWER

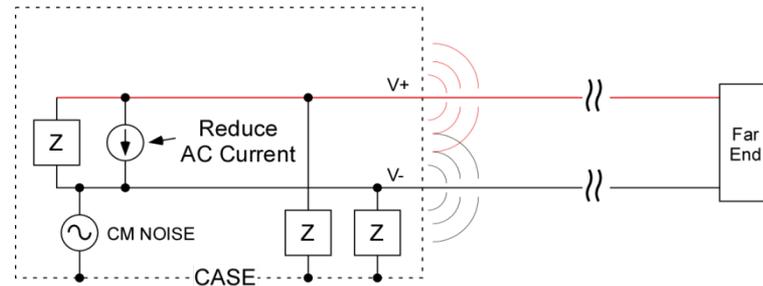

AND/OR

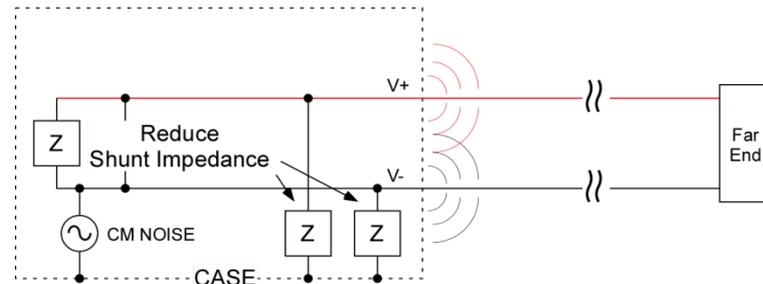

AND OPTIONALLY


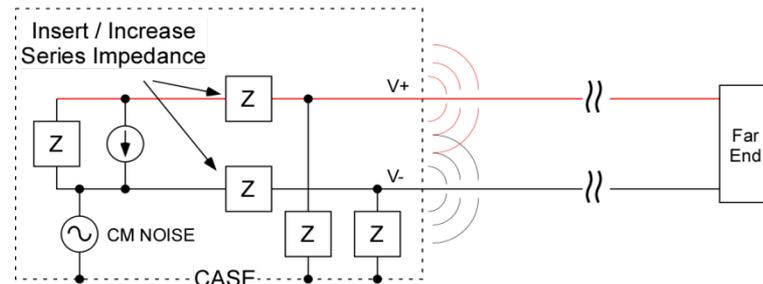


Reduce Coupling



- Reduce antenna efficiency
 - Cable length
 - Cable routing / shielding
- Mismatch antenna impedance
 - Increase driving impedance $\gg 377 \text{ Ohms}^*$
 - Inserted Z effective when $\gg Z_{\text{SOURCE}} + Z_{\text{ANTENNA}}$
 - Decrease driving impedance $\ll 377 \text{ Ohms}^*$
 - Inserted Z effective when $\ll Z_{\text{ANTENNA}}$

* Antenna impedance may be anywhere from 10's to 100's of Ohms
Typically 100 – 180 Ohms


REDUCE COUPLING EFFICIENCY

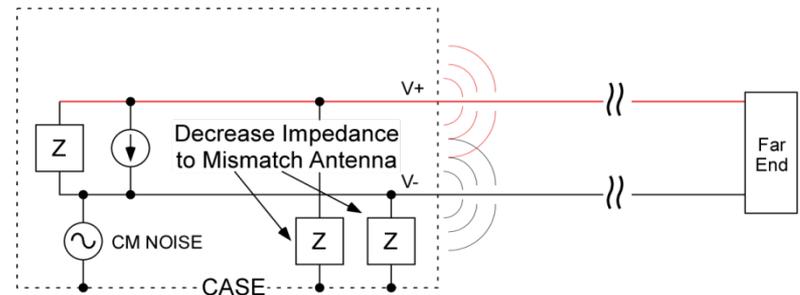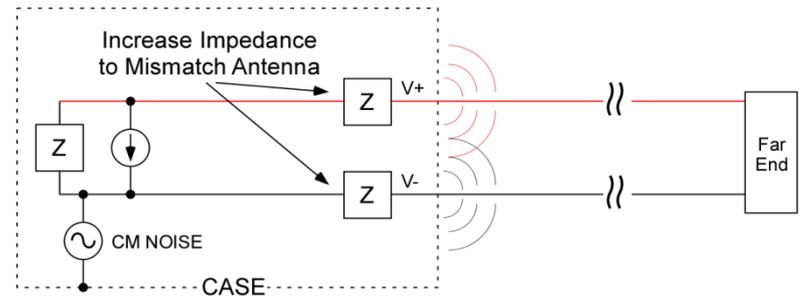

EMI Filter Attenuation

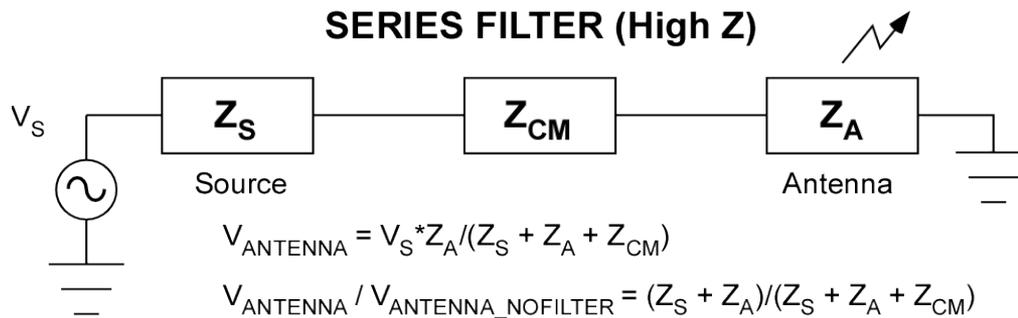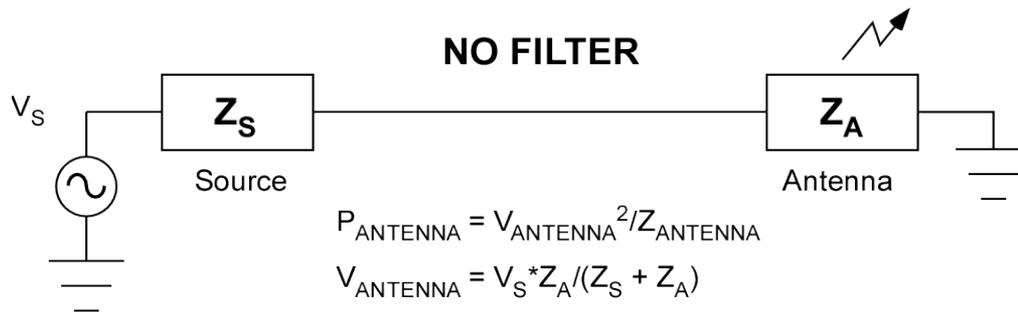

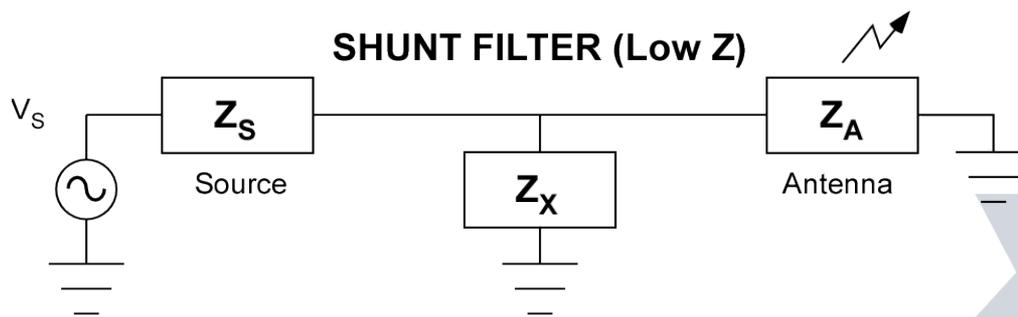EFFECTIVENESS CRITERIA:
 $Z_{CM} \gg (Z_S + Z_A)$




EFFECTIVENESS CRITERIA:
 $Z_X \ll Z_S || Z_A$

$V_{\text{ANTENNA}} = V_S * (Z_A || Z_X) / (Z_S + Z_A || Z_X)$
 $V_{\text{ANTENNA}} / V_{\text{ANTENNA_NOFILTER}} = Z_X / (Z_X + (Z_S || Z_A))$



Differential Mode Radiated Noise Model

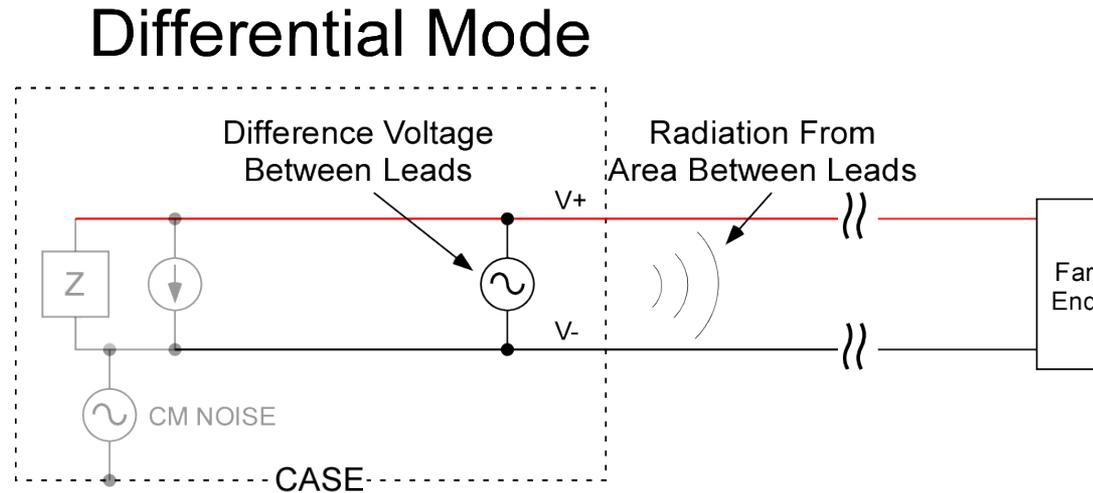


- Voltage(s) between multiple leads that form an antenna in the area between.

Mode Conversion


- Occurs when individual filters are not matched.
- Differential signal energy converts into common-mode energy.
- Common-mode energy converts into differential energy.
- Avoid by matching filters throughout stop-band.
- Not an emissions concern where signals do not exist in the noise stop band.
- Mode conversion is a susceptibility concern at all frequencies.

Single Chokes / Beads as EMI Filters

- Chokes attenuate noise emissions when they substantially increase the total noise source impedance relative to the antenna impedance.
 - Insertion loss in dB is:
 - $20\text{LOG}((Z_S + Z_A)/(Z_S + Z_A + Z_{\text{CHOKE}}))$
- Bead impedance is limited by effective parallel resistance.
 - 600 Ohm bead max insertion loss:
 - -17dB: 50Ω source / 50Ω antenna
 - -12dB: 50Ω source / 150Ω antenna
- Chokes and beads limited at high frequency by parasitic mounted capacitance.
 - Device & mounting structure capacitance in parallel
 - PCB layout & adjacent components can defeat insertion loss

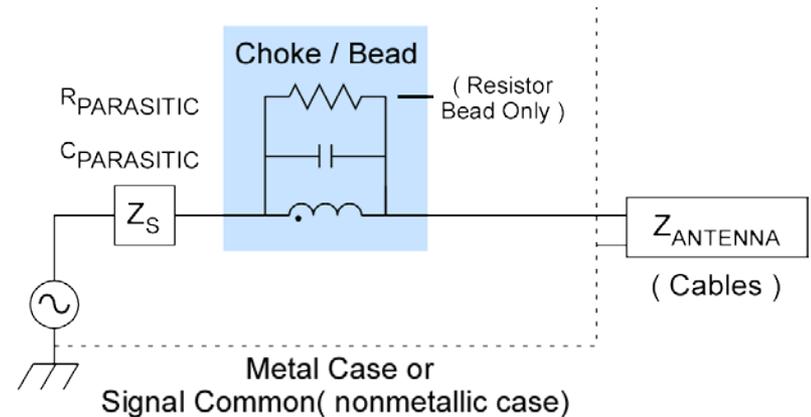


Choke / Bead Series Impedance Asymptotes

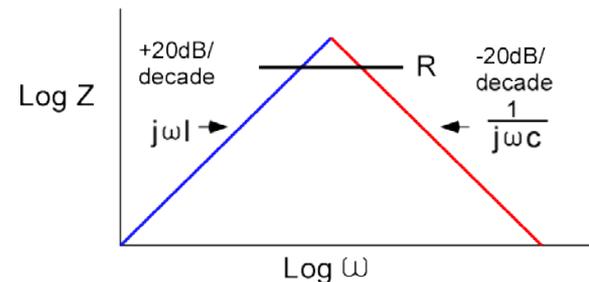


CM Choke Mechanics

- A CM choke couples chokes on a common core
 - Usually two windings / core.
 - Coupling improves CM rejection on each lead in the stop band,
 - CM chokes can pass differential signals in the stop band.
- A CM choke is a 1:1 transformer where the primary and secondary are both driven.
 - Both windings act as both primary and secondary.
 - Current through one winding induces an opposing current in the **other** winding.
 - For K close to 1.0, total effective CM impedance is:
 - $Z \approx 2\pi F * L_{MAG}$
 - 2X what two independent chokes with the same L_{MAG} would yield.

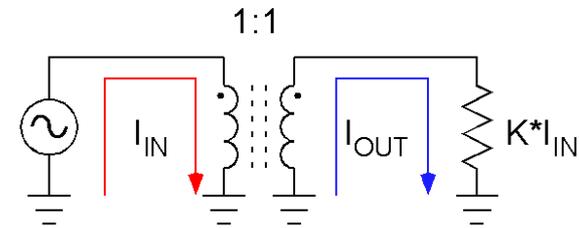

1:1 Transformer, $0.95 \leq K \leq 0.99$

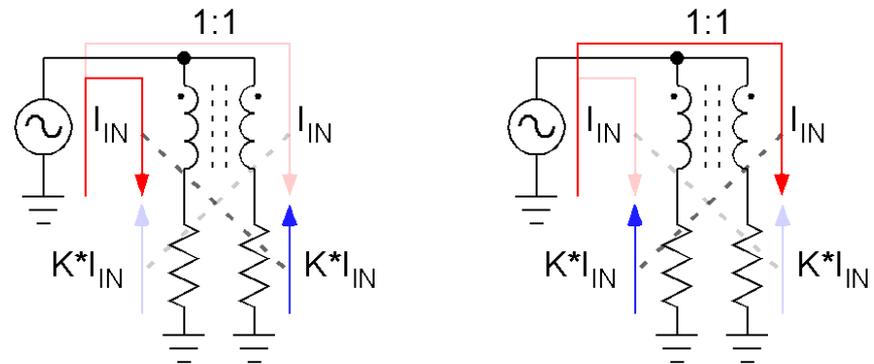


$$I_{OUT} = 2 * (V_{IN} / Z * (1 + K))$$

CM CHOKE, $0.98 \leq K \leq 0.99$

CM Choke Mechanics


- CM choke winding coupling **DOES NOT** cancel all or even a high percentage of CM noise.
- CM chokes **DO** increase CM inductance **up to 2X** compared to each of two independent chokes of the same open circuit inductance rating.
- CM chokes **DO** cancel most core flux allowing much higher CM currents w/o saturation than two independent chokes of the same material and core size.
 - Allows DC and AC to pass as differential currents w/o killing CM attenuating inductance
 - Important to power filter applications that use chokes
 - DC balance must be maintained in wiring and load.

CM CHOKE DC FLUX CANCELLATION

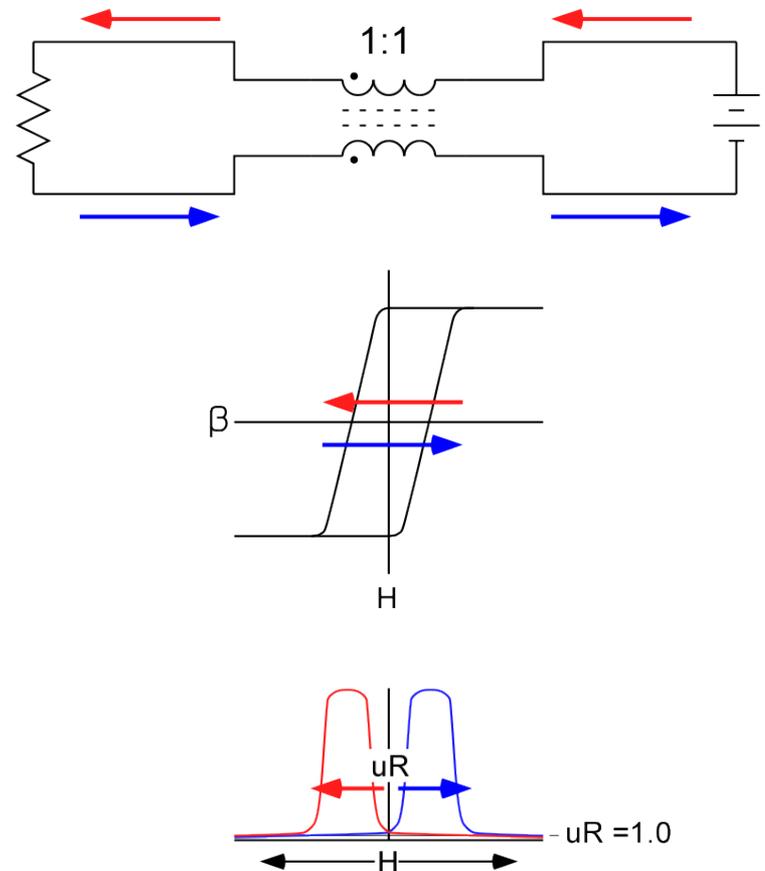

CM Choke Mechanics


- Just as with individual chokes / beads, parasitic capacitance limits the effective frequency range of CM chokes.
- For a given core material, the higher the inductance used to obtain lower frequency filtering, the greater the number of turns required and consequent parasitic capacitance that defeats high frequency filtering.
- At frequencies $> F_{SRF}$, parasitic capacitance defeats impedance gain from coupled windings.

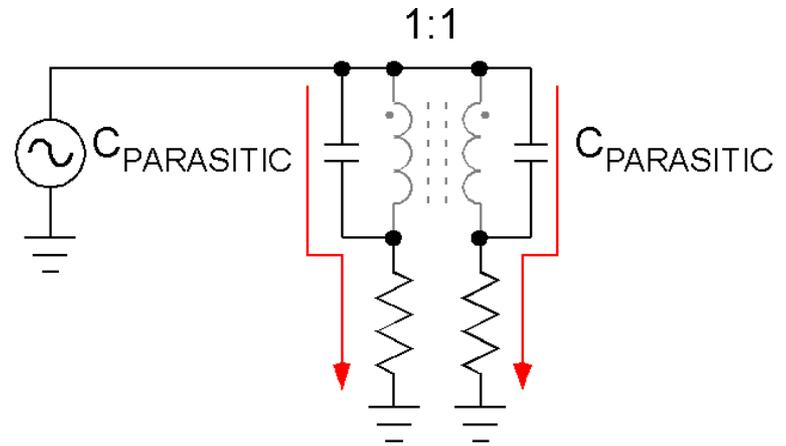


Capacitor current bypasses the transformer coupling.
At frequencies $> F_{RES}$ impedance is capacitive and low.

Choke/Bead/CM Choke Bandstop

- Insertion loss declines past F_{SRF} due to parasitic shunt capacitance.
 - Parasitic capacitance, noise source impedance and lead antenna impedance define high frequency noise attenuation.
 - Parasitic capacitance is combined effects of the CM Choke and the CM Choke PCB mount.
 - Very small capacitances, < 1pF can have very big effects above 100MHz
 - 1pF Limits 1GHz Insertion Loss:
 - -8dB: 50Ω source / 50Ω antenna
 - -5dB: 50Ω source / 150Ω antenna
- $F_{\text{SRF}} = 1/(2\pi(\sqrt{L_{\text{CM}} * C_{\text{PAR}}}))$

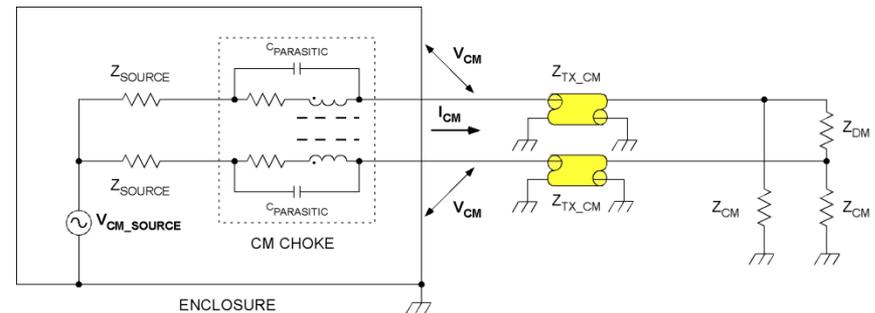


Insertion Loss Characteristics
CM Choke

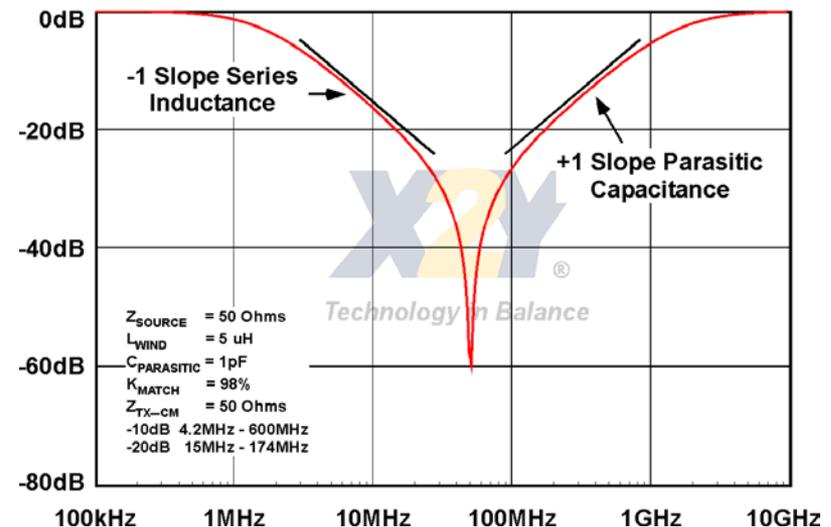



CM Chokes Winding Mismatch

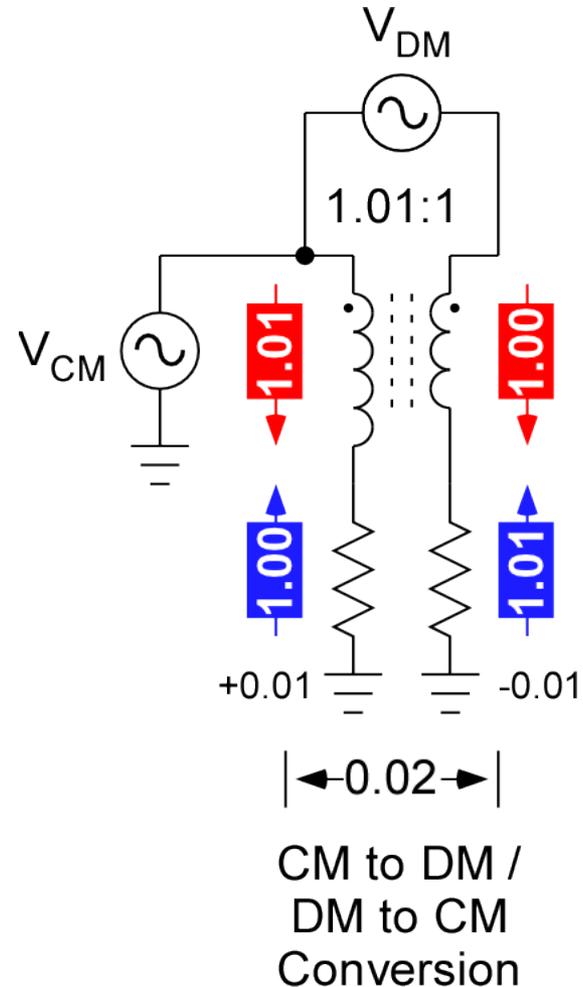- Mismatch between windings from mechanical manufacturing tolerance causes mode conversion.
 - A percentage of signal energy converts to common mode, and vice-versa.
 - This gives rise to EMC issues as well as immunity issues.
- Mismatch reduces the effective inductance in each leg.
 - $L_{\text{EFF}} \approx L_{\text{MAG}} * (1 + K_{\text{MATCH}})$
 - $0.9 < K_{\text{MATCH}} < 0.99$



CMCs Stop Band Mode Conversion

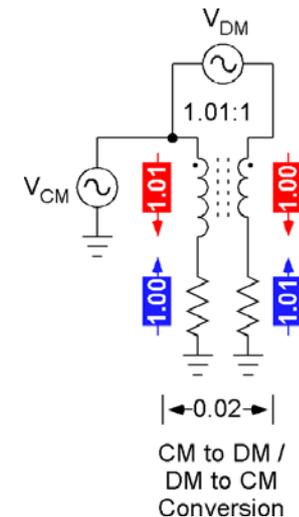
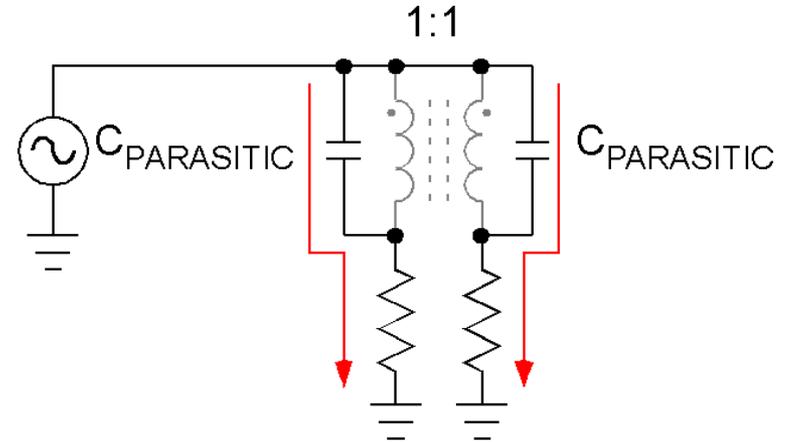
- Parasitic capacitance and winding mismatch both defeat inductive cancellation in the stop band causing mode conversion.
- Not a major radiation concern where signal energy is negligible in the stop band.
 - Conditions under which a shunt filter is a viable alternative.



CMCs Mode Conversion Susceptibility


- ESD discharge onto case induces common mode voltage onto cables.
 - Standard test waveform leading edge knee frequency: 300-500MHz
- Mode conversion increases susceptibility of internal circuits to outside noise:
 - 1% Magnetics mismatch => 2% of CM voltage appears as difference voltage across leads
- Similar mechanics for power leads.

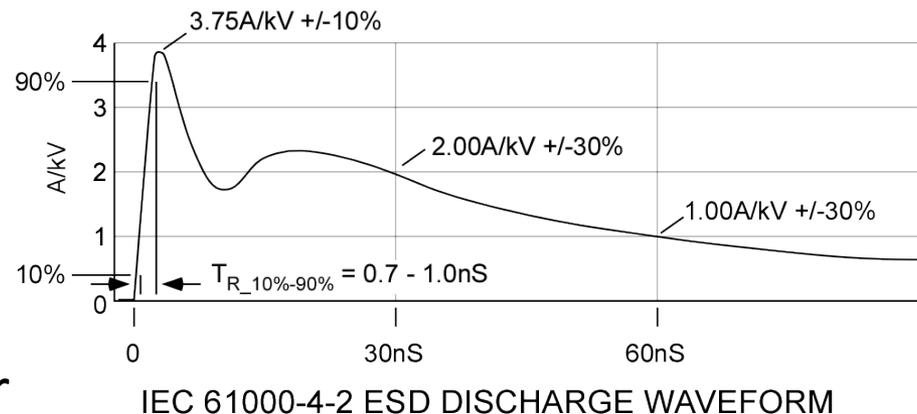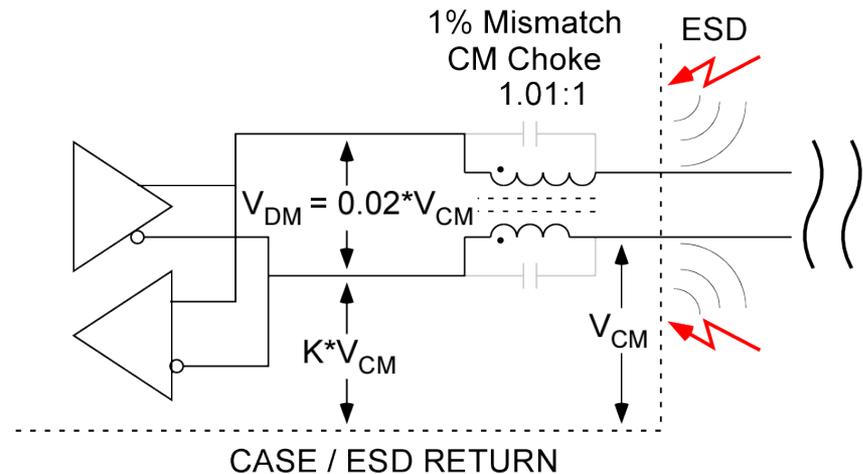CM CHOKE ESD / EFT SUSCEPTIBILITY
DUE TO MODE CONVERSION BELOW F_{SRF}




CMCs Mode Conversion Susceptibility

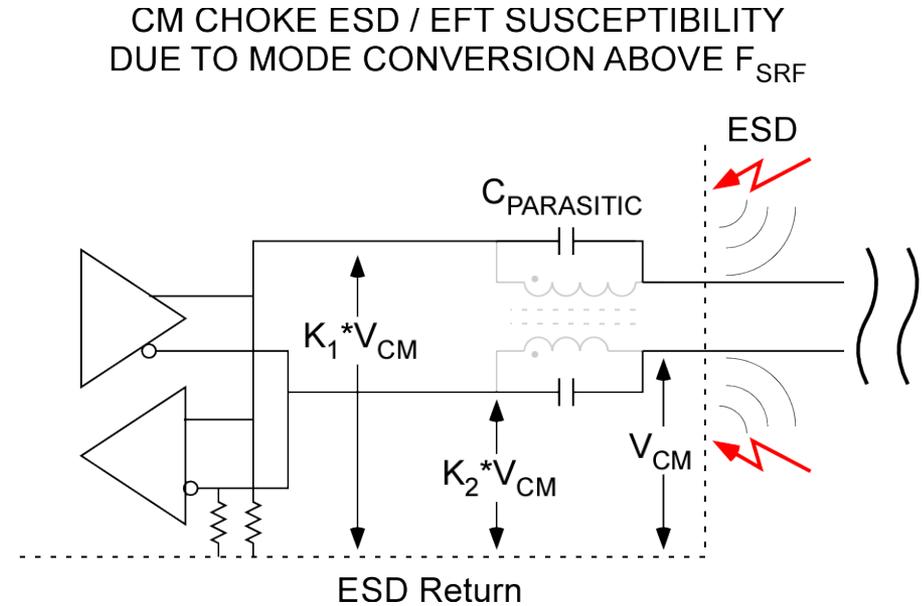- At frequencies above filter F_{SRF} , voltage passed through each winding depends on:
 - Choke parasitic capacitance,
 - Layout, and
 - IC input matching.
- Add transient voltage suppression devices, TVS, to protect ICs / power system





CM Chokes as EMI Filters

- CM chokes have one really good application:
 - Signals must be passed that operate in the same frequency range as CM noise that must be suppressed.
 - Mode conversion and winding mismatch is a major concern in these applications.
- Otherwise: CM chokes are: large, heavy, expensive, and subject to vibration induced failure.
- Estimating CM performance
 - Example: $4.7\text{mH } L_{\text{CM}}, 3\text{pF } C_{\text{PAR}}$
 - $F_{\text{SRF}} = 1.3\text{MHz}$
 - $IL_{\text{dBMAX}} = 20\text{LOG}(100/8.4\text{E}6)$
 - $\approx -52\text{dB}$

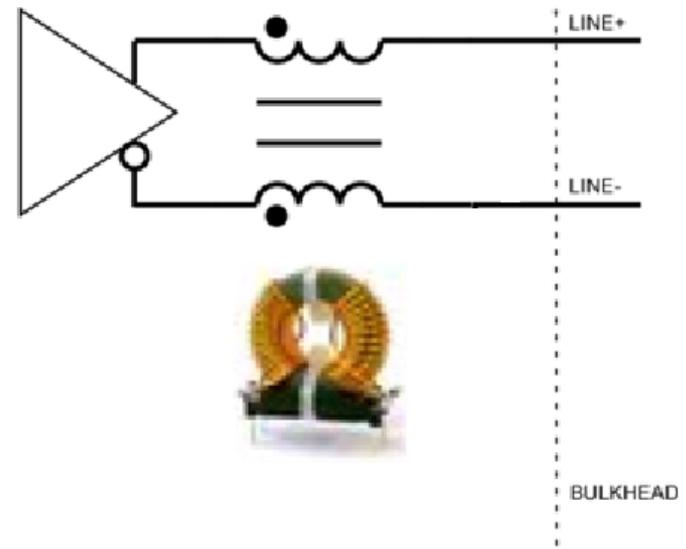


X2Y[®] Capacitors, Nearly Ideal Shunts

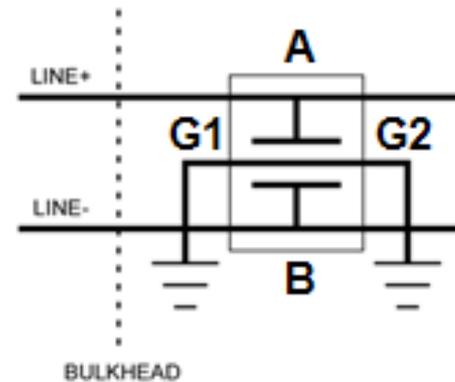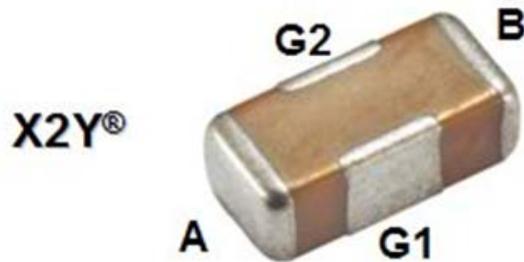- Two closely matched capacitors in one package.
 - Effects of temperature and voltage variation eliminated
 - Effect of ageing equal on both lines
- Very low inductance between terminals.



X2Y[®] Capacitors, Nearly Ideal Shunts

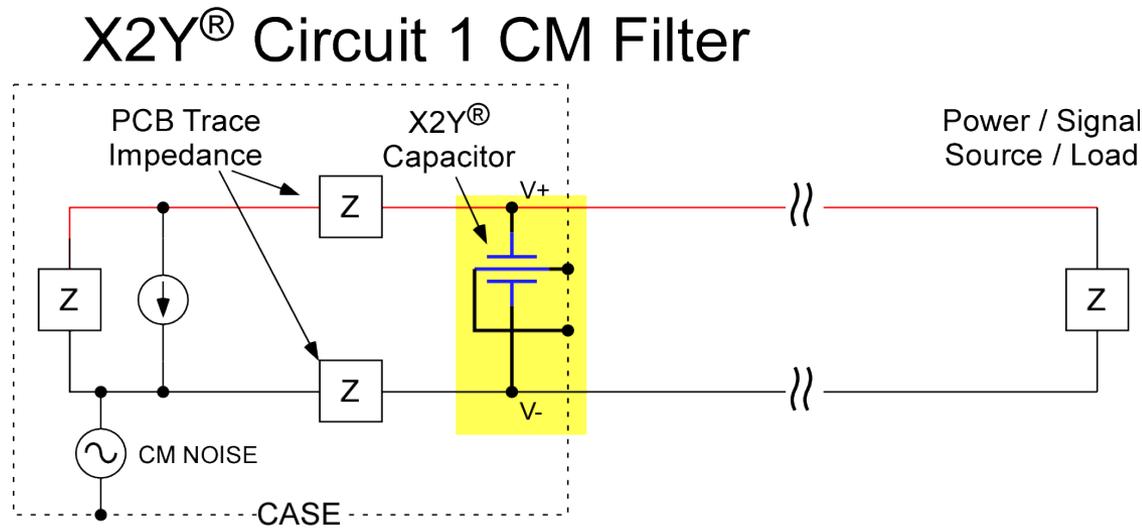
- When properly applied, X2Y[®] capacitors filter CM noise by **both** attenuating source energy, and mismatching antenna impedance.
- The key is very low, and matched inductance.
- Proper application must mind inductance in the common path: G1/G2 terminals.



X2Y[®] Capacitors, Nearly Ideal Shunts


- X2Y[®] capacitor shunts between A, B, and G1/G2 attachments.
 - Component inductance is very low:
 - $\approx 110\text{pH}$ from each A or B to G1/G2.
- Low impedance shunt serves two purposes:
 - Divides noise voltage
 - Mismatches external antenna impedance
 - Reflects inside noise back inside
 - Reflects external noise: EFT/ESD back towards outside.
- Performance is typically limited by external capacitor mounting inductance relative to protected traces and RF common:
 - L3A/L3B, L4A, L4B
 - Minimize w/ best practices
 - See slides 52-54 for technique
 - RF common is the case for metallic enclosures.
 - RF common is circuit common for non-metallic enclosures

X2Y[®] Circuit 1 CM Filter

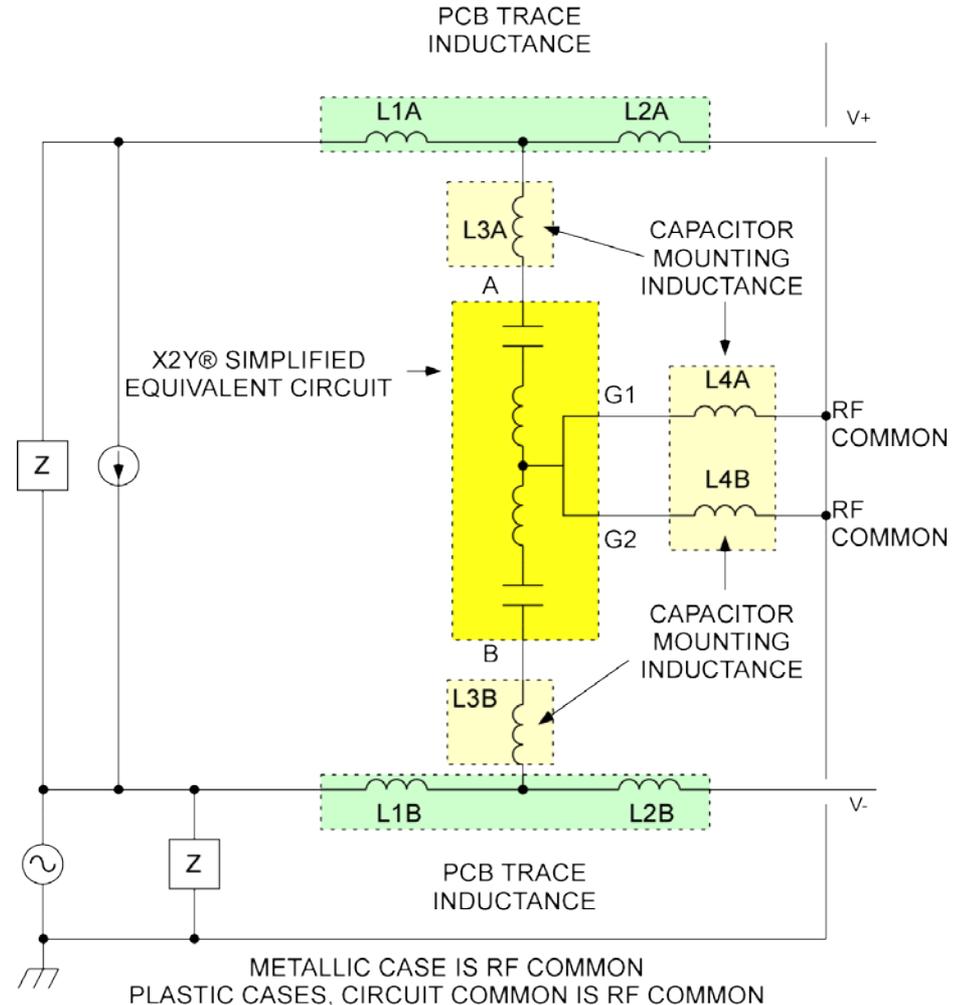


X2Y[®] Bandstop

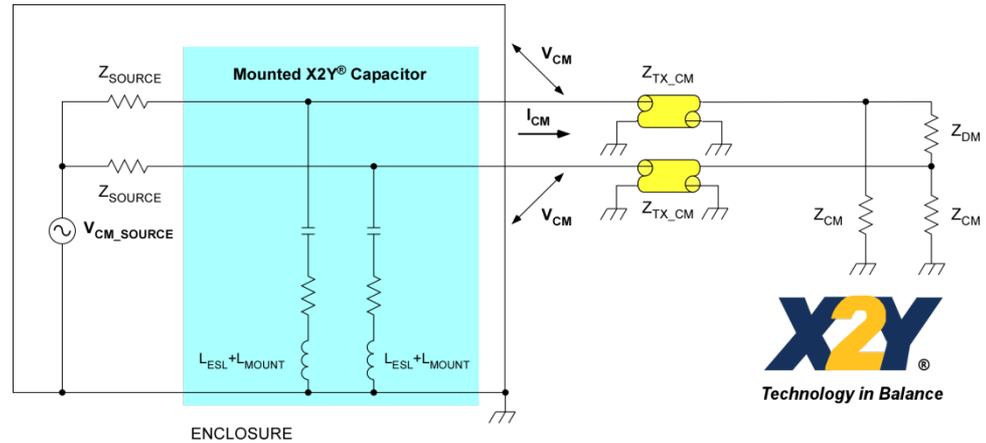- Insertion loss builds up to F_{SRF} due to parallel capacitance.
- Insertion loss declines past F_{SRF} due to parasitic common inductance.
- Y capacitor mismatch reduces insertion loss below F_{SRF} .
 - Increases low frequency cut-off by $\approx 2/(1 + K_{\text{MATCH}})$
 - $0.9 < K_{\text{MATCH}} < 0.99$
 - Generally no concern




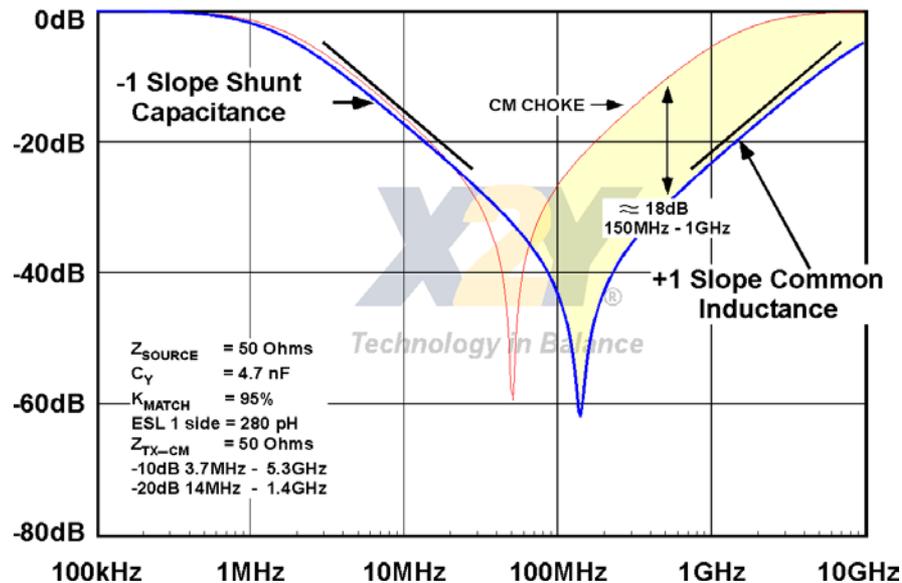Insertion Loss Characteristics
X2Y[®] Capacitor



X2Y[®] vs. CM Choke Bandstop

Insertion Loss Characteristics

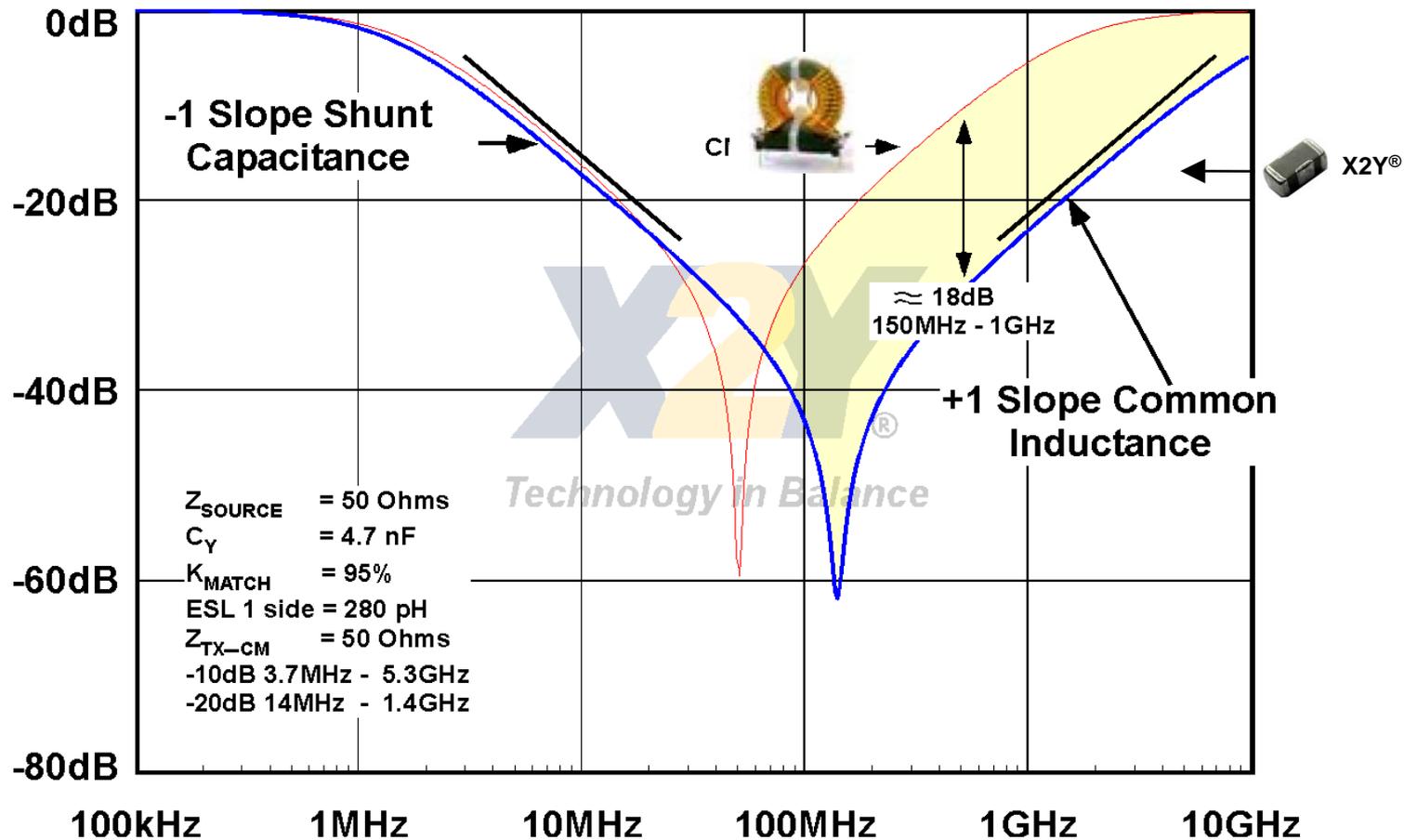

X2Y[®] Bandstop

- **Insertion Loss:**

$$20\text{LOG}(Z_{X2Y}/(Z_{X2Y}+(Z_{\text{SOURCE}} || Z_{\text{ANTENNA}})))$$

- **Low frequency performance** determined by X2Y[®] capacitance.

- Increase capacitance as required to set filter lower cut-off frequency.

- **High frequency attenuation** determined by:

- Mounted capacitor common inductance.
- Essentially constant across X2Y[®] values.


- **Insertion Loss @1GHz**

- Using 4mil top dielectric PCB
- -24dB: $50\Omega Z_{\text{SOURCE}} / 50\Omega Z_{\text{ANTENNA}}$
- -27dB: $50\Omega Z_{\text{SOURCE}} / 150\Omega Z_{\text{ANTENNA}}$

- **Unique X2Y[®] advantage:**

- Larger capacitors do not hurt HF performance.

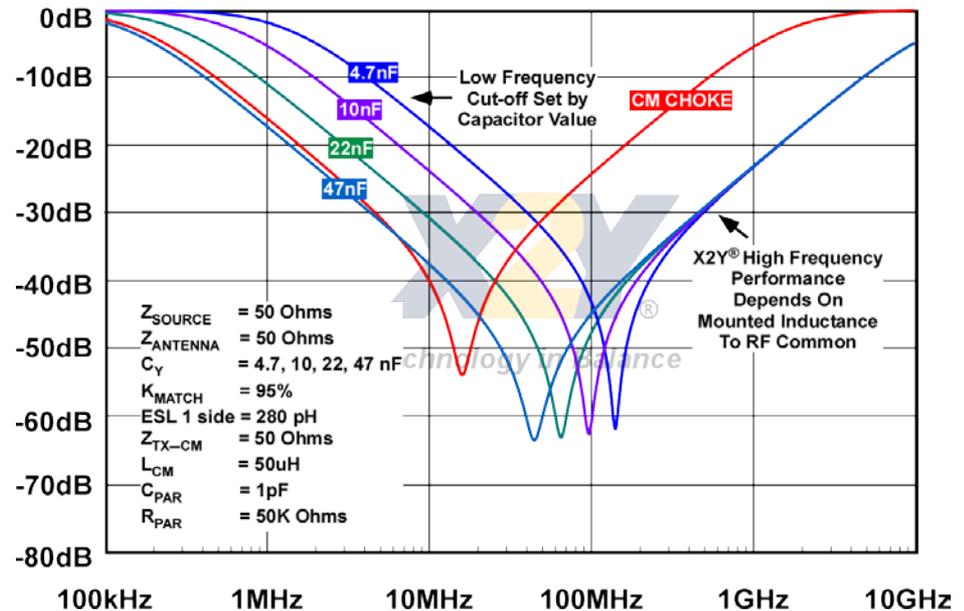**Insertion Loss Characteristics
X2Y[®] Capacitor**




X2Y[®] and ESD/EFT Susceptibility


X2Y[®] ESD SUSCEPTIBILITY

- X2Y[®] is a shunt solution with very low and **matched** parasitic inductance.
 - Common mode attenuation is high over a wide frequency range.
 - Mode conversion has two contributors:
 - @Low frequencies: capacitor value matching.
 - @High frequencies: inductance matching.

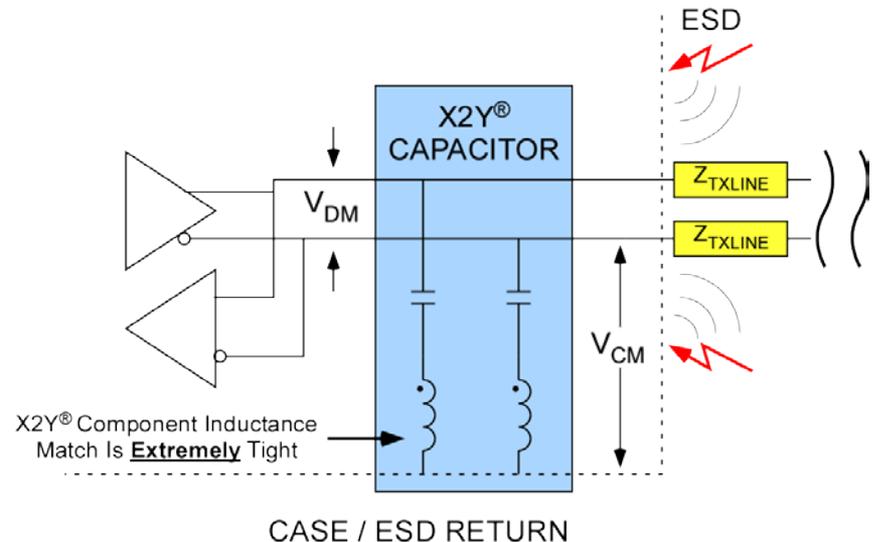- Mode conversion for 1nF and larger parts, @ 350MHz is better than -50dB




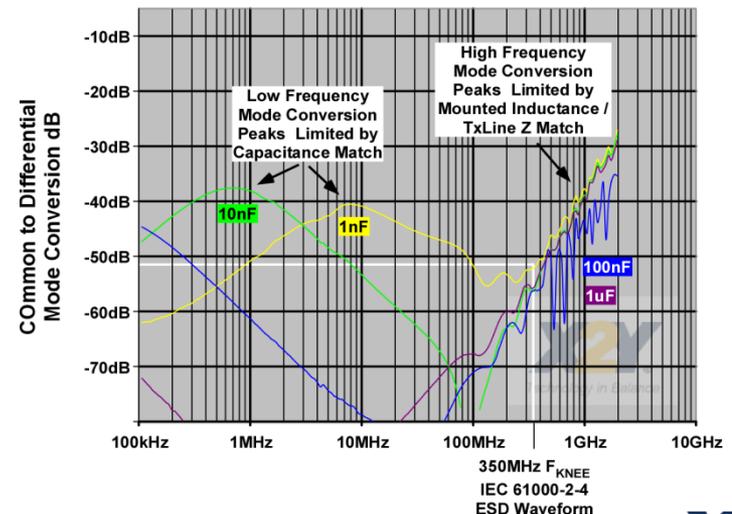CASE / ESD RETURN
Measured Common to Differential Mode Conversion
X2Y[®] 0603 Capacitors



X2Y[®] and ESD/EFT Susceptibility


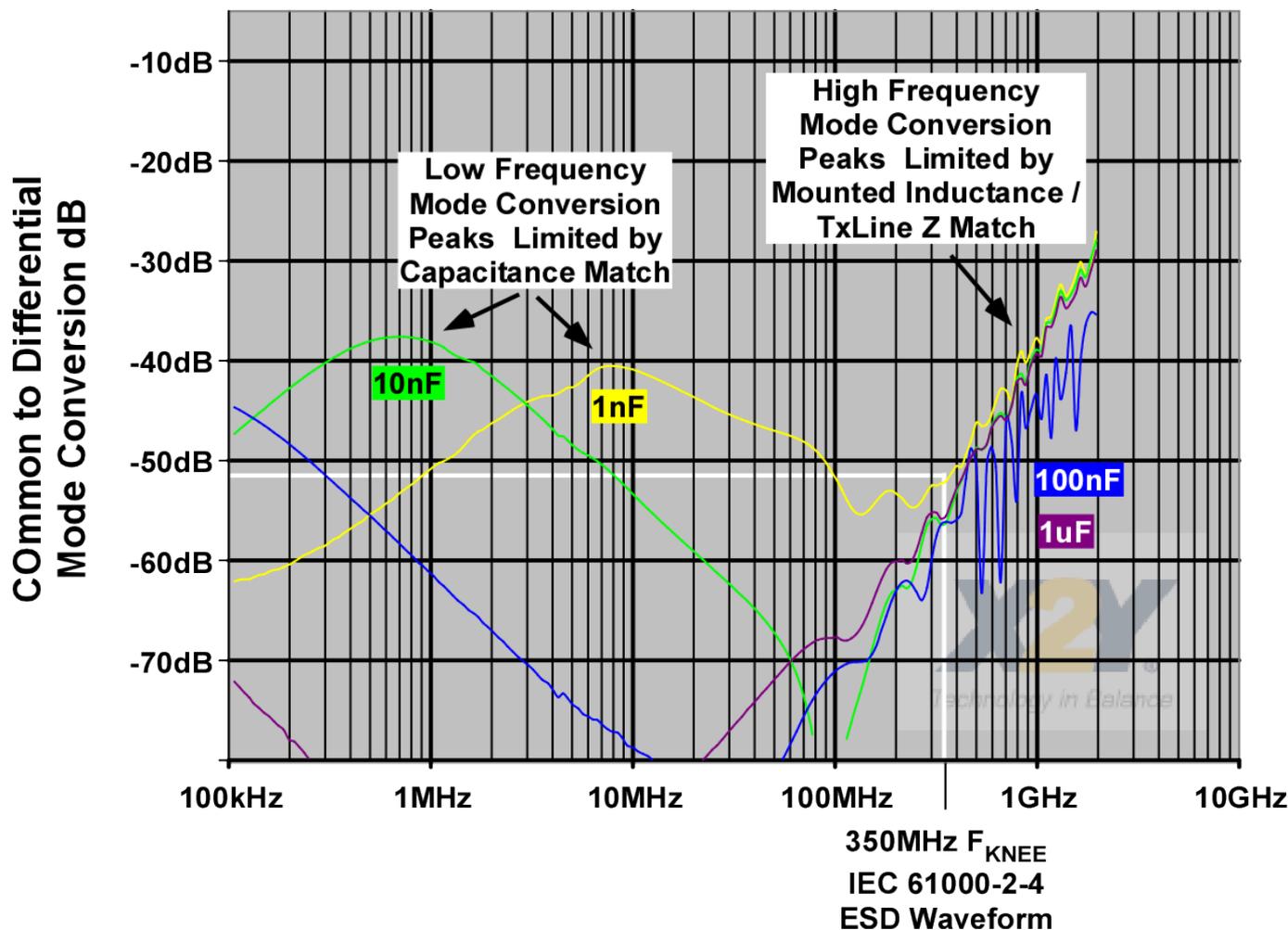
Measured Common to Differential Mode Conversion X2Y[®] 0603 Capacitors



Test Comparisons


- Test Setup

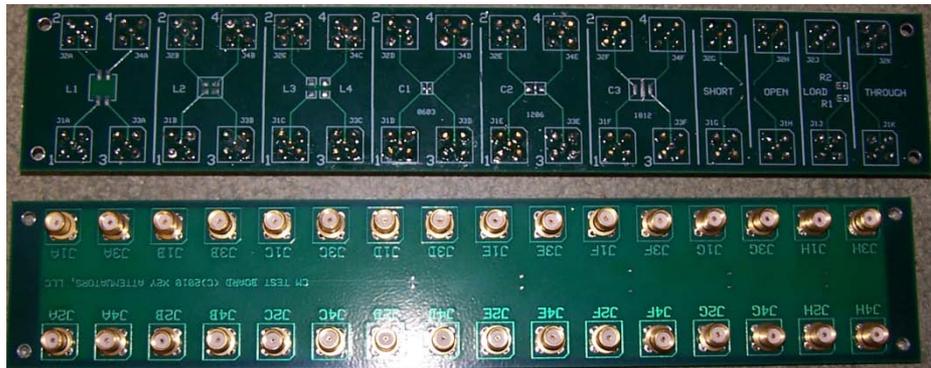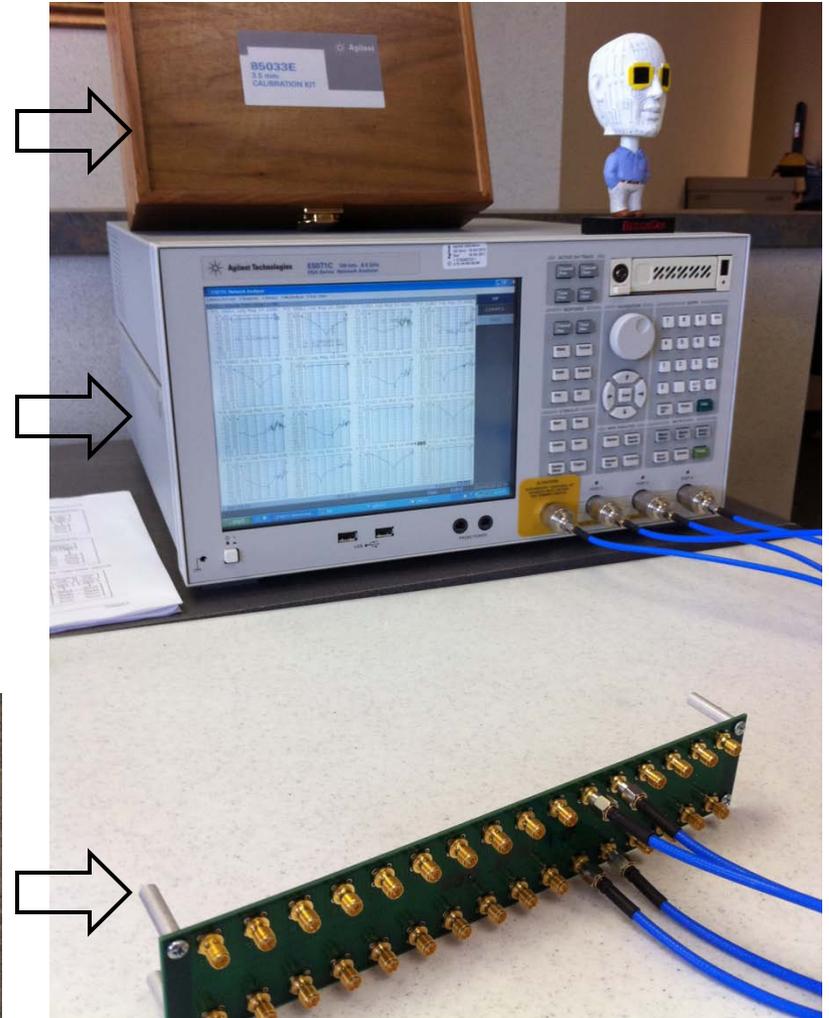- Agilent 85033D 3.5mm Calibration Kit
- Agilent E5071C ENA Network Analyzer
 - 100 kHz - 8.5 GHz
 - Balanced measurements (4-port option)
- DUT test board




Test PCBs

Calibration Positions on PCB

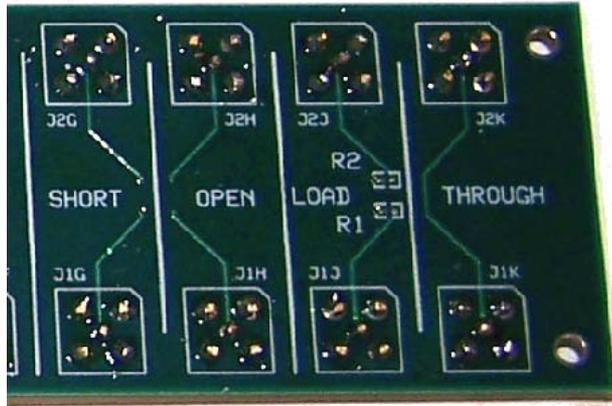


Short/Open/Load/Through (SOLT) calibration is used to de-embed the test fixture effects.

Inductor DUTs

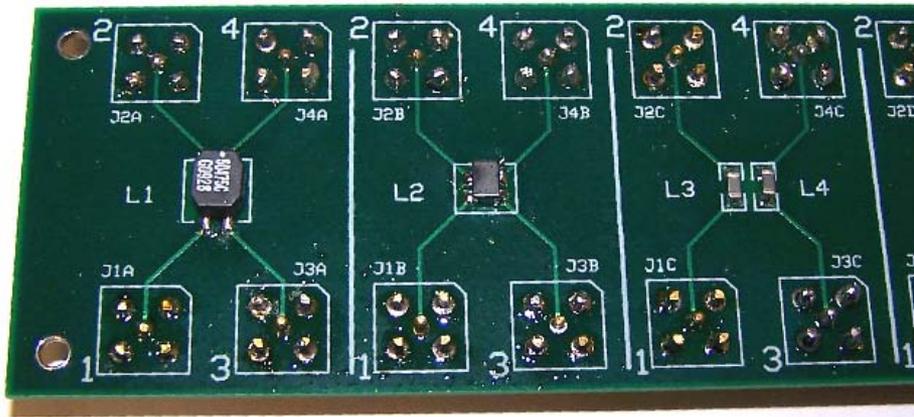


X2Y® Capacitor DUTs

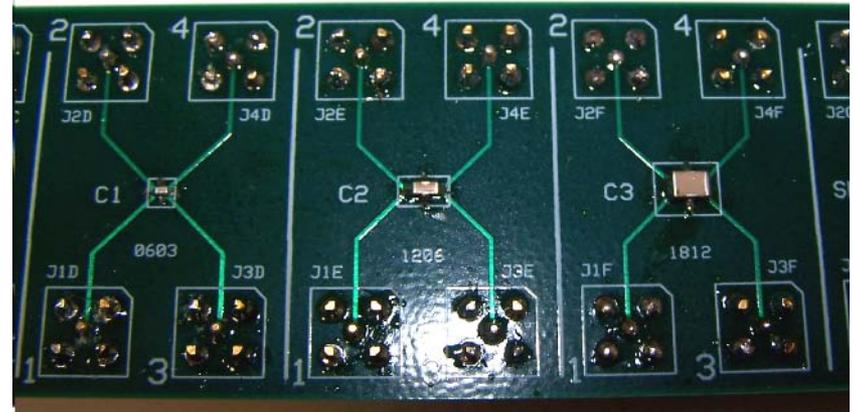



Mixed-Mode Derivations

- Mixed-mode measurements are derived mathematically from full four-port single-ended VNA measurements.
- The Agilent E5071C VNA includes the matrix manipulation software to perform these transformations.
- Of key importance are:
 - SCC21/SCC12 common mode rejection from one side to the other
 - Measures EMI filter effectiveness
 - SDC21/SDC12 common mode to differentiation conversion from one side to the other
 - Measures ESD suppression effectiveness

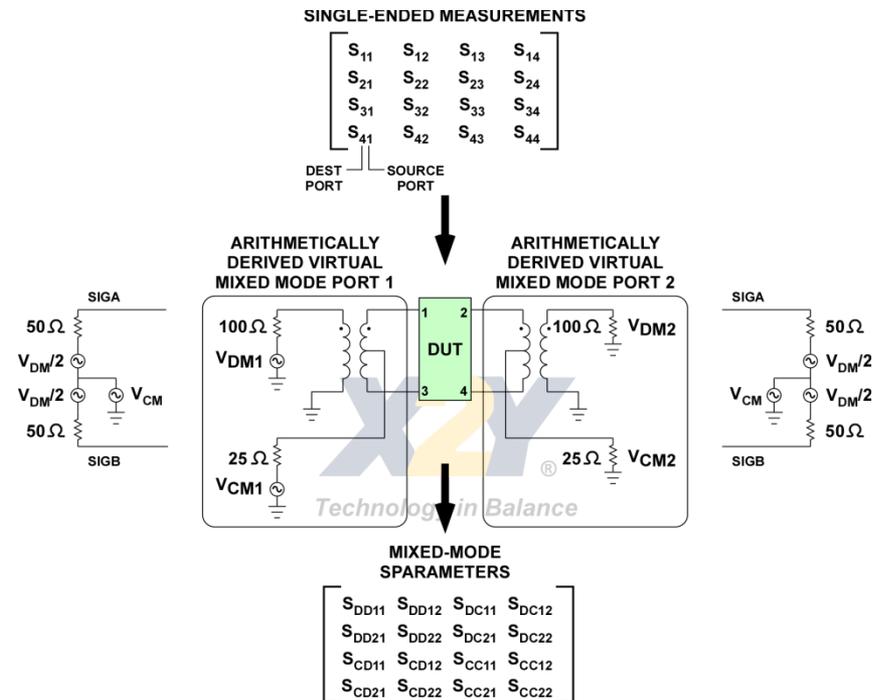


Mixed-Mode Derivations

SINGLE-ENDED MEASUREMENTS

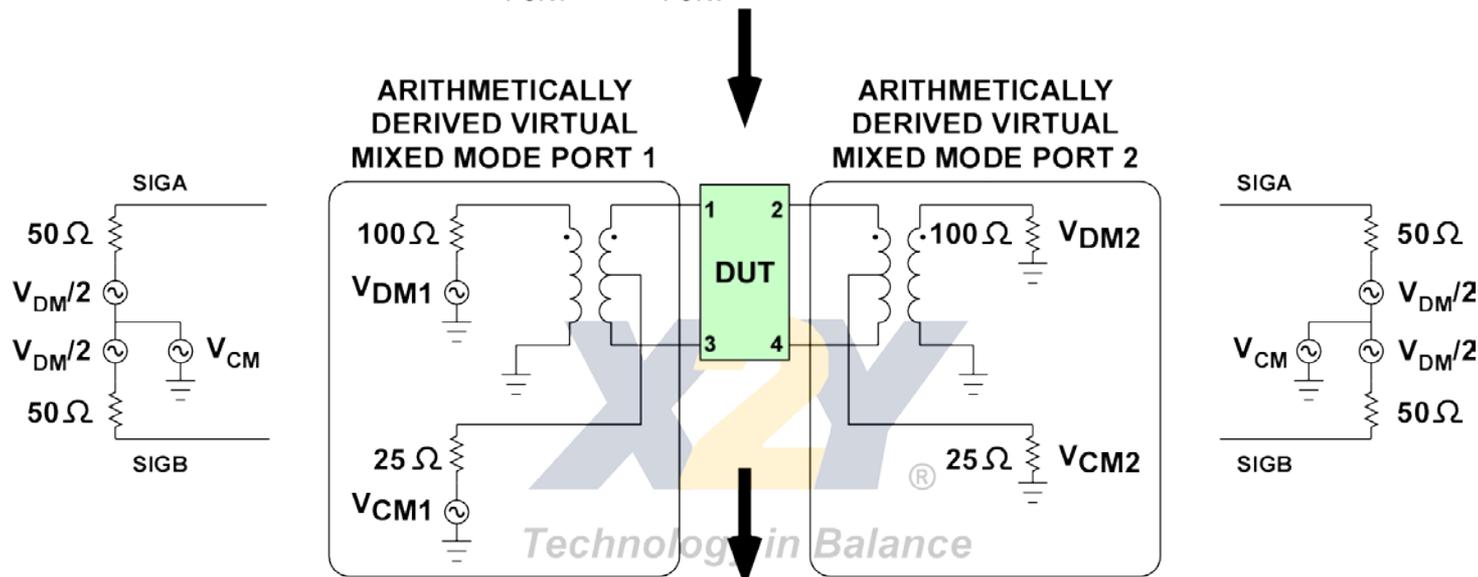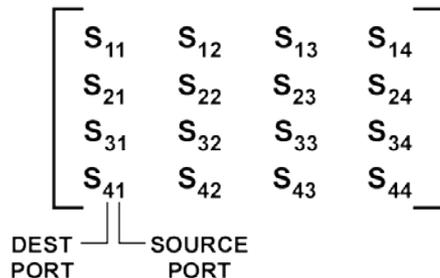


MIXED-MODE SPARAMETERS

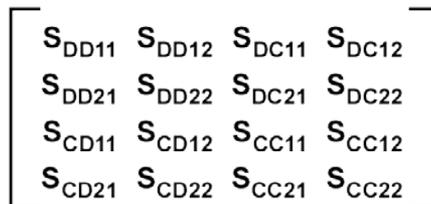

Common Mode Derivation

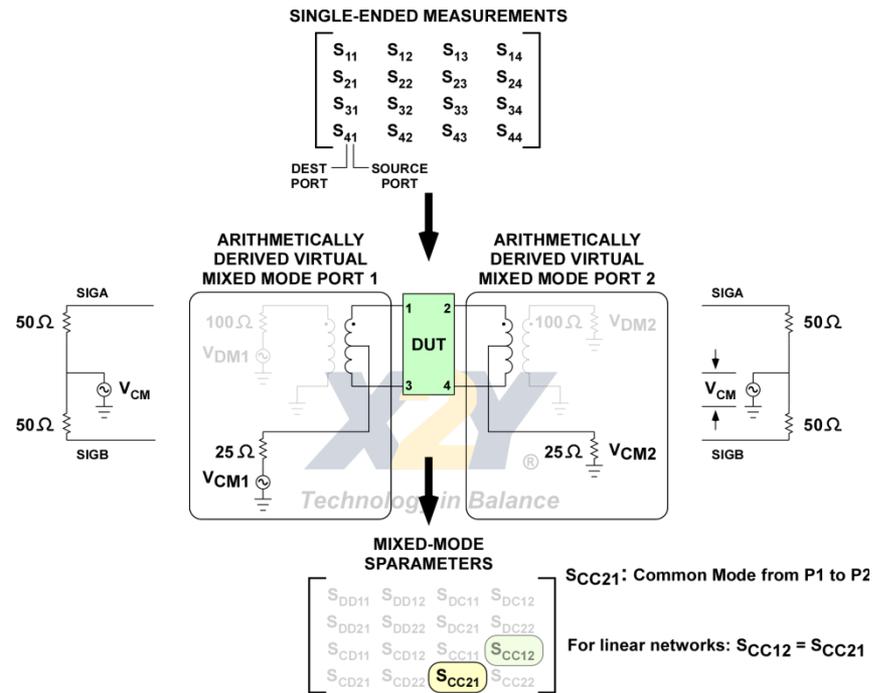- Goal: Determine the amount of common mode energy relative to ground driving Ports 1 and 3 that reaches Ports 2 and 4.
 - Indicates EMI suppression performance
- Both Port 1 and Port 3 drive CM energy in parallel.
 - The two parallel 50Ω ports appear as 25Ω on each side of the filter.
- Operation is symmetric:
 - S_{CC21} matches S_{CC12}




Common Mode Derivation

SINGLE-ENDED MEASUREMENTS

$$\begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

DEST PORT SOURCE PORT

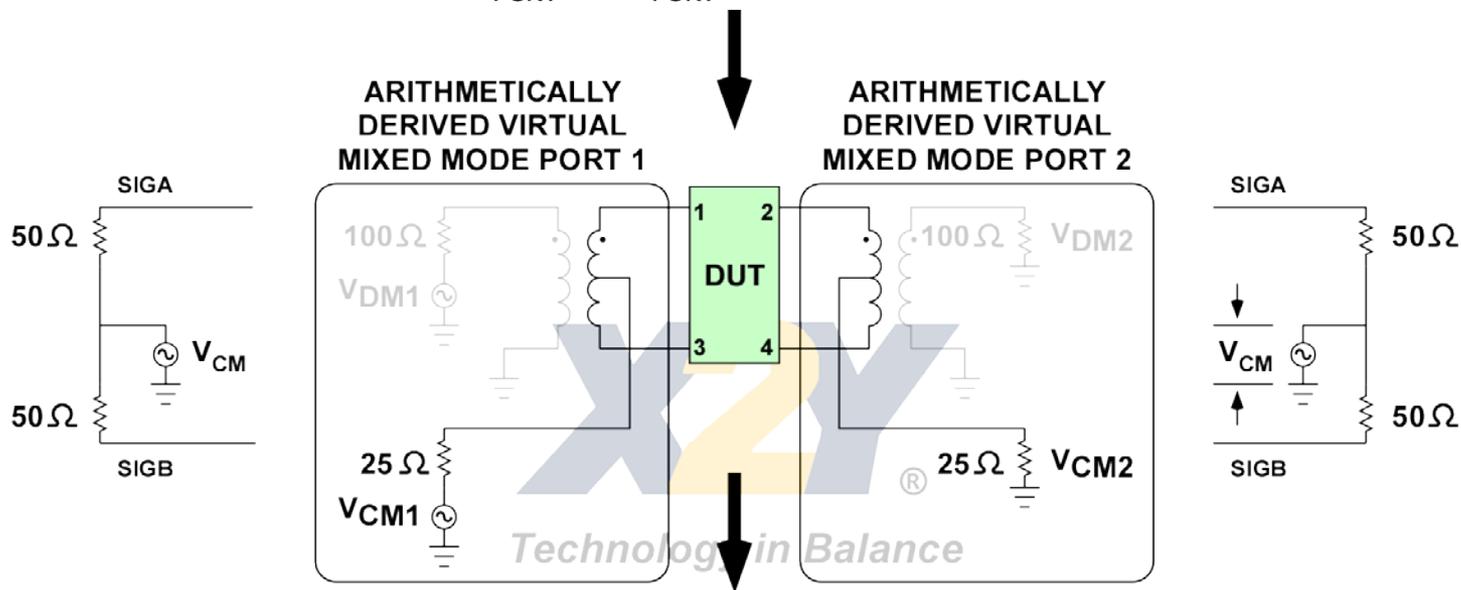

ARITHMETICALLY DERIVED VIRTUAL MIXED MODE PORT 1

ARITHMETICALLY DERIVED VIRTUAL MIXED MODE PORT 2

MIXED-MODE SPARAMETERS


$$\begin{bmatrix} S_{DD11} & S_{DD12} & S_{DC11} & S_{DC12} \\ S_{DD21} & S_{DD22} & S_{DC21} & S_{DC22} \\ S_{CD11} & S_{CD12} & S_{CC11} & S_{CC12} \\ S_{CD21} & S_{CD22} & S_{CC21} & S_{CC22} \end{bmatrix}$$

S_{CC21} : Common Mode from P1 to P2

For linear networks: $S_{CC12} = S_{CC21}$

Common to Diff Mode Conversion Derivation

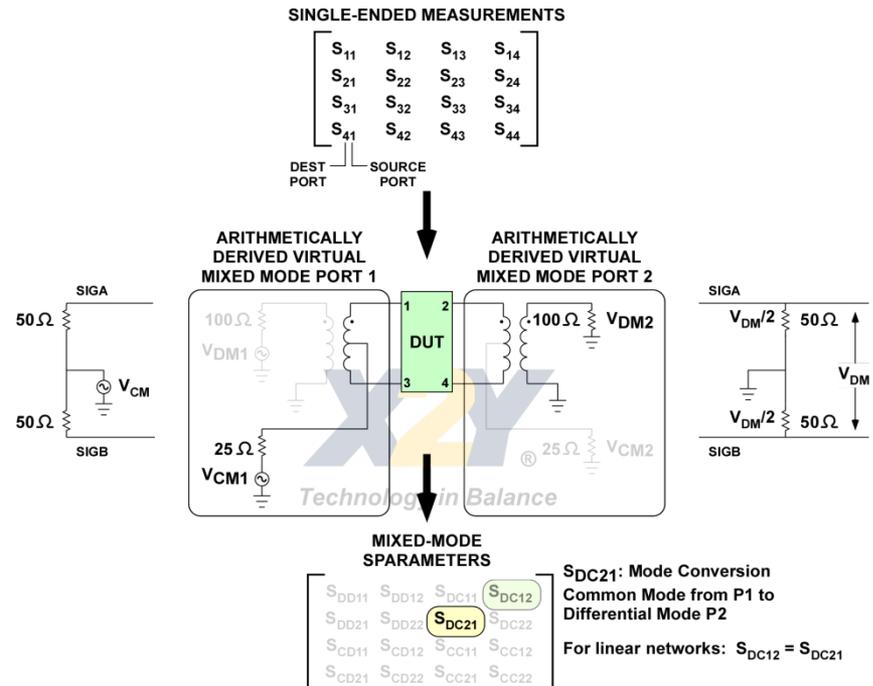- Goal: Determine the amount of common mode noise from the external port that converts to differential energy across the internal ports.
 - Indicates immunity to interference: cell phone, ESD, EFT, etc.
- CM input is two parallel 50Ω sources, 25Ω net.
- DM output appears across series 50Ω loads, 100Ω net.
- Operation is symmetric:
 - S_{DC21} matches S_{DC12}




Common to Diff Mode Conversion Derivation

SINGLE-ENDED MEASUREMENTS

$$\begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

DEST PORT SOURCE PORT

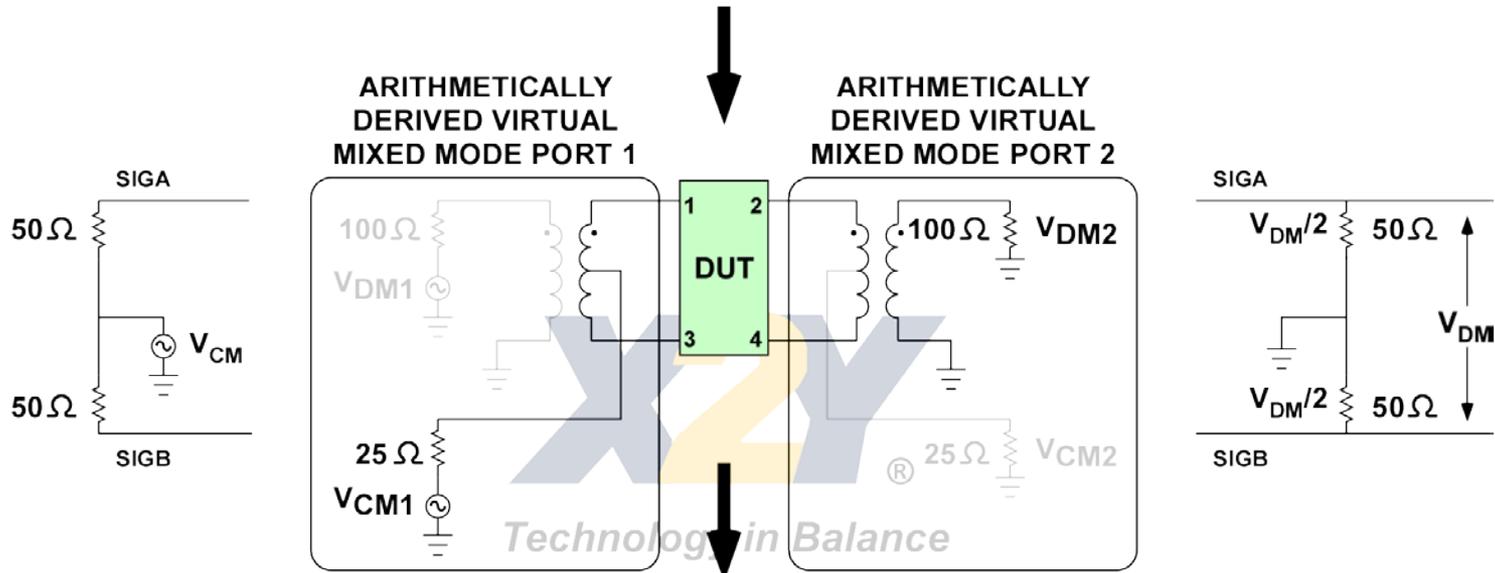


MIXED-MODE SPARAMETERS

$$\begin{bmatrix} S_{DD11} & S_{DD12} & S_{DC11} & S_{DC12} \\ S_{DD21} & S_{DD22} & S_{DC21} & S_{DC22} \\ S_{CD11} & S_{CD12} & S_{CC11} & S_{CC12} \\ S_{CD21} & S_{CD22} & S_{CC21} & S_{CC22} \end{bmatrix}$$

S_{DC21} : Mode Conversion
Common Mode from P1 to
Differential Mode P2


For linear networks: $S_{DC12} = S_{DC21}$

DUTs

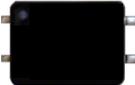DUT	Component Size (mm)	DC Current Rating	Pic
X2Y® 1812	4.4 x 3.2	In bypass, no current limit	
X2Y® 1206	3.2 x 1.6	In bypass, no current limit	
X2Y® 0603	1.6 x 0.8	In bypass, no current limit	
(1) 4000 Ohm Common Mode Choke	5.0 x 3.6	200 mAmps	
(1) 1000 Ohm Common Mode Choke	5.0 x 4.7	1500 mAmps	
(1) 4.7 mH Common Mode Choke A	9.0 x 6.0	400 mAmps	
(1) 4.7mH Common Mode Choke B	9.3 x 5.9	400 mAmps	
(2) 1uH Chip Inductors	(2) 3.2 x 1.6	1200 mAmps	
(2) 120 Ohm Ferrite beads	(2) 3.2 x 1.6	3000 mAmps	
(2) 600 Ohm Ferrite beads	(2) 3.2 x 1.6	3000 mAmps	


Footprint Comparisons

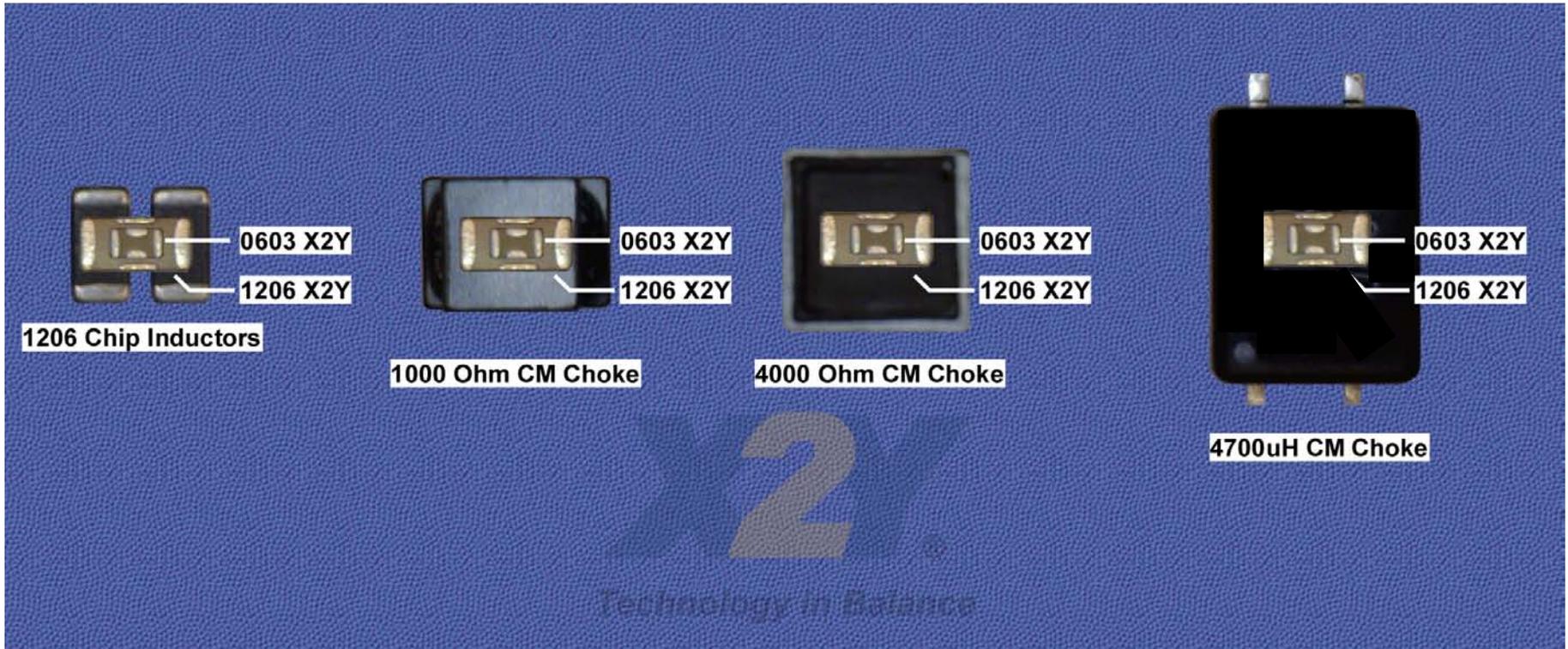X2Y[®] CAPACITORS SUPERIMPOSED OVER MAGNETIC CM FILTERS




Common Mode Rejection Performance

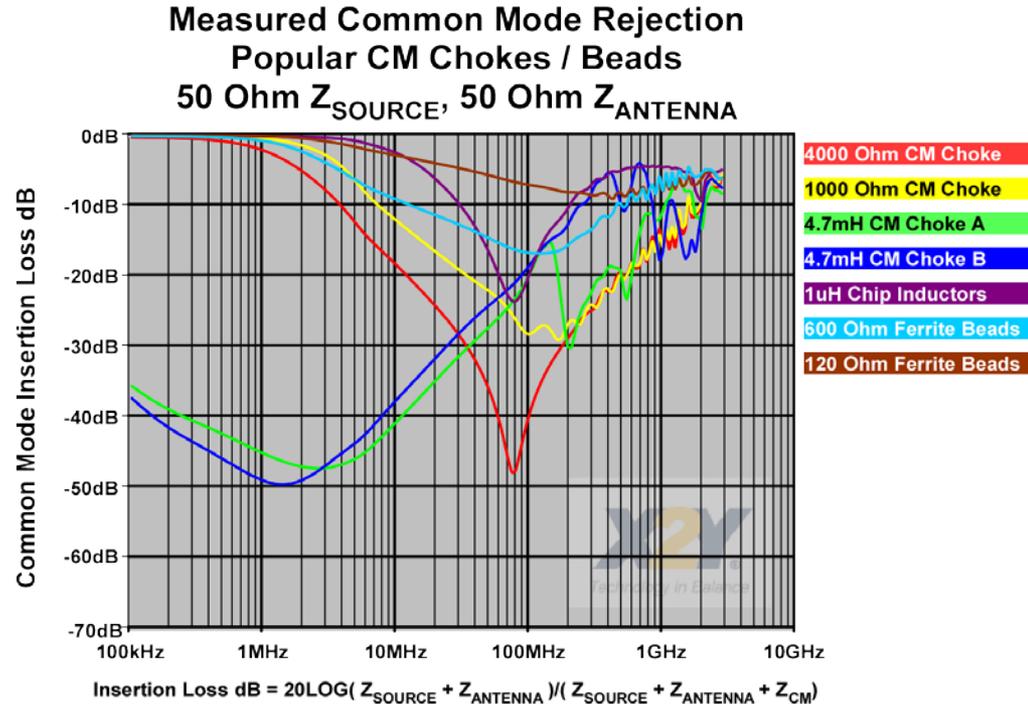- CM Rejection at frequencies $> 100\text{MHz}$ is generally weak with magnetics
 - Interwinding capacitance bypasses series inductance at high frequencies.
 - Ferrite interdomain capacitance bypasses series loss at high frequencies.




Common Mode Rejection Performance

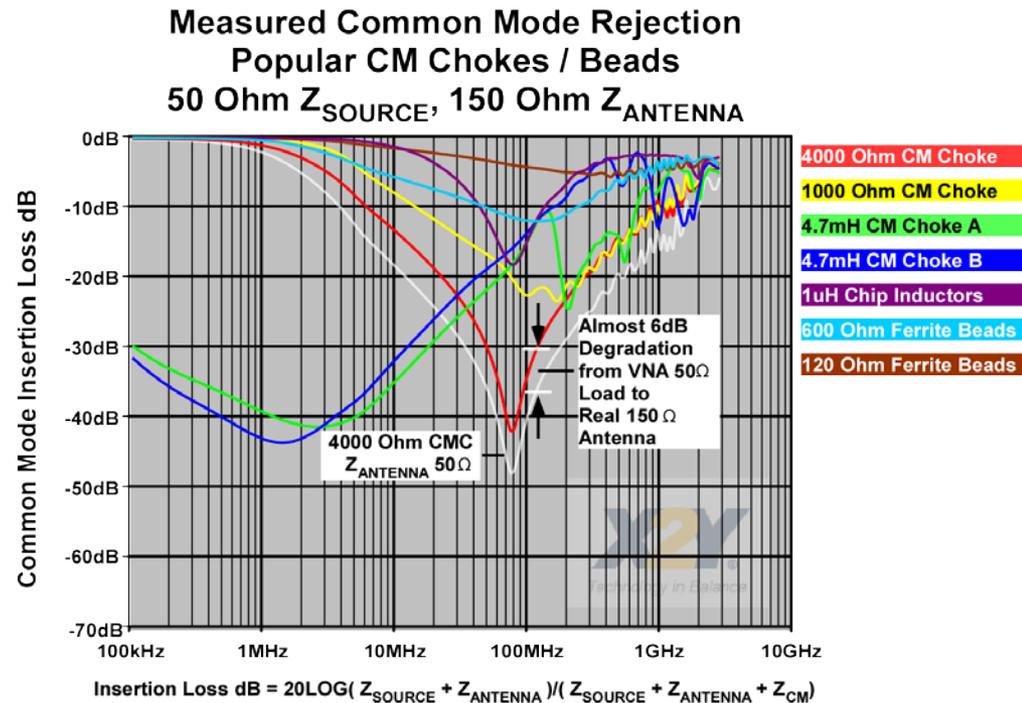- Rejection ratio degrades for real antenna $Z > 50\Omega$
 - 120 – 180 Ohms typical
 - 150 Ω degrades by
 - 6dB at high loss,
 - ≈ 3 dB near 10dB
- Where $Z_{CM} \gg (Z_S + Z_A)$:
 - Loss $\approx 20\text{LOG}(Z_S + Z_A)/(Z_{CM})$
 - Increasing Z_A from 50 to 150 doubles $(Z_S + Z_A)$




Common Mode Rejection Performance

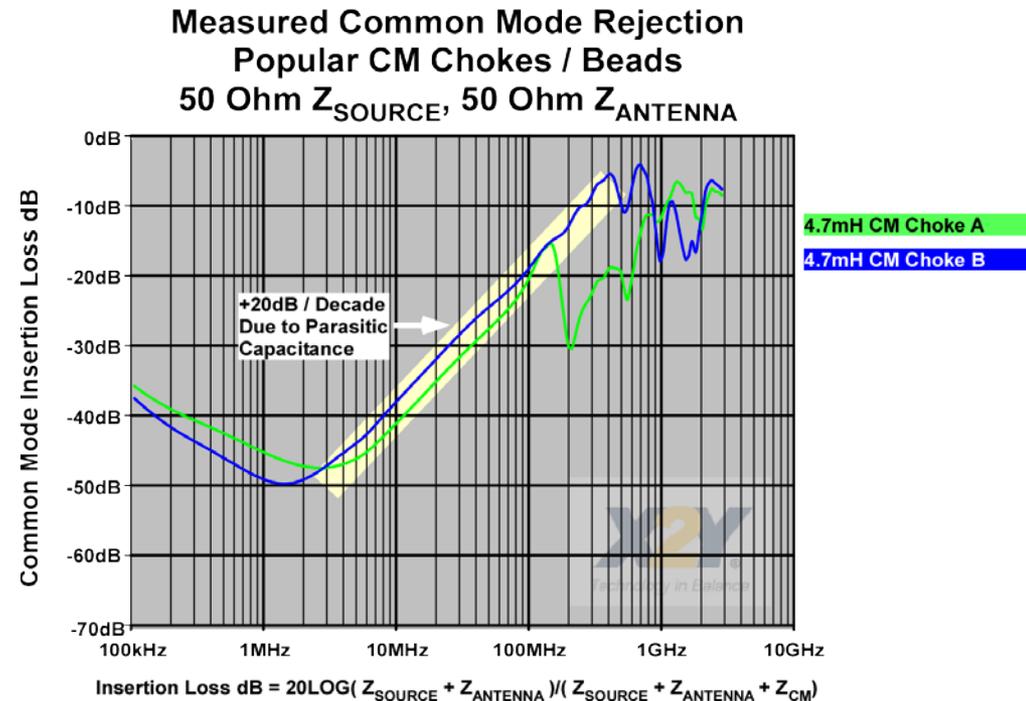- Low frequency chokes:
 - Capable of good insertion loss at modest frequencies.
 - Capacitive parasitics reduce attenuation to 20dB or less @ 100MHz
- Resonances create unstable insertion loss @ high frequencies.
 - Actual insertion loss highly dependent on:
 - Circuit source impedance
 - Cable geometry




Common Mode Rejection Performance

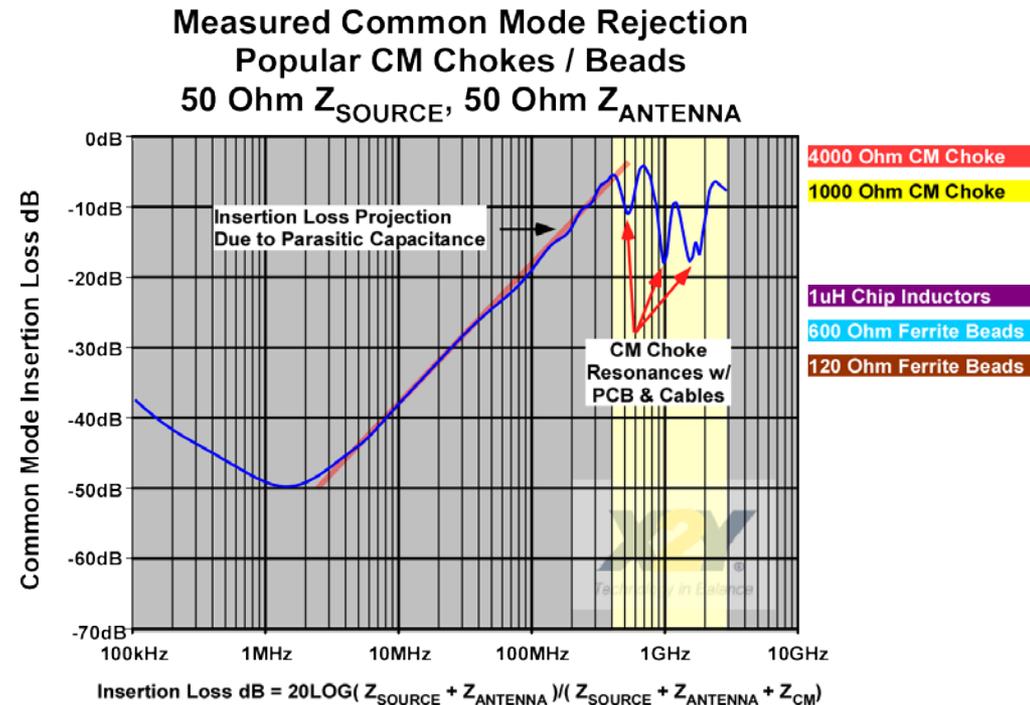- Complex HF resonances
 - High inductance / capacitance chokes exhibit complex interactions with PCB traces, connectors, & cables @ high frequencies.
 - As frequency moves between odd and even $1/4\lambda$ multiples of cable lengths, unterminated cable noise attenuation moves between local minima and maxima.



Common Mode Rejection Performance

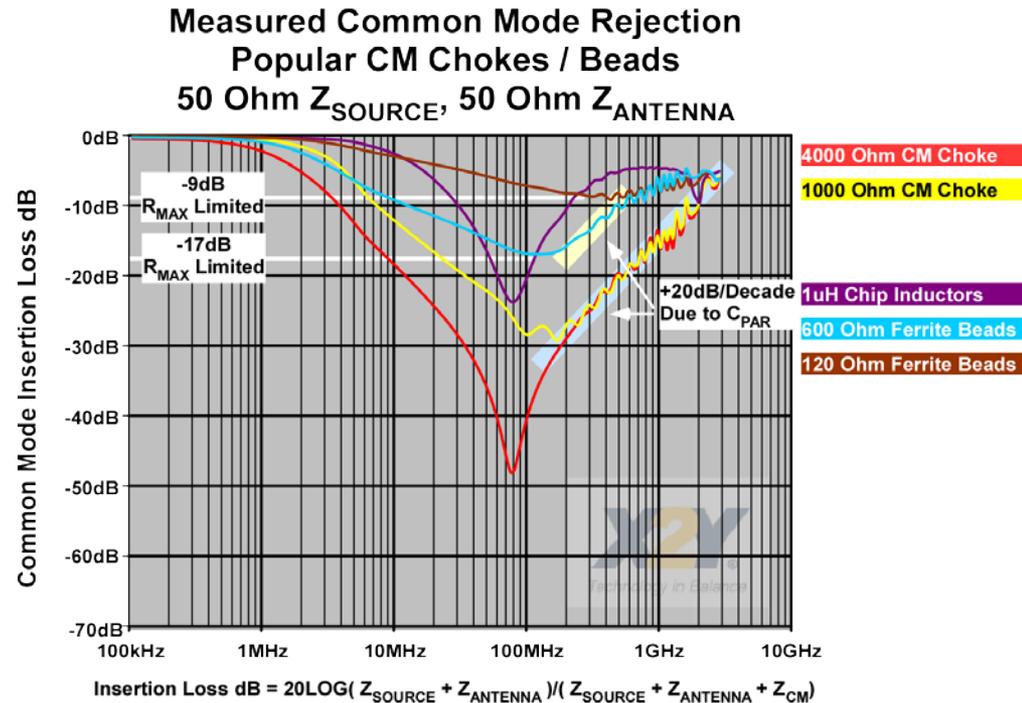
- High frequency chokes / beads
 - Bead insertion loss limited by parasitic resistance and capacitance.
 - 600 Ohm bead limits max. insertion loss to -17dB
 - 1pF limits insertion loss @ 1GHz to -8dB
 - Must include PCB parasitics
 - Nearby etch or parts can destroy HF insertion loss



Common Mode Rejection X2Y[®]

- Consistent high frequency performance independent of capacitance.
 - Mounted inductance controls
 - Linear decrease in noise attenuation w/frequency
 - 0603 parts -24dB or better @ 1GHz into 25 Ohm even mode impedance.
- Capacitor value only affects low frequency attenuation.
 - Larger capacitance values filter lower frequencies

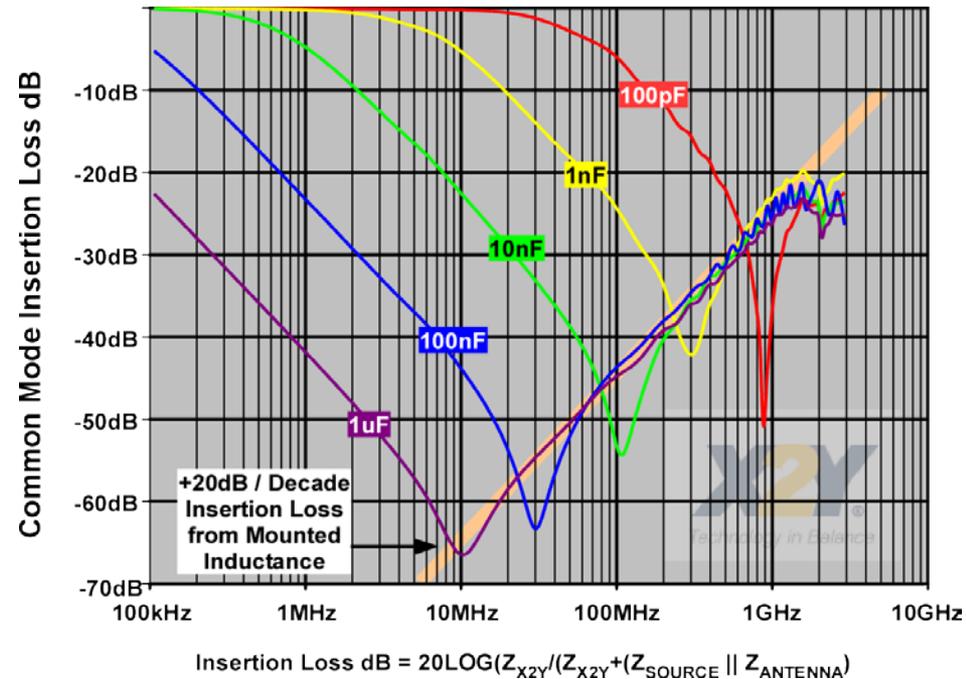
Measured Common Mode Rejection
X2Y[®] 0603 Capacitors
50 Ohm Z_{SOURCE} / 50 Ohm $Z_{ANTENNA}$



Common Mode Rejection X2Y[®]


- Rejection ratio improves for real antenna $Z > 50\Omega$
 - $120\Omega - 180\Omega$ Ohms typical
 - 150Ω improves by
 - 2.5dB at high loss, (>20 dB)
- Where $Z_{X2Y} \ll (Z_S || Z_A)$:
 - $Loss \approx 20\text{LOG}(Z_{X2Y}) / (Z_S || Z_A)$
 - Increasing Z_A from 50Ω VNA port to 150Ω practical antenna value decreases $(Z_S || Z_A)$ by 0.75:1.

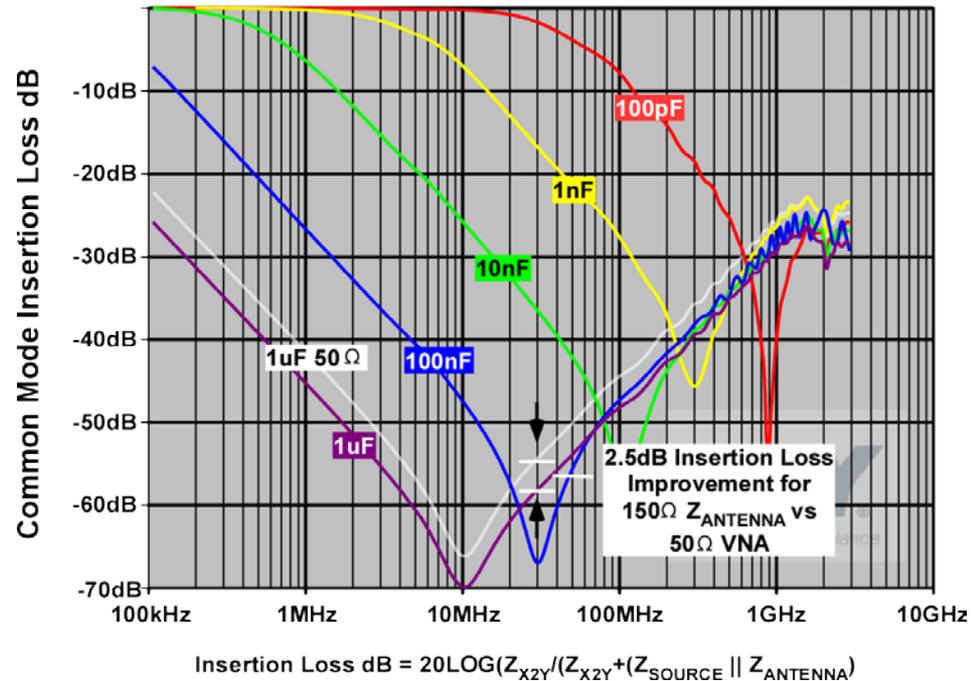Measured Common Mode Rejection
X2Y[®] 0603 Capacitors
50 Ohm Z_{SOURCE} / 150 Ohm $Z_{ANTENNA}$



Common Mode Rejection Comparisons

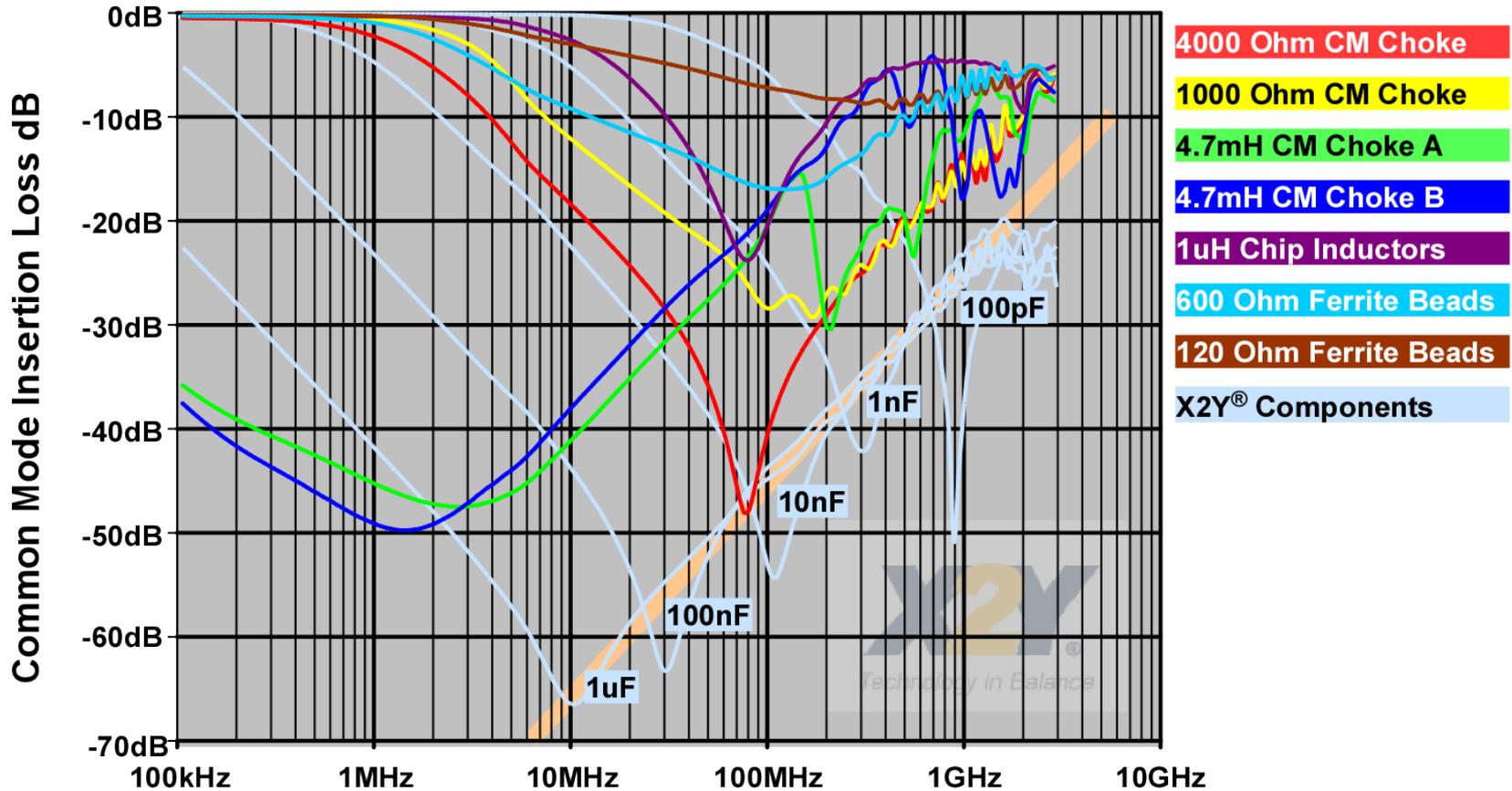Measured Common Mode Rejection
 Popular CM Chokes / Beads
 50 Ohm Z_{SOURCE} , 50 Ohm $Z_{ANTENNA}$




$$\text{Insertion Loss dB} = 20\text{LOG} \left(\frac{Z_{SOURCE} + Z_{ANTENNA}}{Z_{SOURCE} + Z_{ANTENNA} + Z_{CM}} \right)$$

Common Mode Rejection Comparisons

Measured Common Mode Rejection Popular CM Chokes / Beads


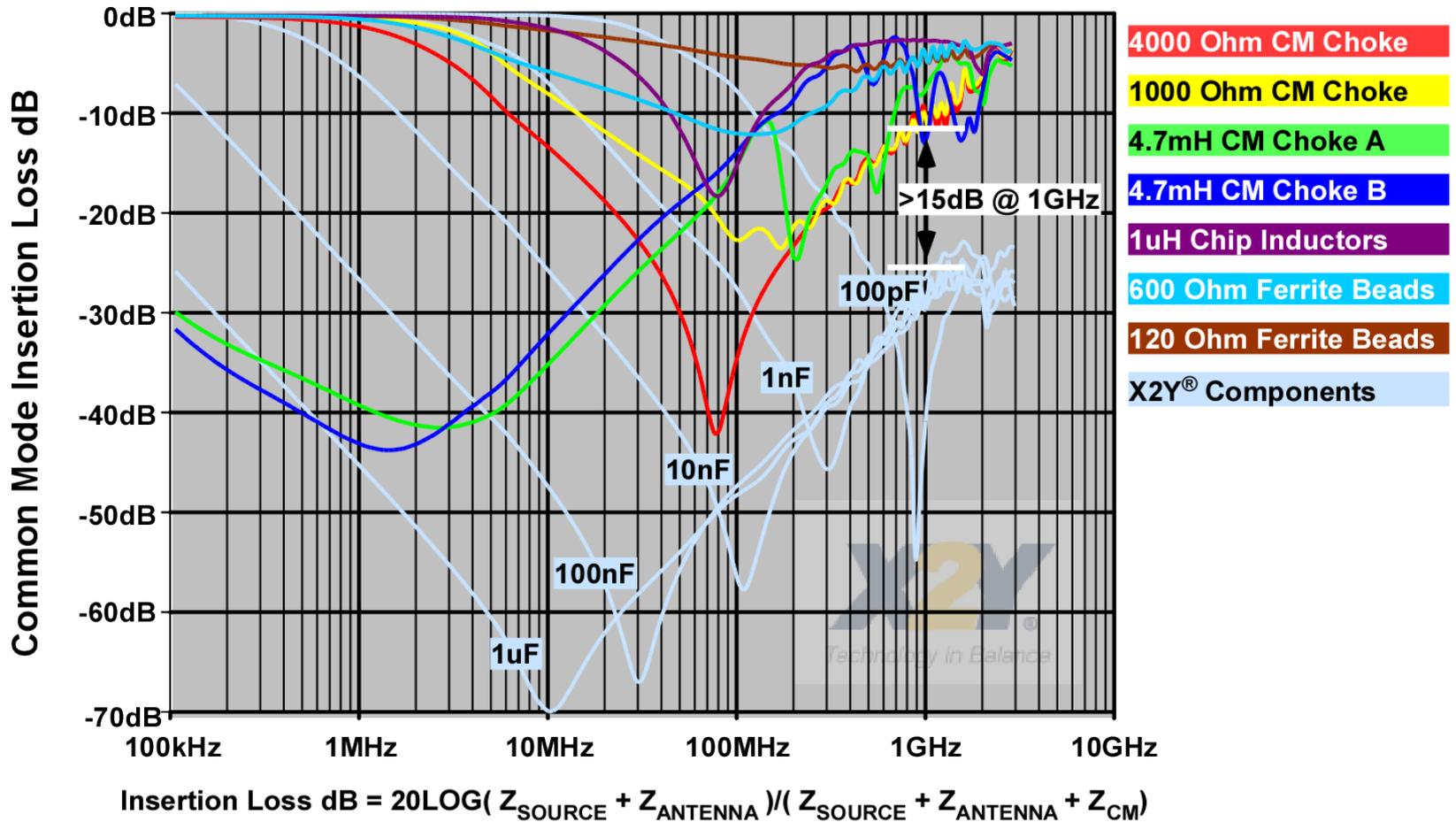
50 Ohm Z_{SOURCE} , 150 Ohm $Z_{ANTENNA}$



Common Mode Rejection Comparisons

Load Antenna Impedance

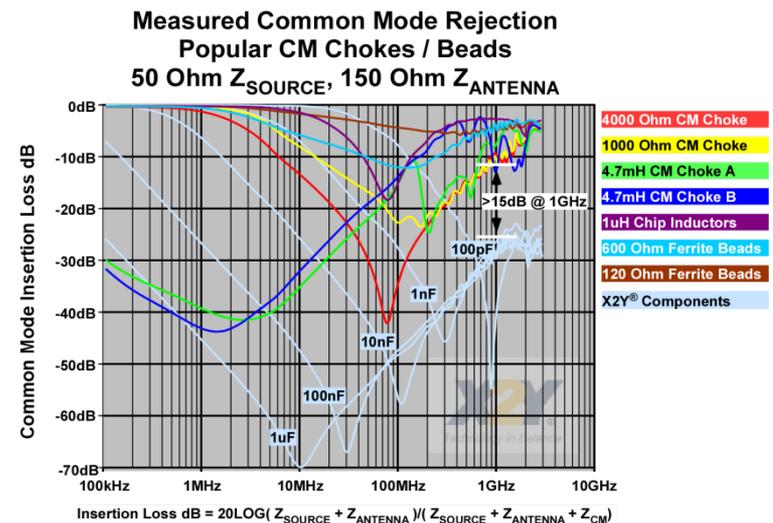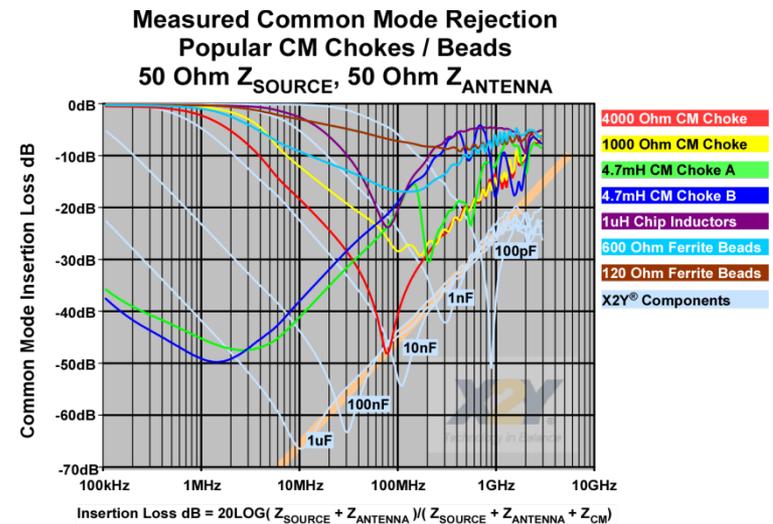
- X2Y[®] capacitors significantly outperform CM chokes using 50Ω VNA ports
- X2Y[®] capacitors exhibit even greater advantage in real applications using typical 150Ω antennae.



Differential to Common Mode Conversion Measurements


- Parasitic capacitive coupling in CM chokes results in significant mode conversion at even modest frequencies.
 - Typical $\approx -35\text{dB}$ @ 350MHz
(F_{KNEE} IEC 61000-2-4)
 - Some devices are much worse
- Results in weak ESD immunity.

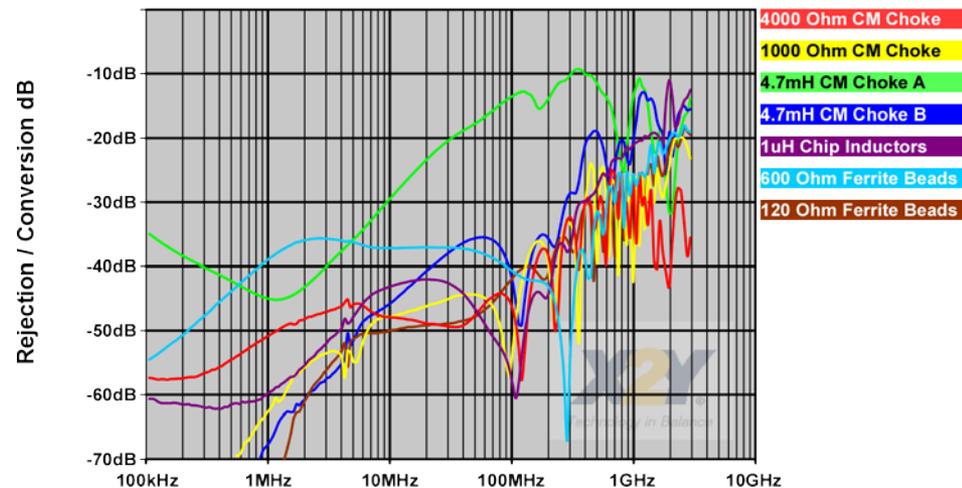Measured CM Rejection and Differential to Common Mode Conversion Popular Chokes, Beads 100 Ohm / 25 Ohm




Differential to Common Mode Conversion Measurements

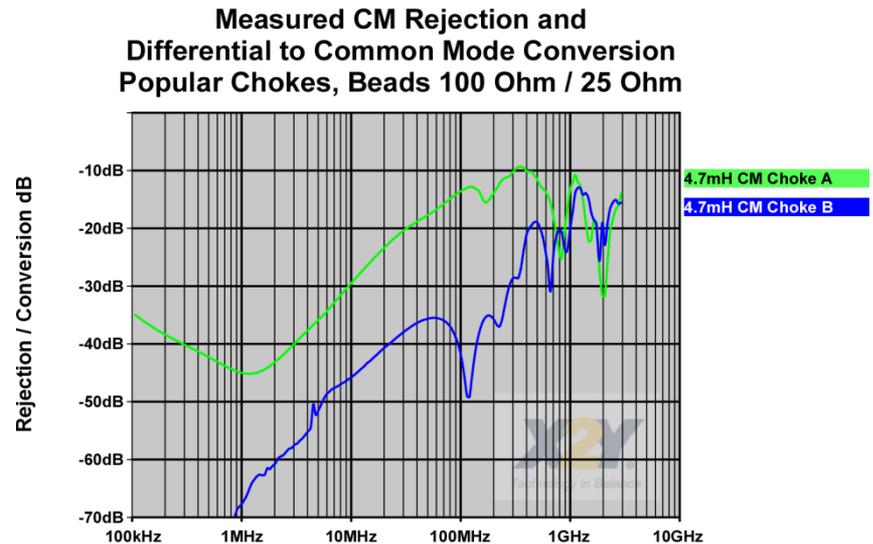- Different chokes with the same datasheet specifications can result in dramatically different mode conversion characteristics.
- LF chokes exhibit particularly poor mode conversion at high frequencies.



Differential to Common Mode Conversion Measurements

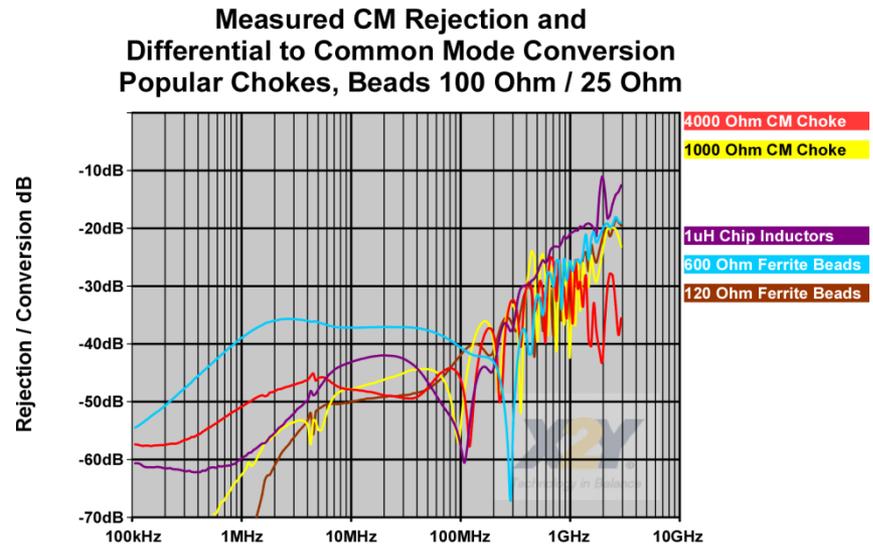
- Ferrite beads and smaller value chokes improve mode conversion, but exhibit poorer common mode rejection



Differential to Common Mode Conversion Measurements


- X2Y[®] capacitors convert a small amount of differential energy to common mode due to finite tolerance mismatches.
- Conversion is -52dB @ 350MHz, -40dB @1GHz
 - 17dB better than typical CM choke / bead solution

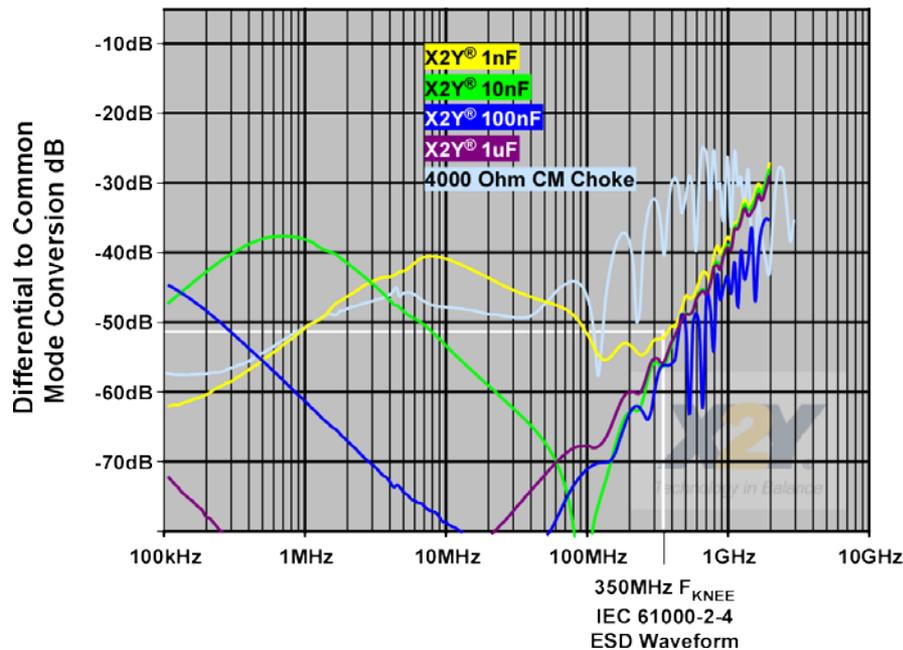Measured Differential to Common Mode Conversion
X2Y[®] 0603 Capacitors



Test Comparisons

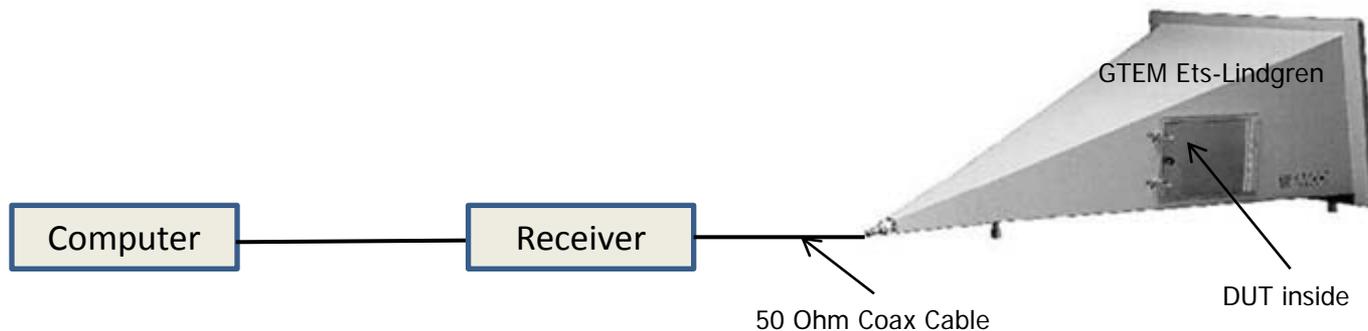
- Example, Single Board Computer Power Feed:
 - 68HC11 processor
- 5uH CM choke tested
- PI filter w/ 5uH CM choke tested
 - 0.1uF cap_5uH CM choke_220nF cap
- Seven values of X2Y[®] capacitors tested
 - 47pF, 100pF, 220pF, 330pF, 470pF, 560pF, 1000pF
- Radiated Emissions Setup:



Comparative Performance Application


- CM Choke and PI filters both exhibit similar performance
 - Filter cut-off $\approx 32\text{MHz}$
 - Attenuation effective to about 450MHz
- Parasitic capacitance completely defeats CM choke and PI filter above 450MHz

HC11 (1MHz – 500MHz, CMC and PI)

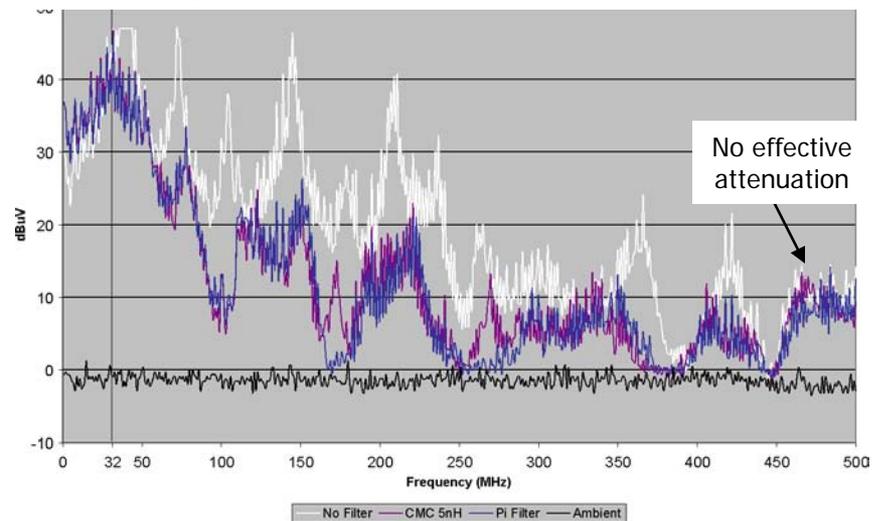

Comparative Performance Application

HC11 (1MHz – 500MHz, CMC and PI)

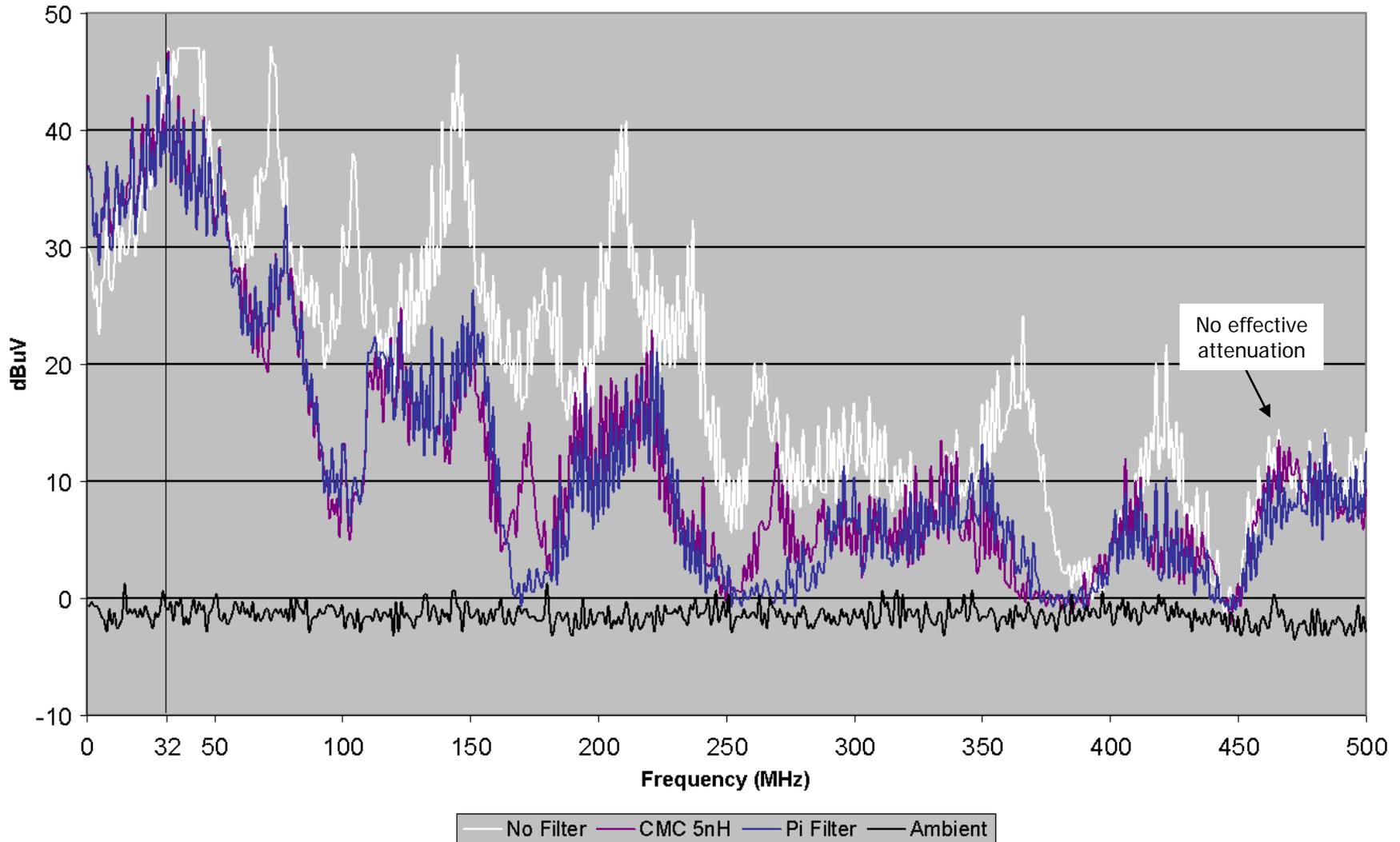


Comparative Performance Application

Slides 37-44, 50MHz –1GHz:

- X2Y[®] capacitors effective to 1GHz and beyond.
- Capacitance value determines low frequency rejection.
- Very small X2Y[®] caps (47pF) superior solution vs. CM chokes or PI filters down to 300MHz.
- 470pF and larger X2Y[®] caps superior over all frequencies.


Comparative Performance Application

HC11 (50MHz –1GHz, 47pF X2Y)

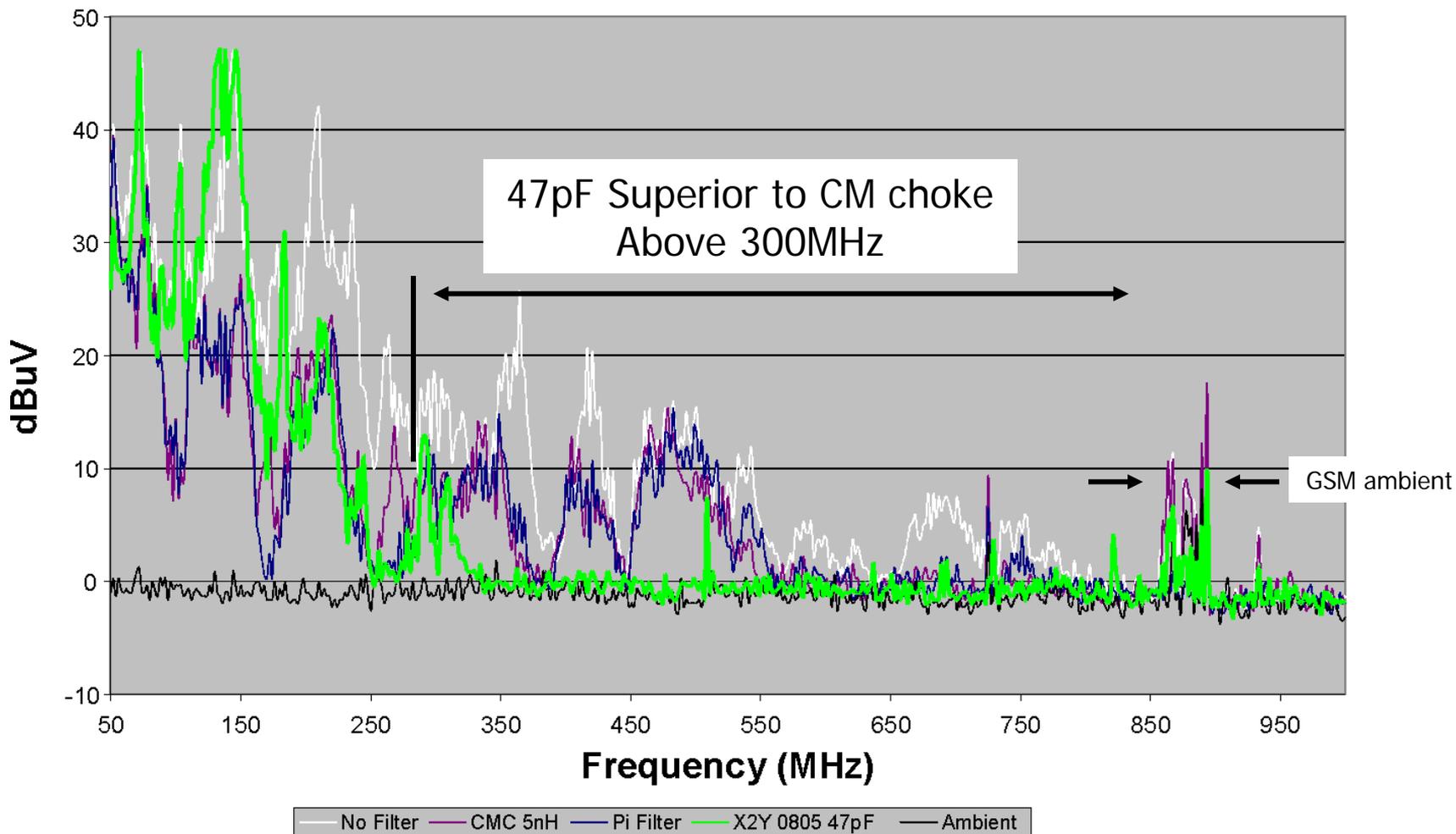


Comparative Performance Application

HC11 (50MHz –1GHz, 100pF X2Y)

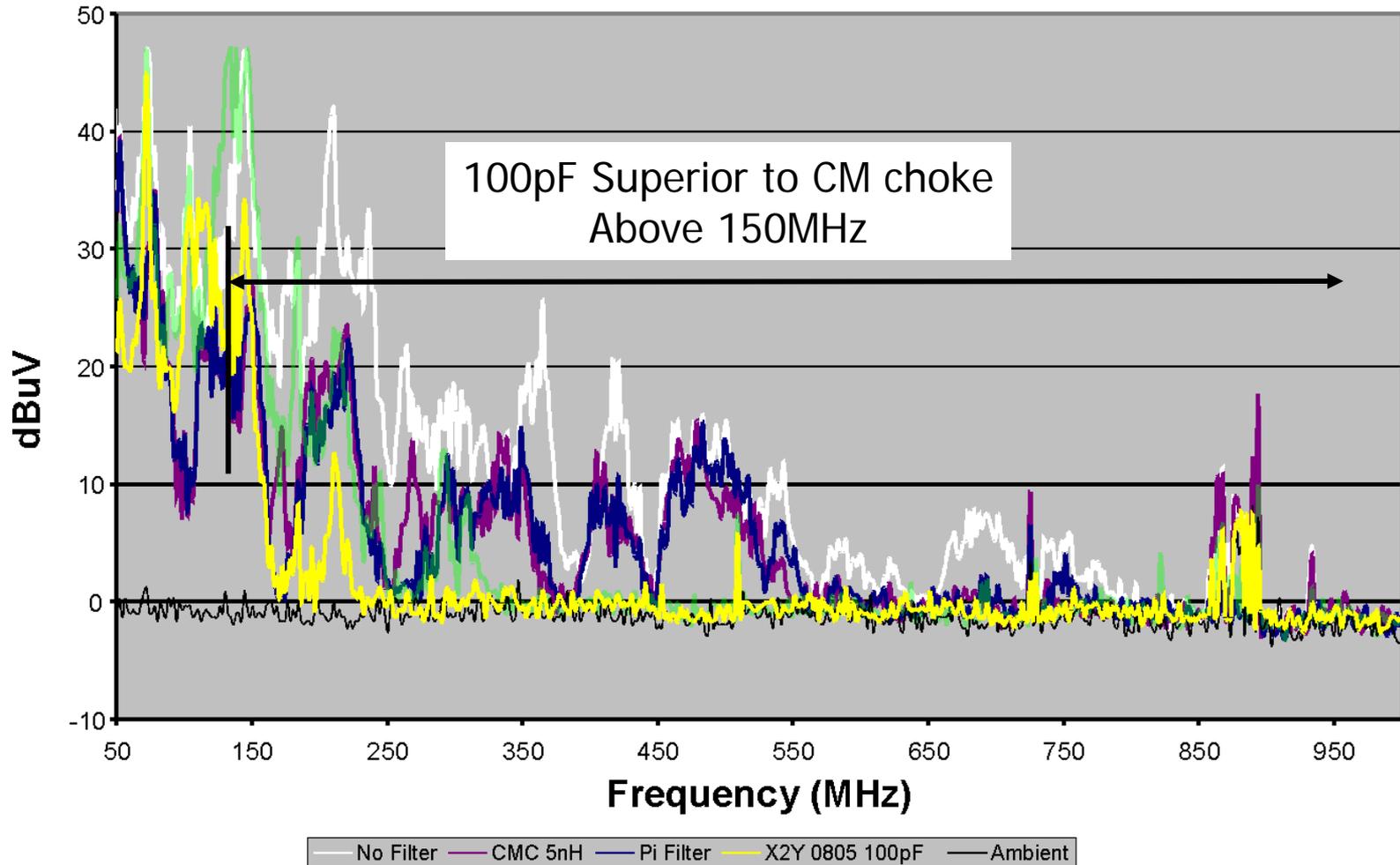


Comparative Performance Application

HC11 (50MHz –1GHz, 220pF X2Y)

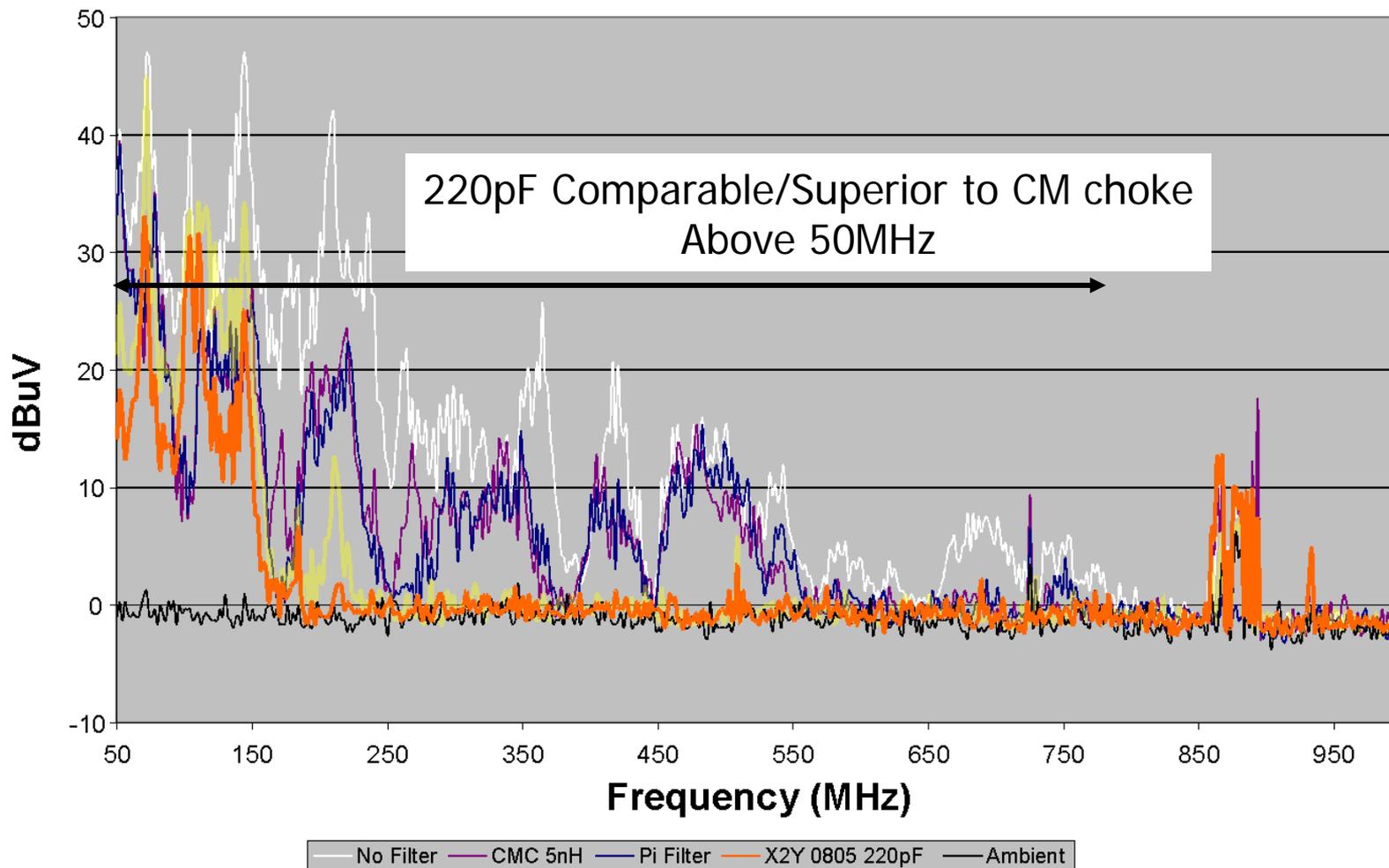


Comparative Performance Application

HC11 (50MHz –1GHz, 330pF X2Y)

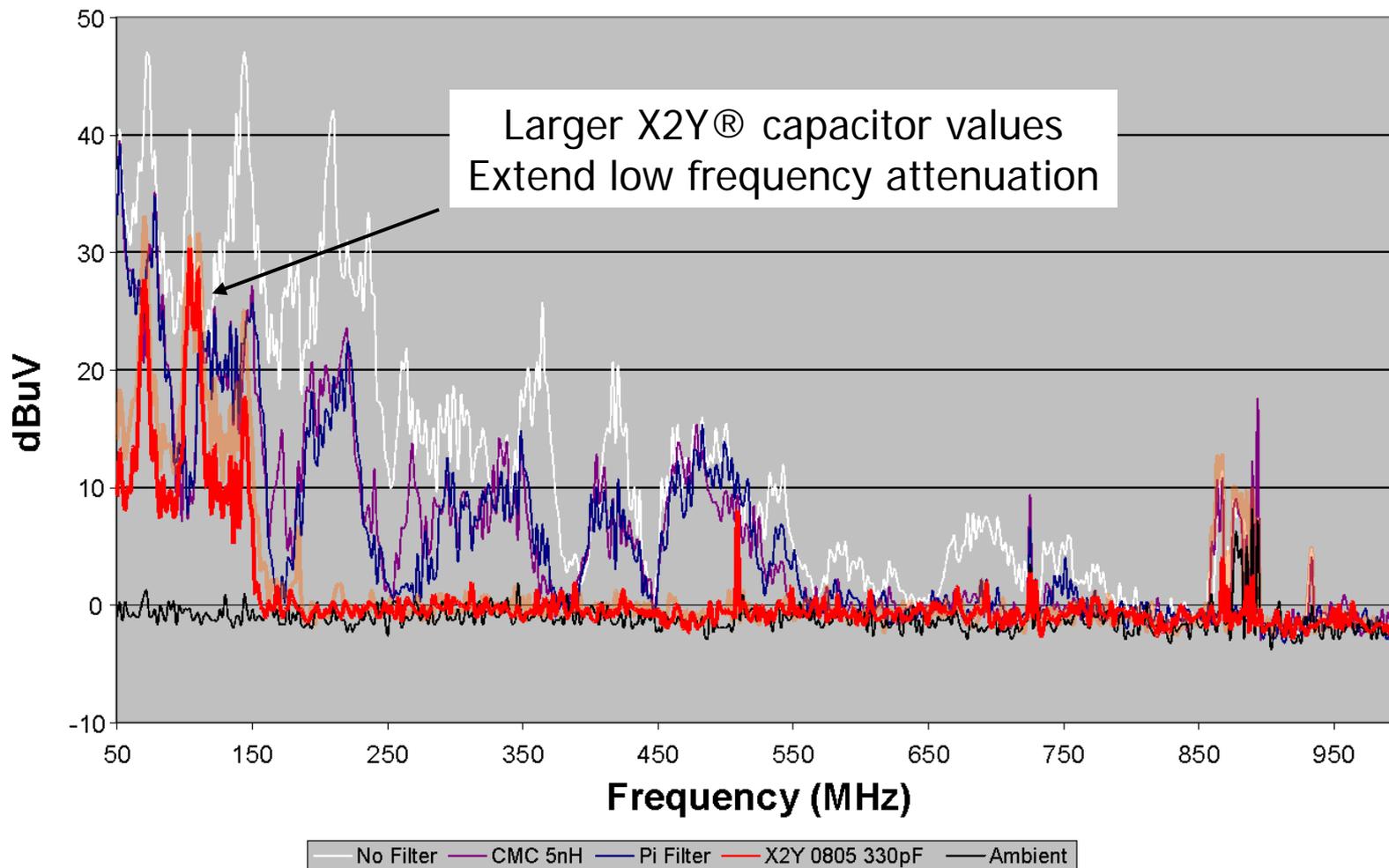


Comparative Performance Application

HC11 (50MHz –1GHz, 470pF X2Y)

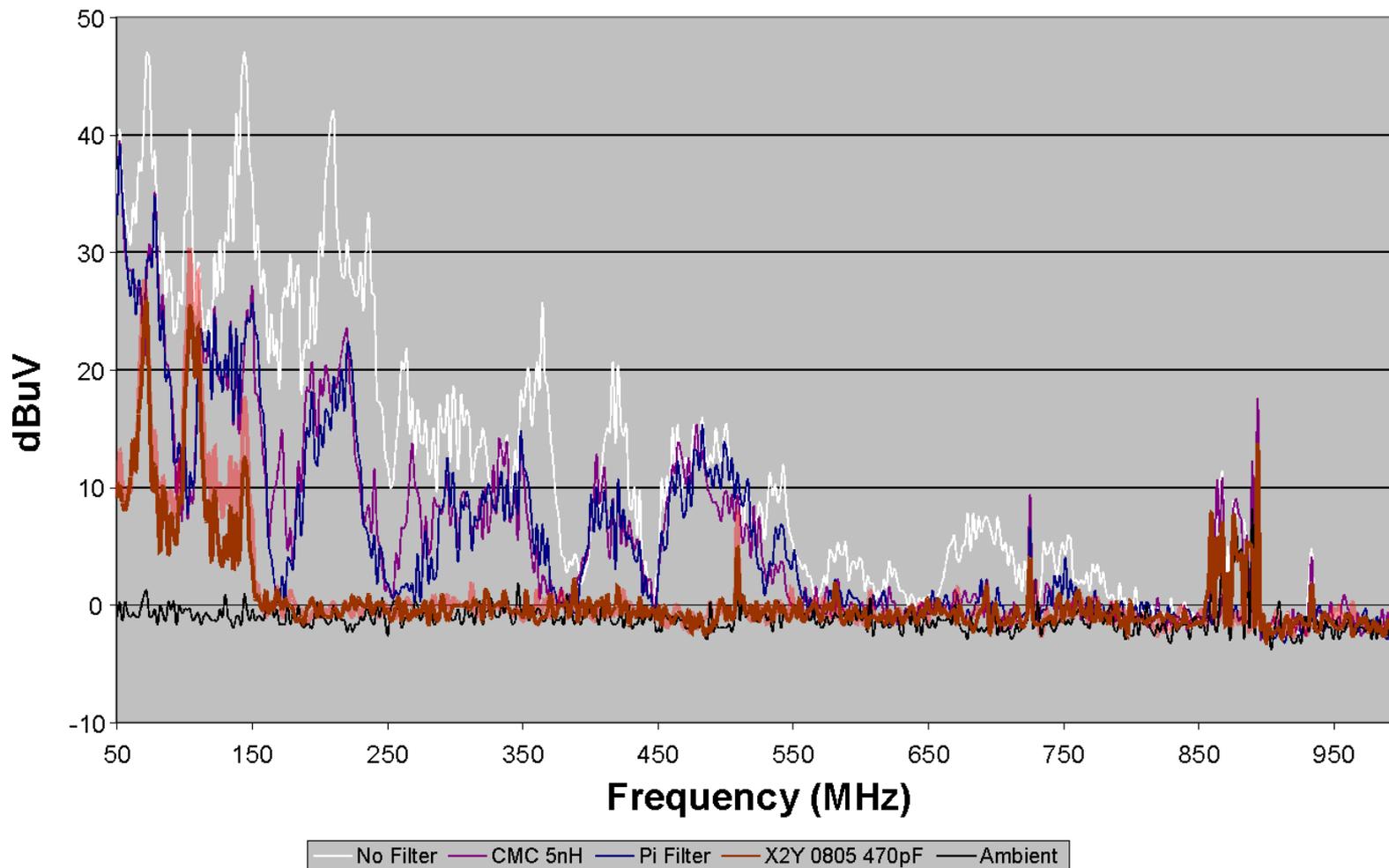


Comparative Performance Application

HC11 (50MHz –1GHz, 560pF X2Y)

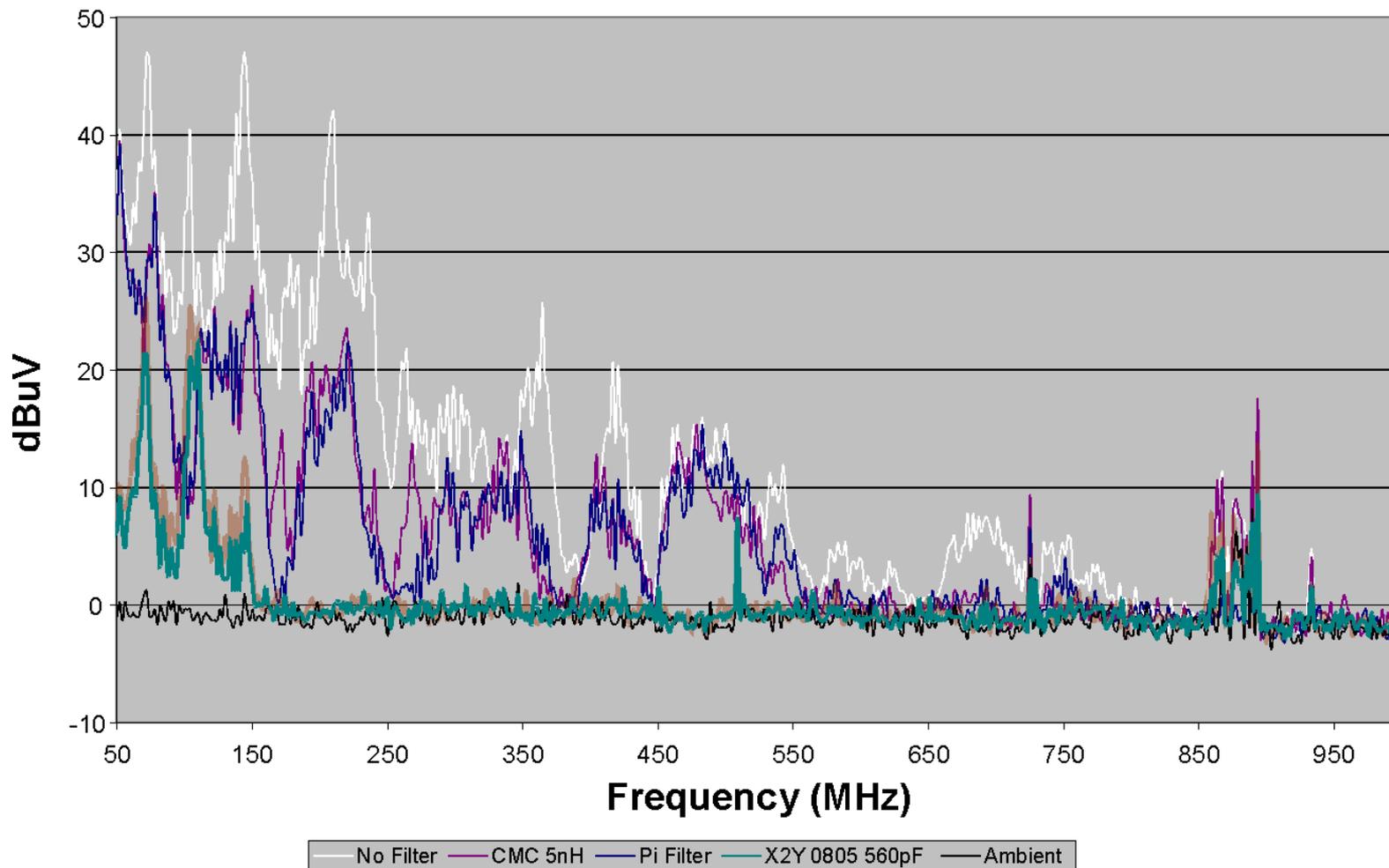


Comparative Performance Application

HC11 (50MHz –1GHz, 1000pF X2Y)

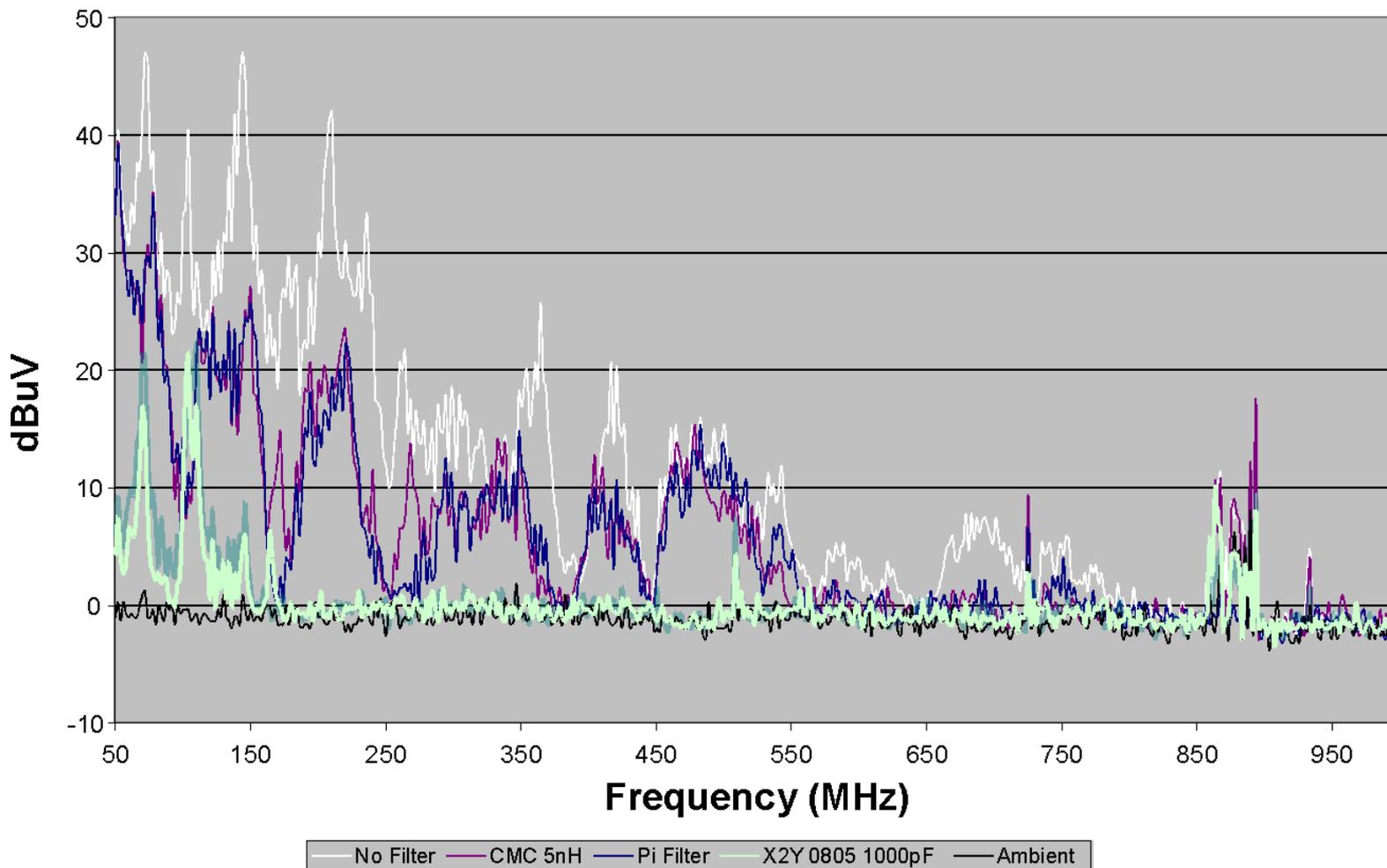


Comparative Performance Application

HC11 (50MHz –1GHz, 1000pF X2Y)

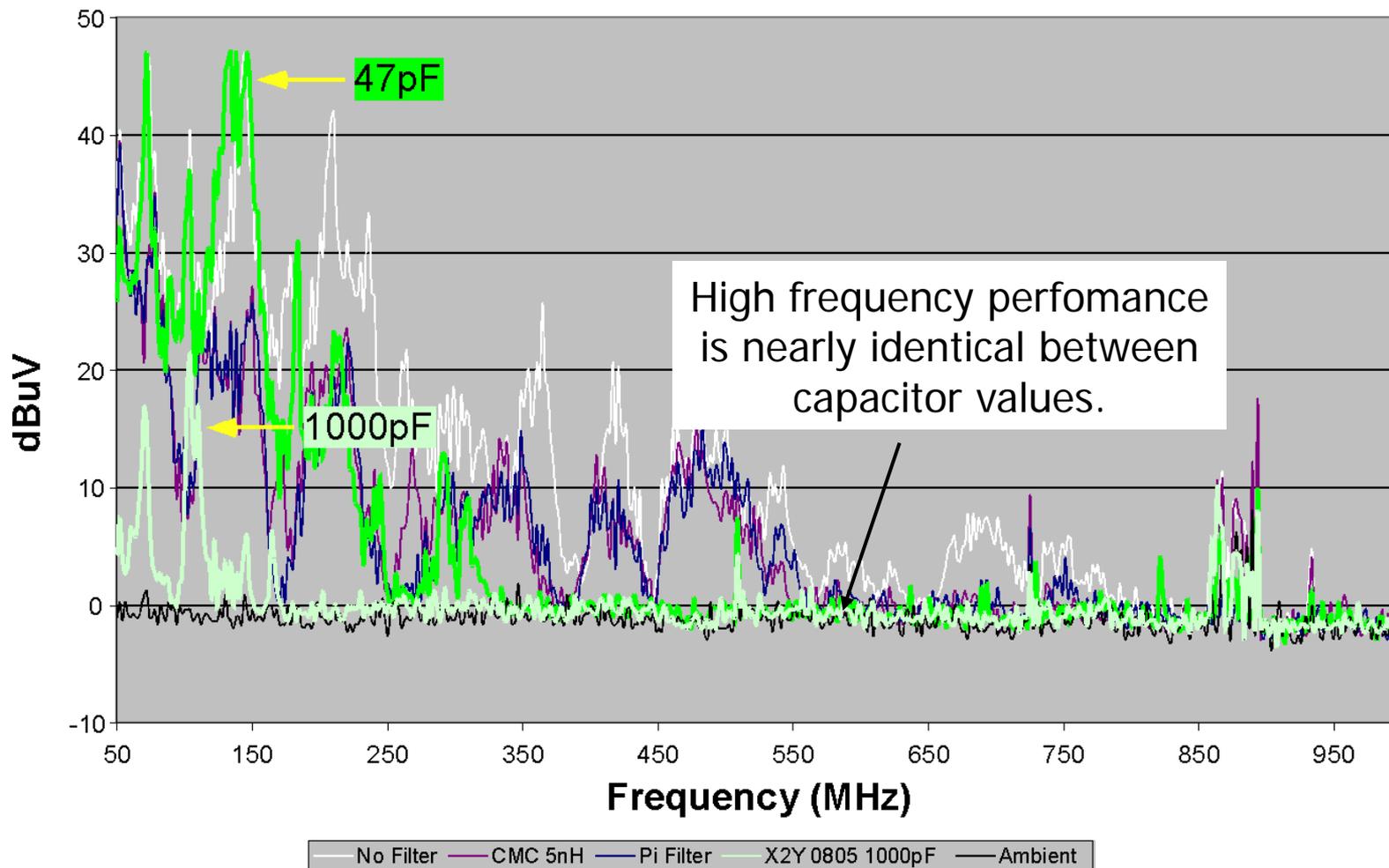



Comparative Performance Application

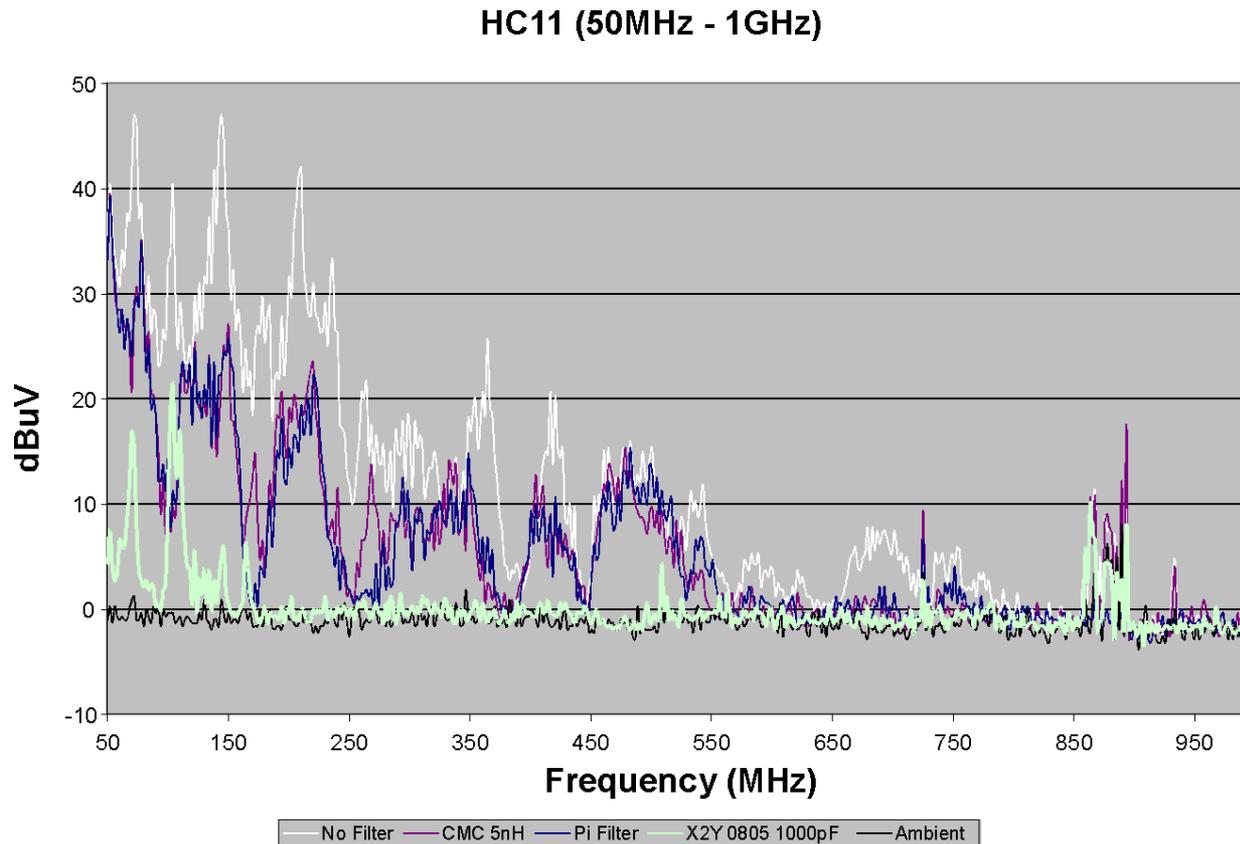- X2Y[®] 1000pF vastly better radiated emissions than 5uH CM choke or PI filter



Comparative Performance Application

CLASS D AUDIO DRIVER CM CHOKE vs X2Y®

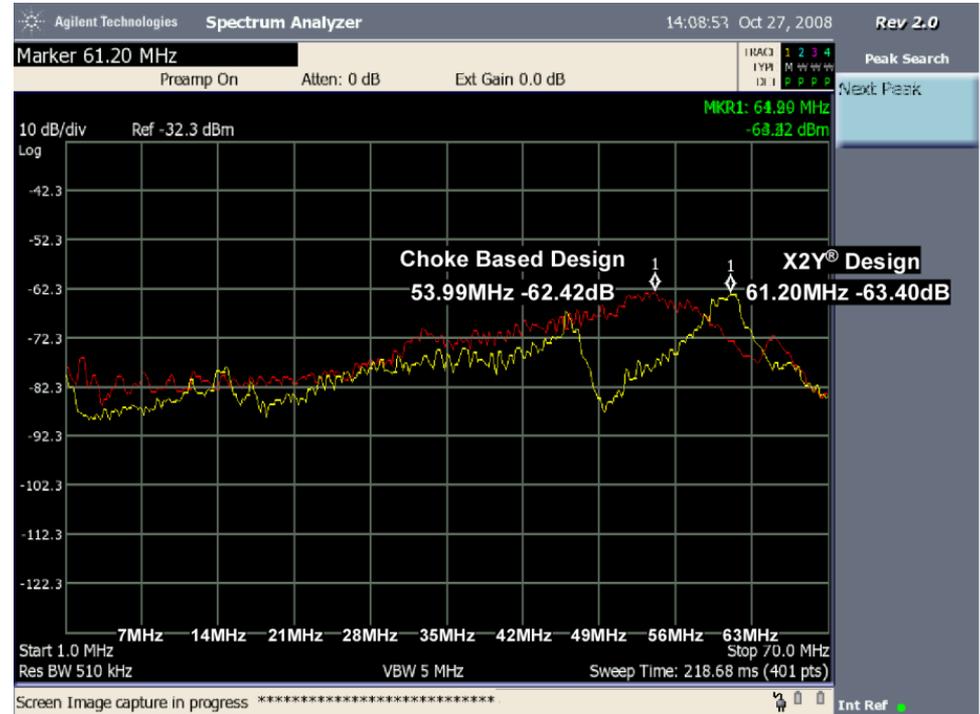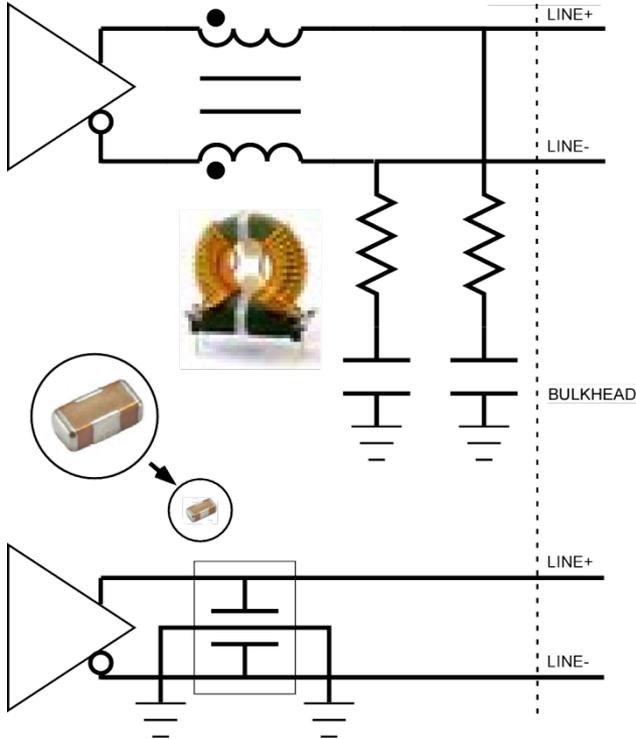

In this design, each X2Y 1206 0.1uF capacitor was used to replace a common mode choke, two resistors and two capacitors to achieve the filter results shown above.

X2Y[®] Capacitor Selection

- X2Y[®] capacitors operate as shunts.
 - Attenuate all energy above cut-off frequency
 - Select to pass required signal energy / block offensive HF noise.
 - Use capacitance value that is large enough to attenuate effectively to lowest noise frequency, but no larger than necessary.
- Four recommended selection methods:
 - 1. Pass a required signal rise / fall time.
 - 2. Pass a required signal rise / fall time as a bit interval %.
 - 3. Cut-off HF noise at a specific frequency.
 - 4. Substitute for a specific CM choke.

X2Y[®] Capacitor Selection Method 1.

- Use Acceptable Signal Rise and Fall Times
- Establish $T_{\text{RISE}} / T_{\text{FALL}}$
 - $C \leq T_{\text{RISE}_{10\%_{90\%}}_{\text{MIN}}} / (2.2 * Z_{\text{SOURCE}})$
- Example: CAN BUS 1Mbps, 120 Ohm
 - $T_{\text{RISE}_{10\%_{90\%}}} \leq 50\text{ns}$
 - $Z_{\text{SOURCE}} = 120 \text{ Ohms} / 2$ (Loosely coupled diff pair) = 60 Ohms
 - $C_{\text{MAX}} \leq 50\text{ns} / (2.2 * 60 \text{ Ohms})$
 - $C_{\text{MAX}} \leq 380\text{pF}$
 - Recommended value = 330pF
 - $T_{\text{RISE}_{10\%_{90\%}}} \leq 44\text{ns}$

X2Y[®] Capacitor Selection Method 2.

- Pass Signal Rise and Fall Times Based on Signal Bit Rate and % Allowable T_R / T_F
- $T_{RISE_10\%_90\%} / T_{FALL_90\%_10\%} < 5-10\%$ of bit period is usually OK
 - 5%
 - $C \leq 1/(44 * \text{Bit_Frequency} * Z_{SOURCE})$
 - CAN BUS
 - $C \leq 1/(44 * 1\text{MHz} * 60 \text{ Ohms}) \leq 380\text{pF}$
 - 10%
 - $C \leq 1/(22 * \text{Freq} * Z_{SOURCE})$

X2Y[®] Capacitor Selection Method 3.


- Cut Noise Down to a Specific Low Frequency
- Noise cut-off frequency F_{CO} is known, source impedance Z_{SOURCE} and antenna impedance $Z_{ANTENNA}$.
 - $C \Rightarrow 1/(2\pi * F_{CO} * (Z_{SOURCE} || Z_{ANTENNA}))$
- Example: Switching power supply harmonic suppression
 - $F_{CO} = 200\text{kHz}$
 - $Z_{SOURCE} = \text{transmission line impedance } 10 \text{ Ohm}$
 - $Z_{ANTENNA} = 150 \text{ Ohm}$
 - $C_{MIN} \geq 1/(2\pi * 200\text{kHz} * 10 || 150 \text{ Ohm}) = 1/1.26\text{E}7 = 80\text{nF}$
 - Recommended minimum value = 100nF
- Use larger capacitances for lower frequencies and/or lower impedances.

X2Y[®] Capacitor Selection Method 4.

- Substitute for known CM Choke at a known source and antenna impedance:
 - Match choke low frequency insertion loss:
 - $C_{X2Y} \geq L_{CM} / (Z_{SOURCE} * Z_{ANTENNA})$
 - L_{CM} is the coupled inductance.
 - Typically $\approx 2X$ Inductance measured with second winding open
 - If Z_{SOURCE} and/or $Z_{ANTENNA}$ are not known:
 - Assume 50 Ohms for Z_{SOURCE}
 - Assume 100 Ohms for $Z_{ANTENNA}$
 - Yields a conservative result that will perform equal or better in a real application

X2Y[®] Capacitor Selection Method 4.

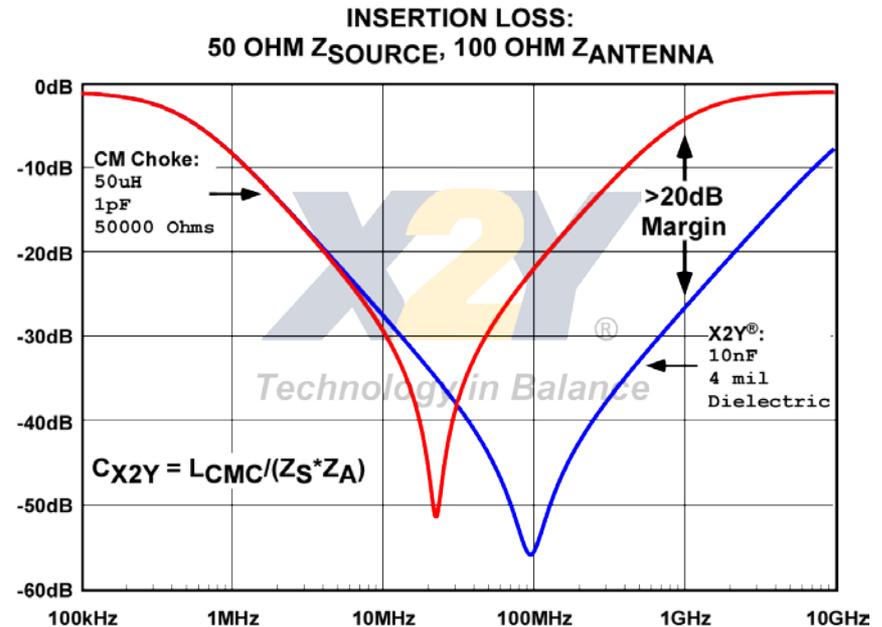
- Example
 - $50\Omega Z_{SOURCE}$
 - $100\Omega Z_{ANTENNA}$
 - $50\mu\text{H}$ CM Choke
- $C_{X2Y} = 50\mu\text{H}/(50\Omega * 100\Omega)$
 - 10nF rated value
 - 4 mil dielectric to ground
- X2Y[®] matches LF performance
- X2Y[®] provides $> 20\text{dB}$ insertion loss improvement @ 1GHz



X2Y[®] Capacitors, Best Practices Circuit 1


X2Y[®] Circuit 1 CM Filter

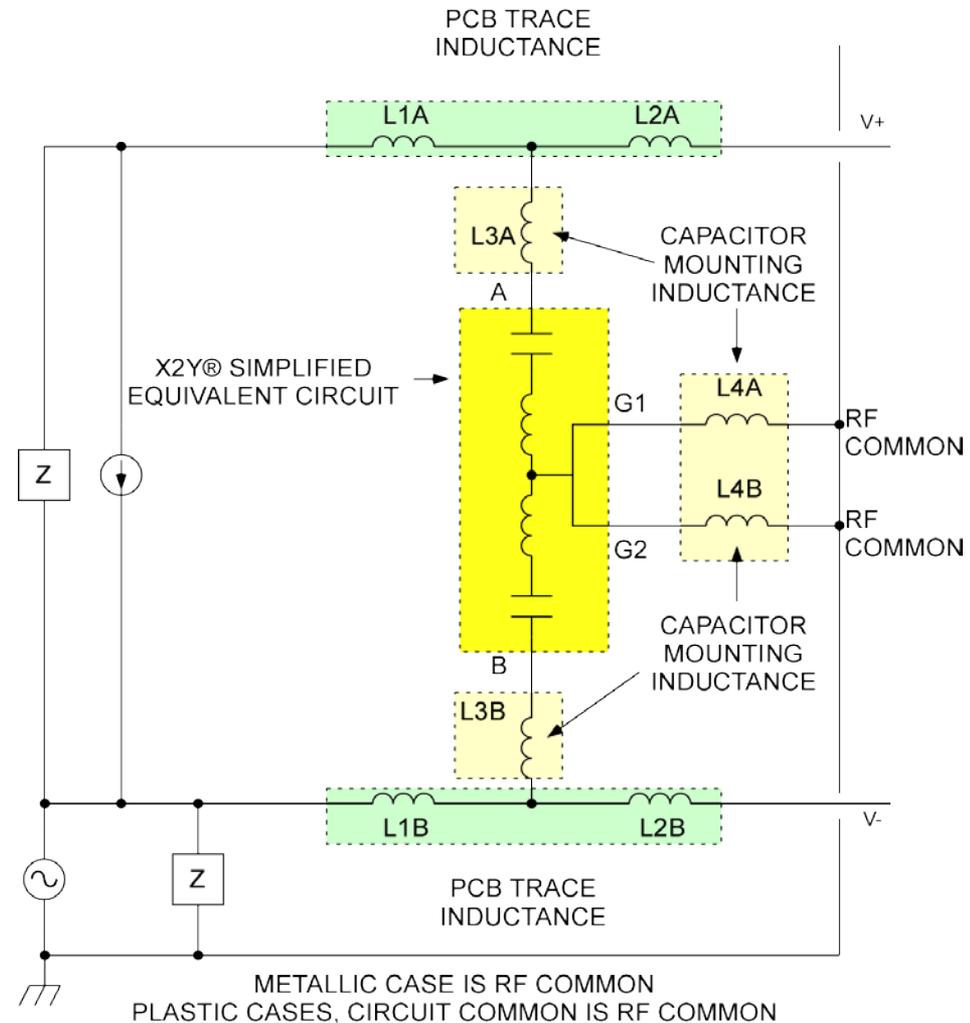- Performance is typically limited by external capacitor wiring inductance:
 - L3A/L3B, L4A, L4B
- Maximize performance by minimizing L3x, and L4x inductances.
 - Follow X2Y[®] mounting guidelines.
- L1x, and L2x inductance is OK and even beneficial when balanced.
 - Limitation on L2 is to keep connection close to egress.




X2Y[®] Capacitors, Best Practices Circuit 1

- Locate capacitors close to bulkhead
- Minimize, L3A, L3B
 - Connect A, B pad connections near base of pads
- Minimize L4A, L4B:
 - Connect G1/G2 to RF return polygon on an internal PCB layer as close to the capacitor surface as possible.
 - Chassis for metal enclosures
 - Power common plane for plastic enclosures.
 - 12mil vs 4mil upper dielectric costs about 3dB insertion loss @1GHz
 - Metal enclosures attach RF return polygon to chassis w/ low inductance
 - Multiple attachments along PCB edge recommended

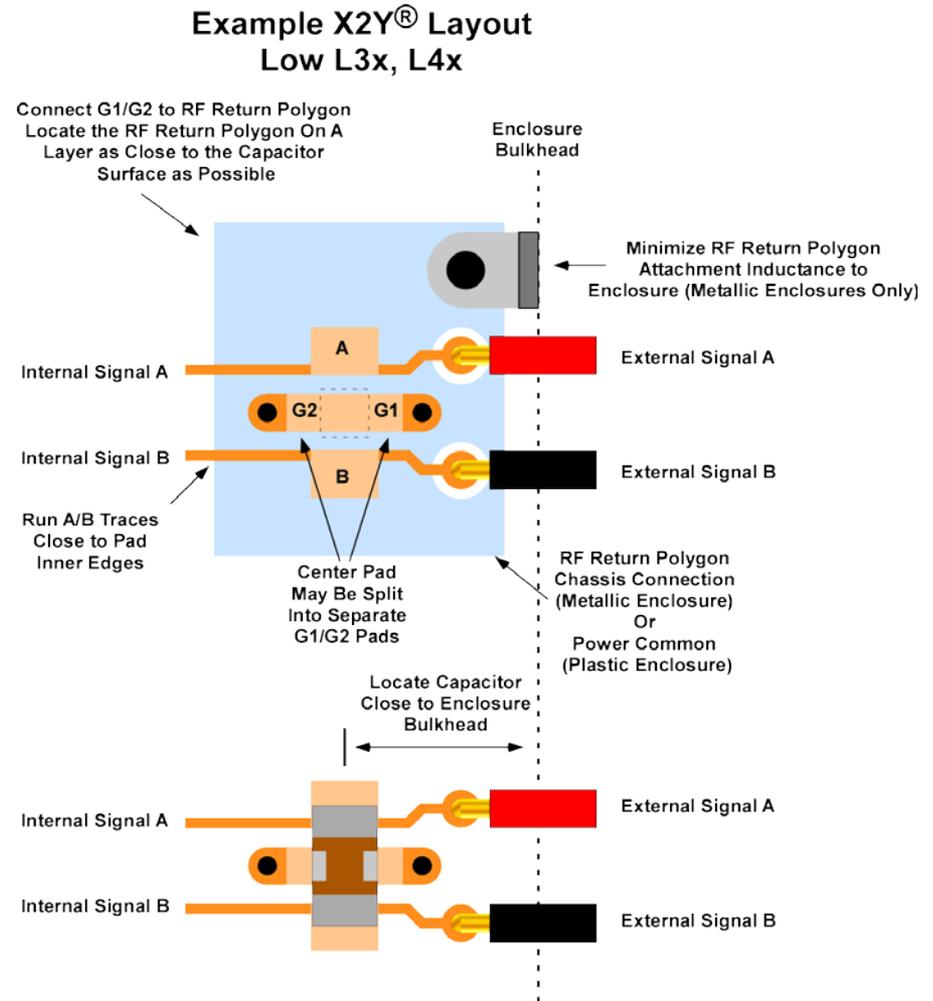

X2Y[®] Capacitors, Best Practices Circuit 1


Example X2Y[®] Layout Low L3x, L4x

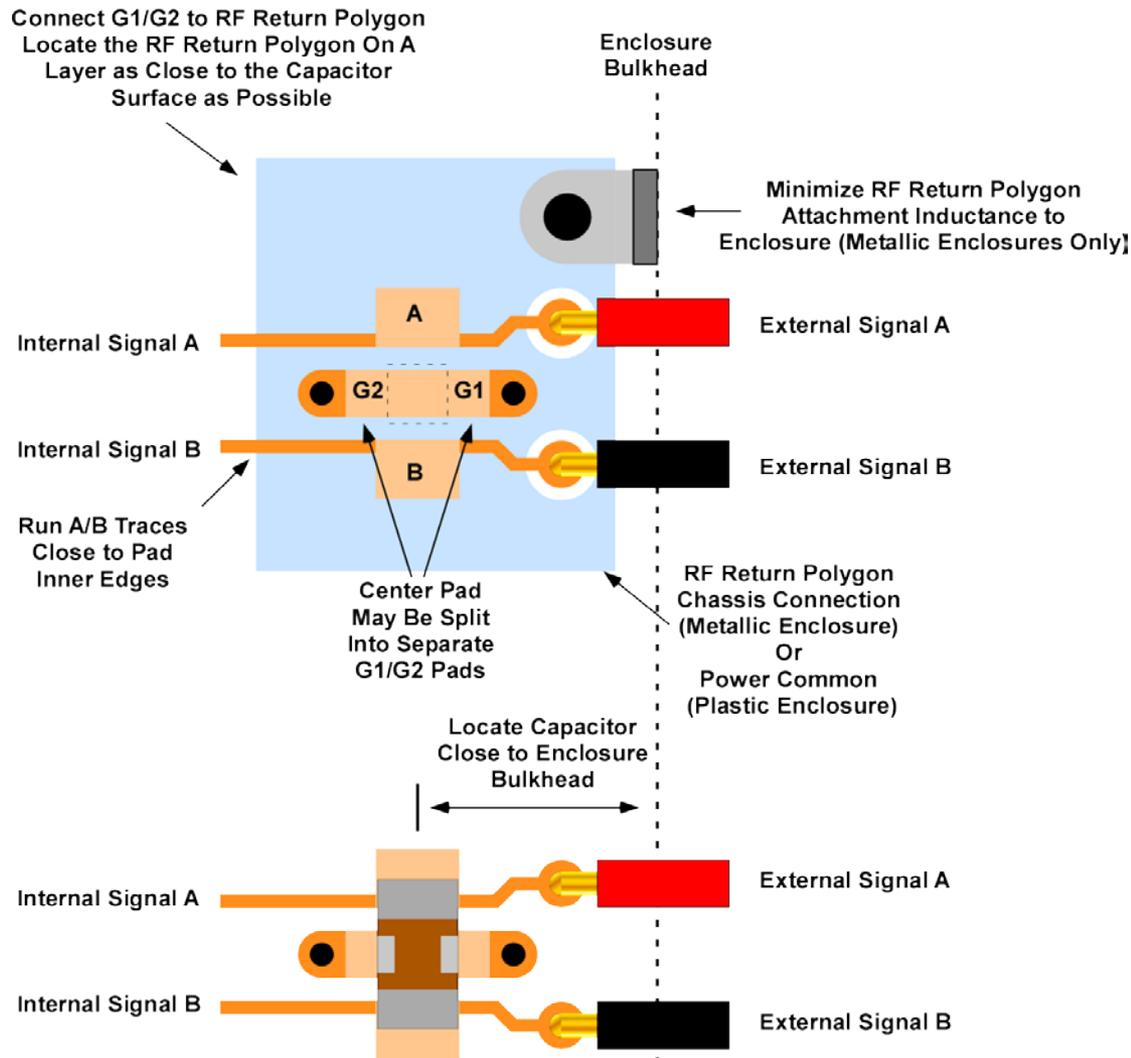

X2Y[®] Capacitors, Mounting Errors

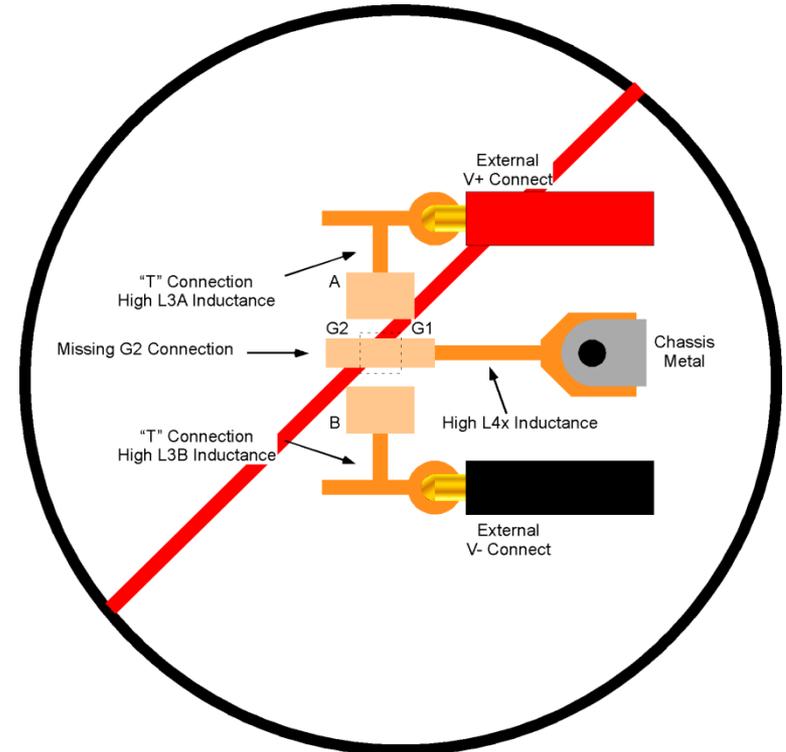Example, Circuit 1 Mount:

- AVOID THESE BAD PRACTICES:
 - “T” to A, or B pad connections
 - Leaving G2 unconnected
 - Stringer trace from any pad.
- Any of the above practices insert substantial inductance which impairs performance at high frequency.



Example X2Y[®] Layout
Mistakes to Avoid
High L3x, L4x


Summary

- Most EMI problems are Common Mode.
- Reduce common mode by attenuating driving voltage and/or mismatching antenna impedance.
 - Properly mounted X2Y[®] caps do both
- Series elements suffer from mode conversion and/or poor CM insertion loss at high frequencies.
- X2Y[®] capacitors maintain good CM insertion loss and mode conversion figures into the GHz.


Summary

- Magnetics noise suppression degrades as actual circuit antenna impedance increases above measuring instrument 50Ω impedance.
 - Real w/150Ω antenna is typically 3dB **worse** than 50Ω VNA measurement
- X2Y[®] noise suppression improves as actual circuit antenna impedance increases above measuring instrument 50Ω impedance.
 - Real w/150Ω antenna is 3dB **better** than 50Ω VNA
- X2Y[®] capacitor values may be easily selected to filter EMI based on any:
 - Required signal pass-band (sets max capacitor value),
 - Required noise stop-band (sets min capacitor value),
 - Improved replacement for existing CM magnetics

Summary

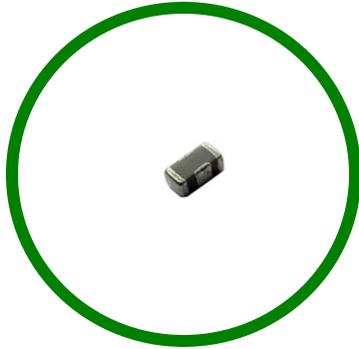

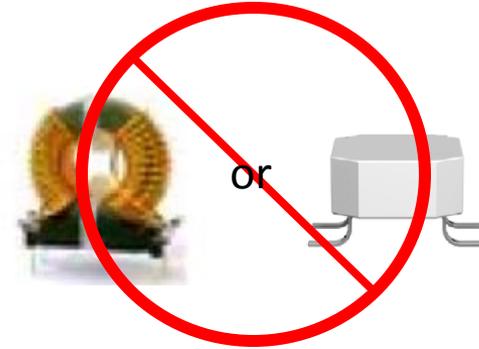- **X2Y[®]**
 - Small, Light
 - Lower Cost
 - Higher Reliability
 - Lowest Assembly Cost
 - Superior HF Performance



- **CM Choke**
 - Large, Heavy
 - Expensive
 - Subject To Vibration Induced Failure
 - Poor HF Performance